

OM
5

20

9574234622

Sujal Patel (+918121564132)

PM 1CB)


ECE


Digital Circuits.

Dr. Chakrapani.

Yeosamsetty Chakri @ gmail.com.

Best of luck

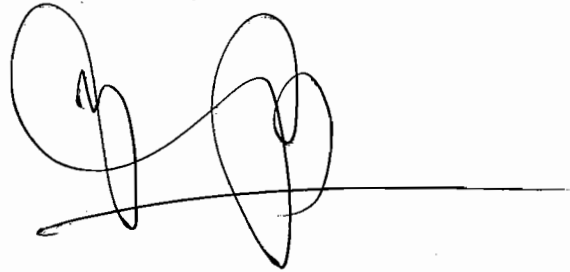 
A stylized handwritten signature consisting of several loops and a horizontal line extending to the right.




Applications

- ① Astable Multivibrators → Square wave generator
(Free running mv)
- ② Monostable multivibrators → { (a) Pulse generator
(b) Pulse stretcher.
(One shot mv)
- ③ Bistable multivibrators → 1-bit memory.

 * Astable Multivibrators Using Logic Gate.



'0', '1' = Unstable States.

 


$\therefore T = 60\text{ns}$

→ Time period of Square wave

$T = 2 \times (\text{sum of Propagation Delays of all Inverters})$

$\therefore f = \frac{1}{T}$


* Bistable Multivibrators.

 

NOTE:

- If odd no. of Inverters then ~~is~~ Astable mv.
- If even no. of Inverters then Bistable mv.

* Monostable Multivibrators

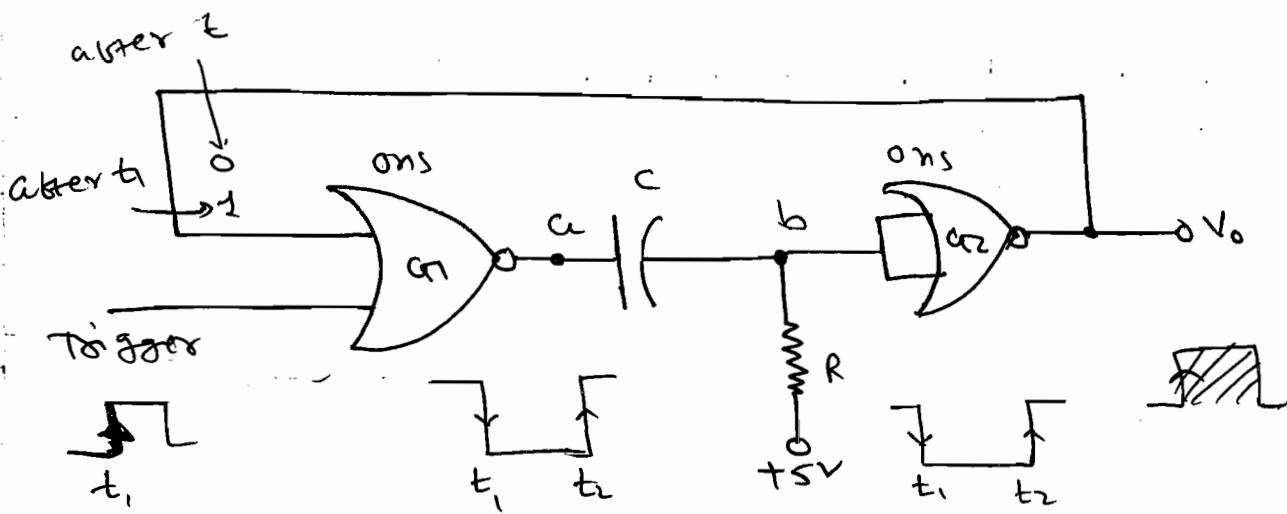


→ After T_1 , the feedback name at gate ① input is cancel to '1' which means the $V_a = 0$. Capacitor charges to +5V with time constant RC .

→ One's capacitor charges to +5 Volts.

$V_b = \text{logic '1'} \Rightarrow \boxed{V_o = 0}$ and $\boxed{V_a = 1}$ and


hence the capacitor discharges.

* Pulse Stretching

 


Ex = Determine the following multivibrators:

a)

 


→ So, it is Astable mv.

b)

 


c)

 


So, it is Astable mv

4

 


|||

 

→ Now it is look like monostable mv.

So, given ckt is monostable mv.

 Ex- In the following circuits determine the values of $Q_2, Q_1, Q_0 = ?$ if it is counting the following sequence $\rightarrow 101, 010, 110$



\rightarrow This is nothing but design a Sync Counter using D-FF which counts through for states 5, 2, 6, 5, ...


\rightarrow at time of design use excitation table
 \rightarrow at time of analysis use truth table.

\rightarrow

	P.S.			N.S			FF Inputs		
	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	D_2	D_1	D_0
⑤	1	0	1	0	1	0	0	1	0
②	0	1	0	1	1	0	1	1	0
⑥	1	1	0	1	0	1	1	0	1

\rightarrow $D_2 = Q_1$

$D_2 = \sum m(2, 5) + d(0, 3, 1, 4, 7)$

 

$\therefore D_1 = \bar{Q}_2 + Q_0$


$$D_1 = \sum m(6) + d(0, 1, 3, 4, 7)$$

	$\bar{a} \bar{b}$	$\bar{a} b$	$a \bar{b}$	$a b$
\bar{c}	x	x	x	0
c	x	0	<u>x</u>	<u>1</u>

$$D_1 = \bar{c} \bar{a} \bar{b} (a) \bar{c} \cdot a$$

★ Logic Families:

* Transistor as an Inverter:

 

$$V_{BE, \text{cutoff}} = 0.8V$$

$$V_{BE, \text{active}} = 0.7V$$

$$V_{CE, \text{sat}} = 0.2V$$

- (i) $V_i = 0V$; Q is OFF $\Rightarrow V_o = +5V$.
- (ii) $V_i = +5V$; Q is ON $\Rightarrow V_o = V_{CE, \text{sat}} = 0.2V$.

$\rightarrow I_B \geq I_{B, \text{min}}$

where $I_{B, \text{min}} = \frac{I_{C, \text{sat}}}{h_{FE}}$

$$\therefore I_B \geq \frac{I_{C, \text{sat}}}{h_{FE}}$$

$$\therefore \boxed{h_{FE} I_B \geq I_{C, \text{sat}}} \rightarrow \text{For } Q \text{ to be in Saturation.}$$

$$\rightarrow I_{C, \text{sat}} = \frac{V_{CC} - V_{CE, \text{sat}}}{R_C} = \frac{5 - 0.2}{1K} = 4.8 \text{ mA.}$$

$$\therefore I_B = \frac{V_i - V_{BE, \text{sat}}}{R_B} = \frac{5 - 0.8}{22} = \frac{4.2}{22} = 0.19 \text{ mA}$$

$$\therefore h_{FE} I_B = (20)(0.19) = \boxed{3.8 \text{ mA.}}$$

* Q is not in Saturation, because,

$$\boxed{h_{FE} I_B < I_{C, \text{sat}}}$$


NOTE: In the above circuits If $h_{FE} = 30$ then
 then $h_{FE} I_B = (30)(0.19) = 5.7 \text{ mA}$.

$$\therefore I_{C, \text{sat}} = 4.8 \text{ mA}$$

So, Transistor is in saturation, because

$$h_{FE} I_B > I_{C, \text{sat}}$$

* Transistor switching time:

 

t_d = delay time.

t_r = Rise time.


t_s = Storage time.

t_f = fall time.

$$\rightarrow t_{on} = t_d + t_r$$

$$t_{off} = t_s + t_f$$

* Parameters of Logic Gates:

 

$$V_{OH} > V_{IH} > V_{IL} > V_{OL}$$

2) Noise margin:

→ It is the amount of noise that can be allowed without disturbing the normal operation of logic gates.

$$NM_H = V_{OH} - V_{IH} = 2.4 - 2.0 = \boxed{0.4V} \quad \uparrow \text{ (-ve noise)}$$

$$NM_L = V_{IL} - V_{OL} = 0.9 - 0.4 = \boxed{0.5V} \quad \downarrow \text{ (+ve noise)}$$

$$\therefore N.M. = \min(NM_H, NM_L)$$


$$= \min(0.5, 0.4)$$

$$\therefore \boxed{NM = 0.4V}$$

③ Fanout:


→ It is the no. of standard load o/p of gate can drive without impairing its normal operation. The standard load is input current of a logic gate which belongs to the family of driving gate.

(a)

 

$$Fan\ out_H = \frac{I_{OH}}{I_{IH}} = 10.$$

(b)

 

$$Fan\ out_L = \frac{I_{OL}}{I_{IL}}$$

$$= \frac{24}{2}$$

$$Fan\ out_L = 12$$

→ $F_{out} = \min (F_{outH}, F_{outL})$.

$\geq \min (10, 12)$

$\therefore F_{out} = 10$


④ FOM (figure of Merit).

→ Prop. delay (ns) X power dissipation (mW) ⇒ Picojoules (PJ).

→ It is used to compare two gates in terms of its performance.

- ① DTL
- ② modified DTL
- ③ TTL
- ④ ECL.

① DTL (Diode Transistor Logic).

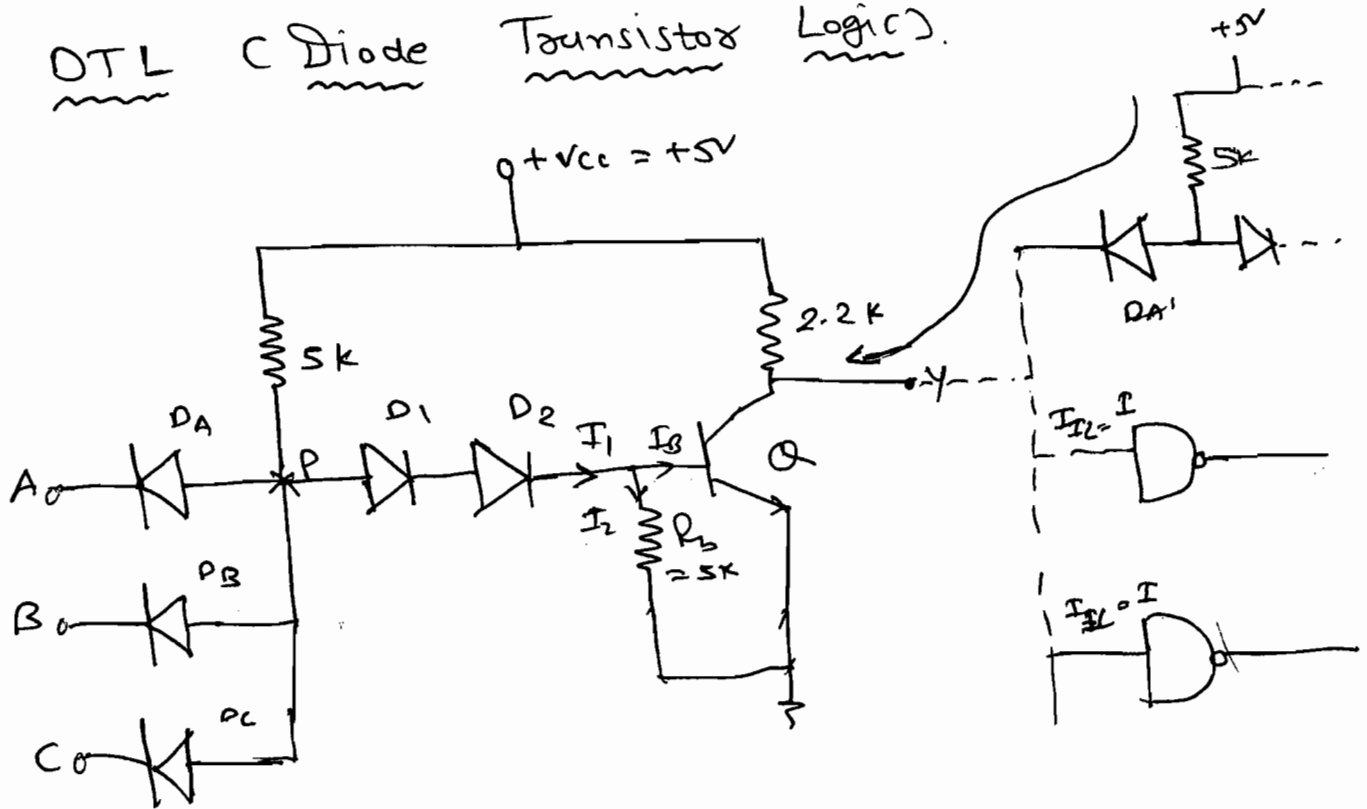

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


D_A, D_B, D_C are ON
 D_1, D_2, D_3 are OFF $\Rightarrow Y = +5V$.

D_1, D_2, Q are OFF $\Rightarrow Y = +5V$

D_A, D_B, D_C are OFF
 D_1, D_2, Q are ON,

$$Y = V_{CE, sat} = 0.2V.$$

So, it is NAND gate.

 

→ (i) when Q is on the voltage at P

$$V_P = 0.7 + 0.7 + 0.8 = \boxed{2.2V}$$

$$(ii) \text{ when } Q \text{ is OFF } \Rightarrow V_P = 0.7 + 0.2 = \boxed{0.9V}$$

→ For Q to be in saturation.

$$h_{FE} I_B \geq I_{C, sat} + N \cdot I.$$

$$I_{C, sat} = \frac{5 - V_{CE, sat}}{2.2} = \frac{4.8}{2.2} = \boxed{2.18 \text{ mA}}$$

Stand. Load $I = ?$

$$I = \frac{5 - V_A' - V_{CE, \text{sat}}}{5} = \frac{5 - 0.7 - 0.2}{5}$$

$$\therefore I = \frac{4.1}{5} = \boxed{0.82 \text{ mA}}$$

$$\rightarrow I_1 = \frac{5 - V_P}{5} = \frac{5 - 2.2}{5}$$

$$\therefore I_1 = \frac{2.8}{5} = \boxed{0.56 \text{ mA}}$$

$$\rightarrow I_2 = \frac{V_{BE, \text{sat}}}{R_b} = \frac{0.8}{5} = \boxed{0.16 \text{ mA}}$$

$$\therefore I_B = I_1 - I_2 = 0.56 - 0.16$$

$$\therefore \boxed{I_B = 0.4 \text{ mA}}$$

Let, $h_{FE} = 30$.

$$\therefore 30 \times 0.4 \text{ mA} \geq 2.18 \text{ mA} + N \cdot (0.82) \text{ mA}$$

$$\therefore 12 \geq 2.18 + (0.82 \times N)$$

$$\therefore 9.82 \geq 0.82 \times N$$

$$\therefore N \leq \frac{9.82}{0.82}$$

$$\therefore N = 11.97$$

$$\therefore \boxed{N = 11}$$


$$\therefore \boxed{\text{Fanout} = 11}$$

→ In OTL two Diodes D_1 & D_2 are used to increase the noise margin of the logic gates.

→ At In OTL, the R_b resistor is used to reduce the storage time of the transistor which in turn reduces the switch off time of the transistor.

② Modified OTL Gate:

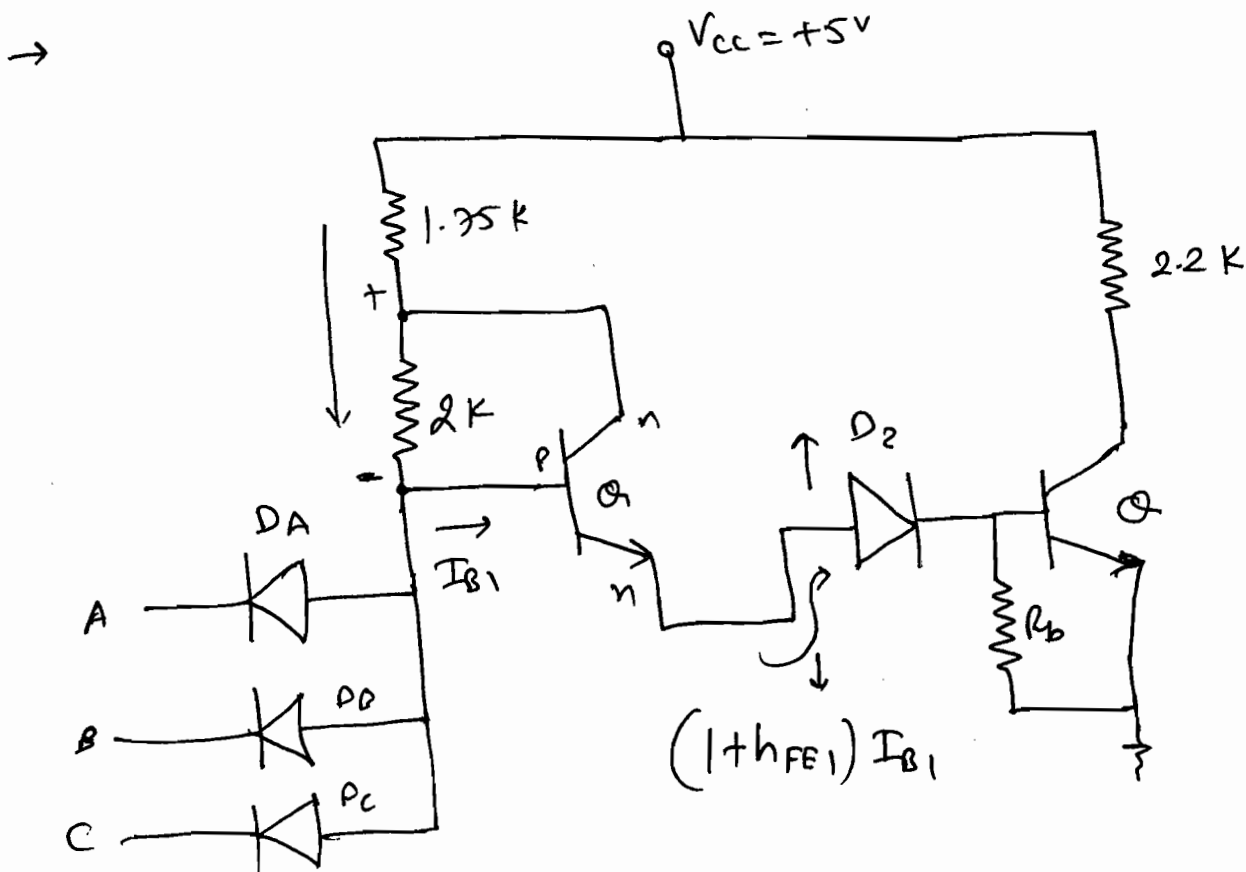→ In modified OTL the Diode D_1 is replaced by a transistor in active region which increases the base current of Q . hence the fanout of the Logic increases




→ 'Q' is in Active region.

③ TTL : (Transistor Transistor Logic). (switched).

- (a) open collector.
- (b) Totempole.
- (c) Tri-State.

→ (a) open collector.

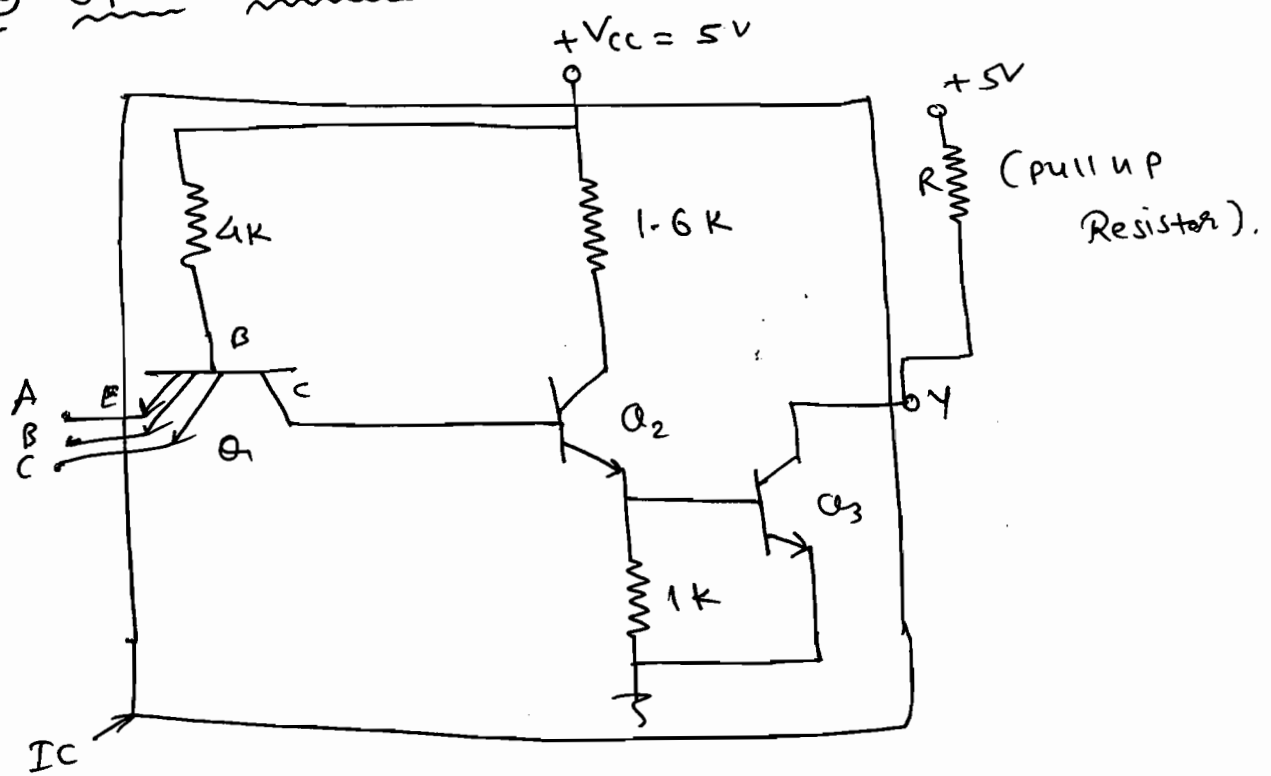


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Q1 is in forward Active region mode
 Q2 and Q3 are OFF ⇒ Y = +5V

Q1 is in Reverse active
 Q2 is ON, Q3 is ON, Y = V_{CE(sat)}



Y = 0.2V

→ So, it is NAND gate.

 


* Advantages:

  - (1) Open Collector TTL
- Wired-AND Logic. ✓



* Disadvantage:

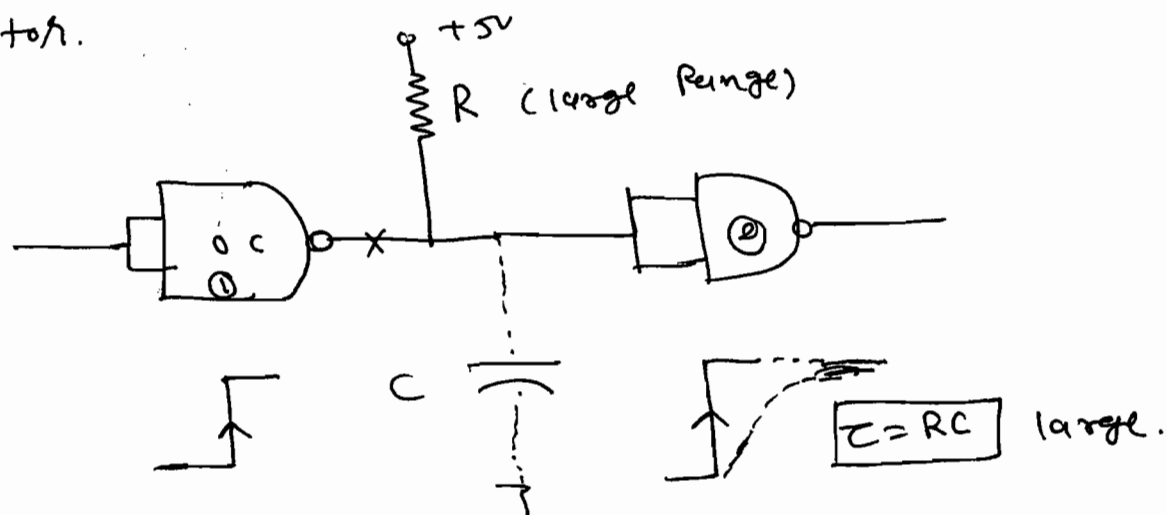→ In open collector TTL, the stray capacitance at the I/P of the driven gate takes more time to change the voltage levels, because of high time constant $\tau = RC$, where $R = \text{pull up resistor}$.




② Totem Pole: TTL;

→ To increase the speed of TTL the passive pull-up resistor is replaced by active pullup which is an emitter follower whose current gain is more and the O/P resistance is less. Hence, the time constant is $\tau = R_o \cdot C$

where

$$\tau = R_o \cdot C$$

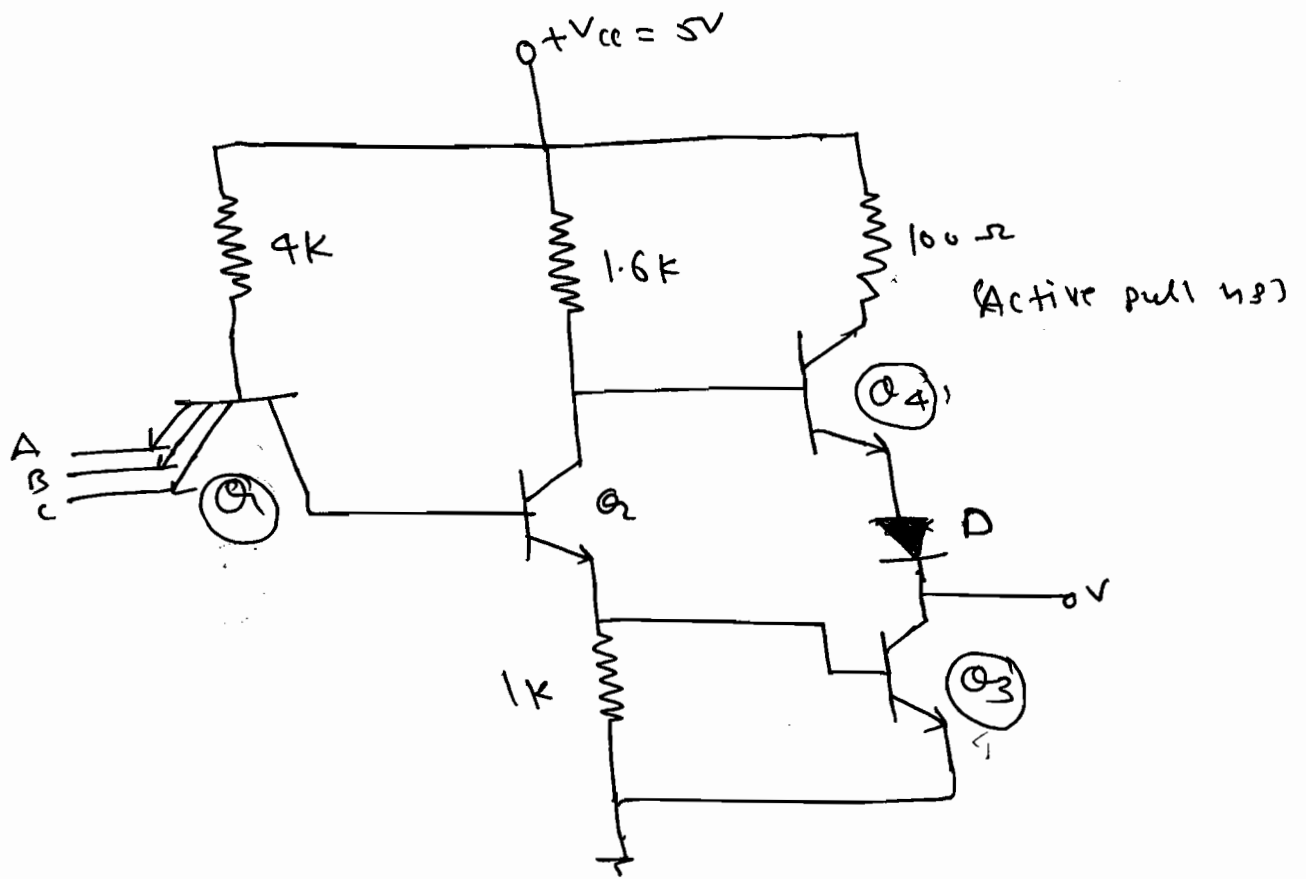where, $R_o =$ output resistance of emitter follower.



Q4 → Emitter follower

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Q1 is in Forward Active mode
 Q2, Q3 are OFF ⇒ Y = +5V
 Q4 ON

Q1 is Reverse Active mode
 Q2, Q3 are ON,
 $V = V_{CE, sat} = 0.2V$
 Q4 OFF, D is OFF.

→ In TTL Logic floating inputs are considered as Logic-1.

→ Q_2 is called phase splitter because it will maintain the exclusive condition betⁿ Q_3 & Q_4 . that is one of them is on other one is off.

* Advantage:

→ High Speed of operation because of less time constant $\tau = R_o \cdot C$
→ $R_o =$ output resistance emitter follower.

* Disadvantage:


→ (i) As switch off time is more than switch on time, for a short period of time both Q_3 & Q_4 will be in the on condition which results in large current drawn from the supply.

(ii) Wired AND logic is not possible with Totem pole TTL.

⇒ To improve the speed of Totem pole TTL Q_4 and D are replaced by Darlington pair which has high current gain and very low o/r resistance.

③ Tristate TTL:

→

 

IB $C=0$ \Rightarrow $y = \overline{A \cdot B}$

IB $C=1$ \Rightarrow $y = 'z'$ high Imp. state.


→ When $C=1$

\Rightarrow 'Both Q_3 and Q_2 will become OFF.

→ Tristate TTL are used in Bus Configuration of Micro Computers.

③ ECL (Emitter Coupled Logic).

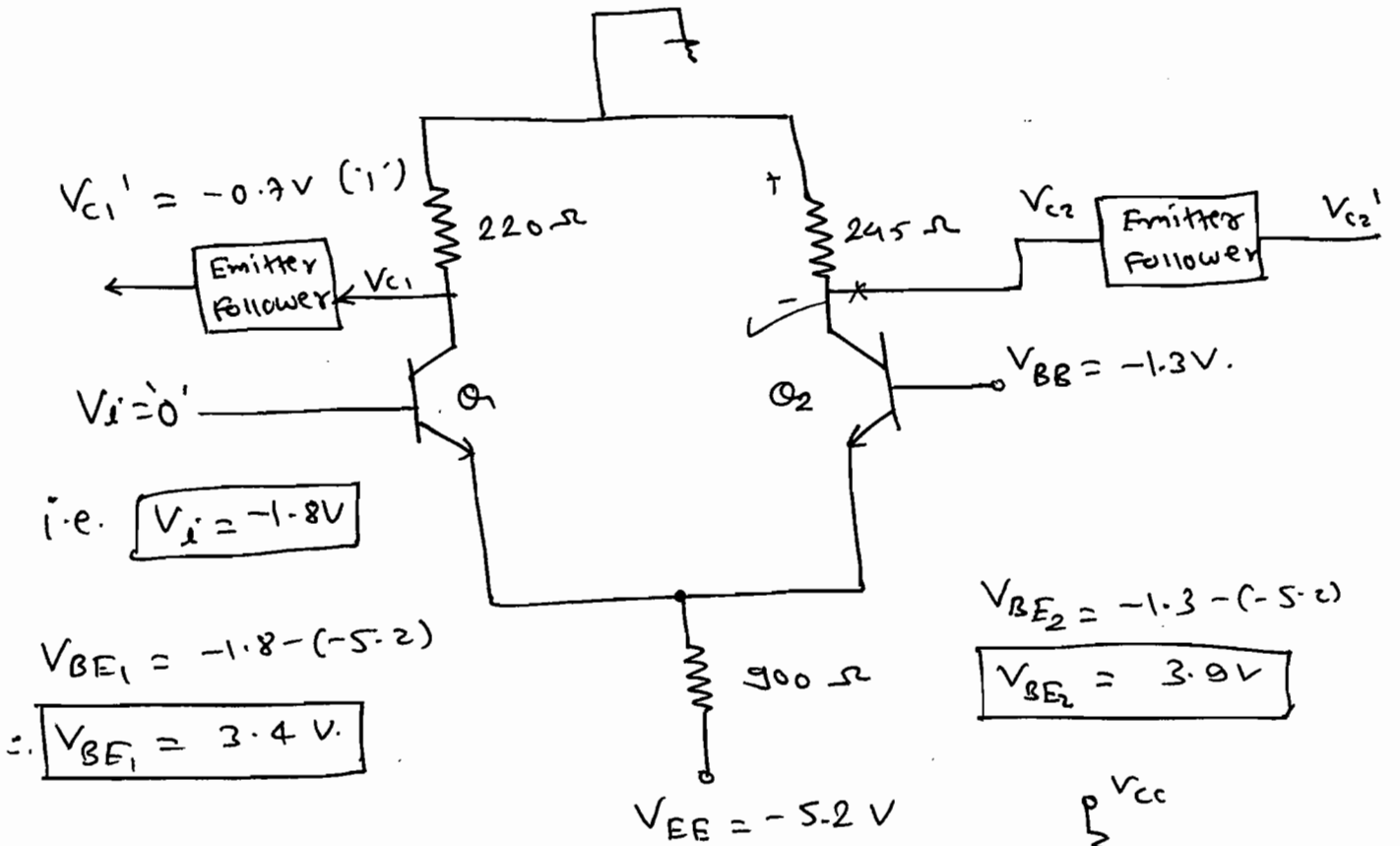(OR) Non-Saturating Logic,
CML (Current Mode Logic).




$\therefore V_{C2} = -I_{E2} \cdot R_{C2}$

$\therefore V_{C2} \approx -I_{E2} \cdot R_{C2}$

$\therefore I_{E2} = \frac{V_{BB} - V_{BE} - V_{EE}}{0.9}$

$\therefore = \frac{-1.3 - 0.7 - (-5.2)}{0.9}$

 $\therefore I_{E2} = \frac{3.2}{0.9} = 3.555 \text{ mA}$



$\therefore V_{C2} = -0.9V$

V_i	Transistor	Outputs.
$0'$ $= -1.8V$	Q_1 OFF Q_2 ON (Active Region)	$V_{C1} = 0$; $V_{C1}' = -0.7V$ (i') $V_{C2} = -0.9V$; $V_{C2}' = -0.9 - 0.7 = -1.6V$ (o')

V_i	Transistor	outputs.
'1'	Q_2 OFF	$V_{c1} = -0.9V$; $V_{c1}' = -1.6V$ ('0')
$(-0.8V)$	Q_1 ON (Active region)	$V_{c2} = 0$; $V_{c2}' = -0.7$ ('1')

(ii) If $V_i = \bar{1} = -0.8V$.

$$V_{BE1} = 4.4V;$$

$$V_{BE2} = 3.9V.$$


Hence Q_1 conducts, Q_2 is OFF.

→ From the above table we can observe

that

$$\begin{aligned} V_{c1}' &= \overline{V_i} \\ V_{c2}' &= V_i \end{aligned}$$

→

 


* Advantage:

- High Speed of operation because it is in non-saturating logic.
- No current spikes.
- High Fanout (≈ 25).

④ Both NOR and OR gates are available.

⑤ Wired-OR logic is possible.

 


* Disadvantages:

- ① High Power dissipation because the Transistors operate in active region.
- ② The Noise margin of ECL gate is very less. [$\approx 0.31V$]

Sr. No.	Parameters	Bipolar			MOSFET family	
		OTL	TTL	ECL	MOS	CMOS
1)	Fanout	8	10	25	20	>25
2)	Power Dissipation (mw)	8-12	12-22	40-55	0.2-1	0.01
3)	Prop. Delay.	30	6-12	1-4	300	70x
4)	Noise Immunity	Good	Very good	Fair	Good	Very good

→ BIMOS: Bipolar + MOSFET.

* RTL (Resistor Transistor Logic).

 


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$\left. \begin{matrix} 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \end{matrix} \right\} \begin{matrix} Q_A, Q_B, Q_C \text{ are OFF} \\ Y = +5V. \\ Y = V_{CE, sat} = 0.2V \end{matrix}$

$Y = \overline{A+B+C}$

So, it is NOR gate.

 

→ RTL has more resistors so it occupies more space than MOSFET families so it is outdated.


* I²L : Integrated Injection Logic. 25

→ I²L is obtained from RTL by making three changes:

(i) Base Resistors are omitted.

(ii) PNP transistor is used in place of collector Resistor.

 (iii) Multicollector transistors are used.



* advantages:


(i) High package density.

(ii) Low power and prop. delay product.


→ In I²L the speed of operation can be controlled by choosing the voltage input of PNP transistor appropriately.

⇒ The high threshold logic (HTL) family is having high noise margin (NM) $\approx 7.1V$.


★ Semiconductor memories:

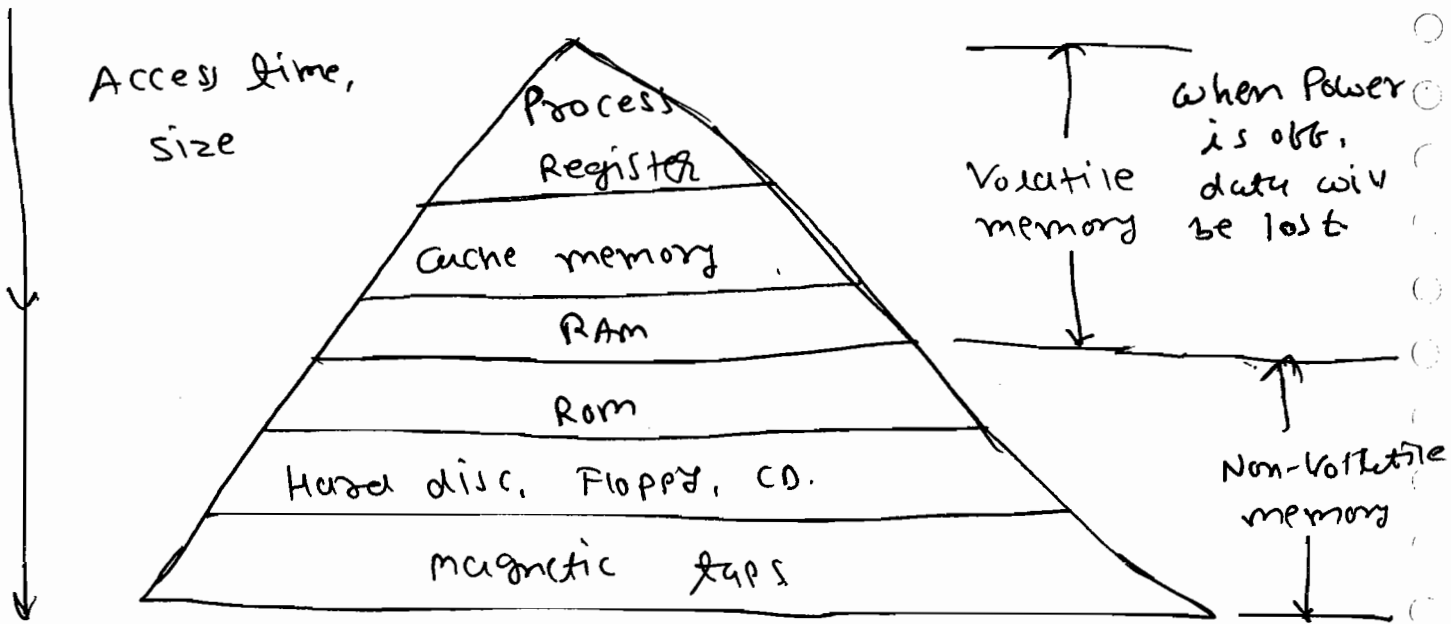

* Semiconductor memory.

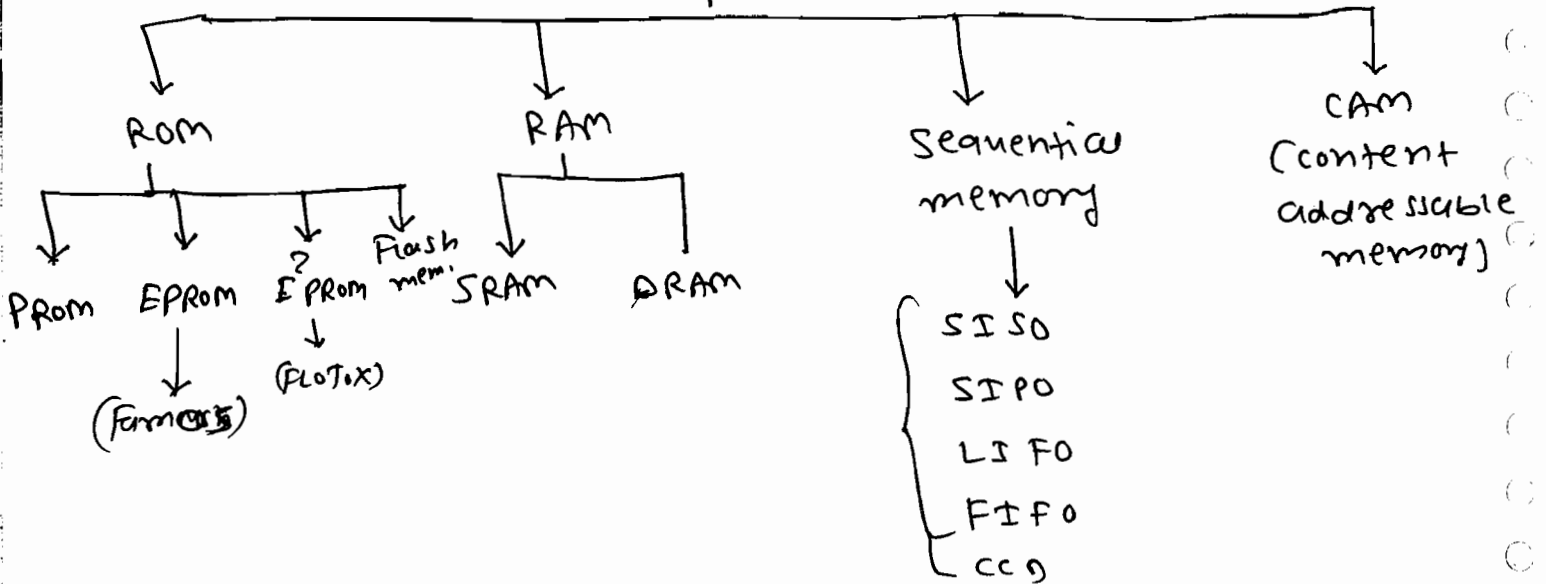

* Rom using Diode matrix:

 


→ Rom of Combinational circuits,

$$\begin{cases} Y_2(A,B) = \Sigma m(1,2). \\ Y_1(A,B) = \Sigma m(0,1,3). \\ Y_0(A,B) = \Sigma m(0,2). \end{cases}$$

$$\text{Rom size} = 2^x \times 8 = 2^2 \times 8 = \boxed{12}.$$

* Prom: (Programmable Rom) (OTP Rom)


(one time programmables).

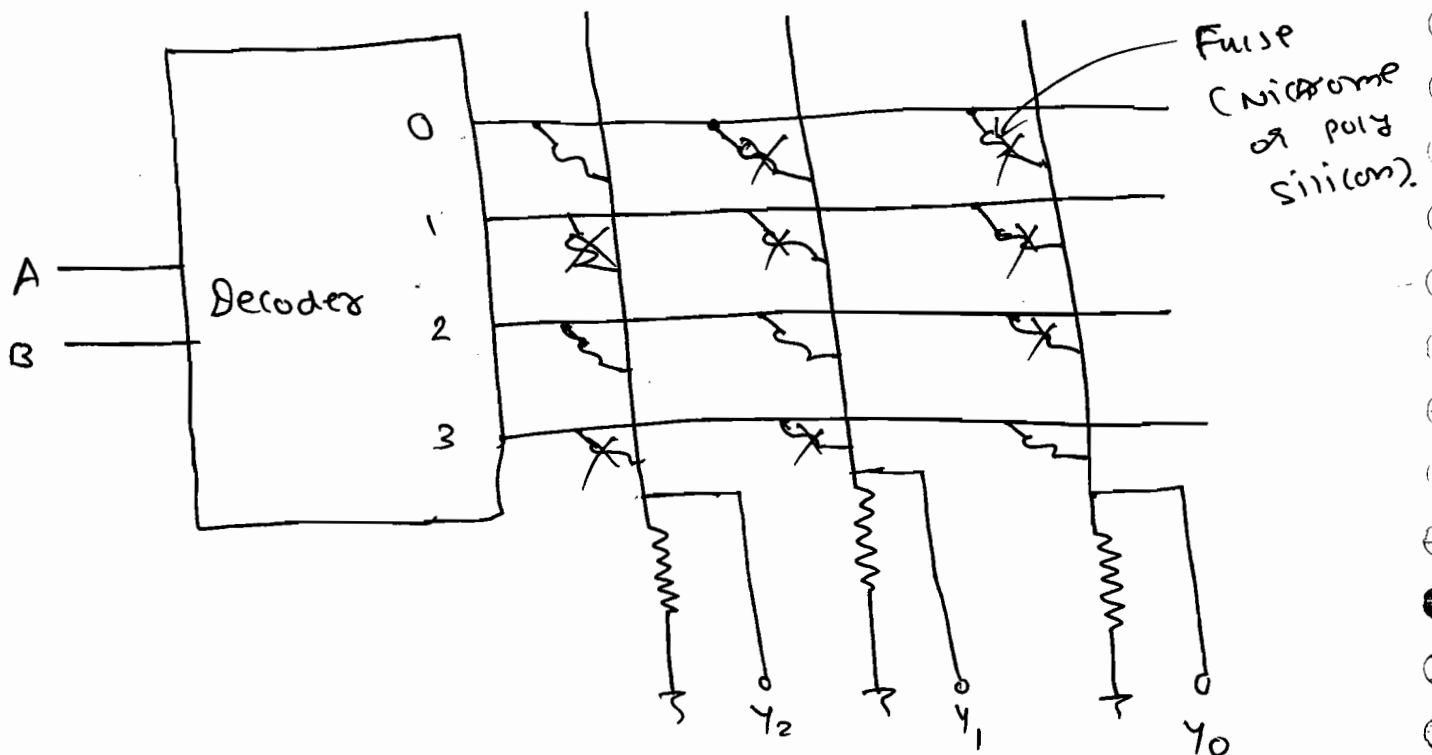

$$Y_2(A, B) = \sum m(1, 3).$$

$$Y_1(A, B) = \sum m(0, 1, 3).$$

$$Y_0(A, B) = \sum m(1, 2, 3).$$

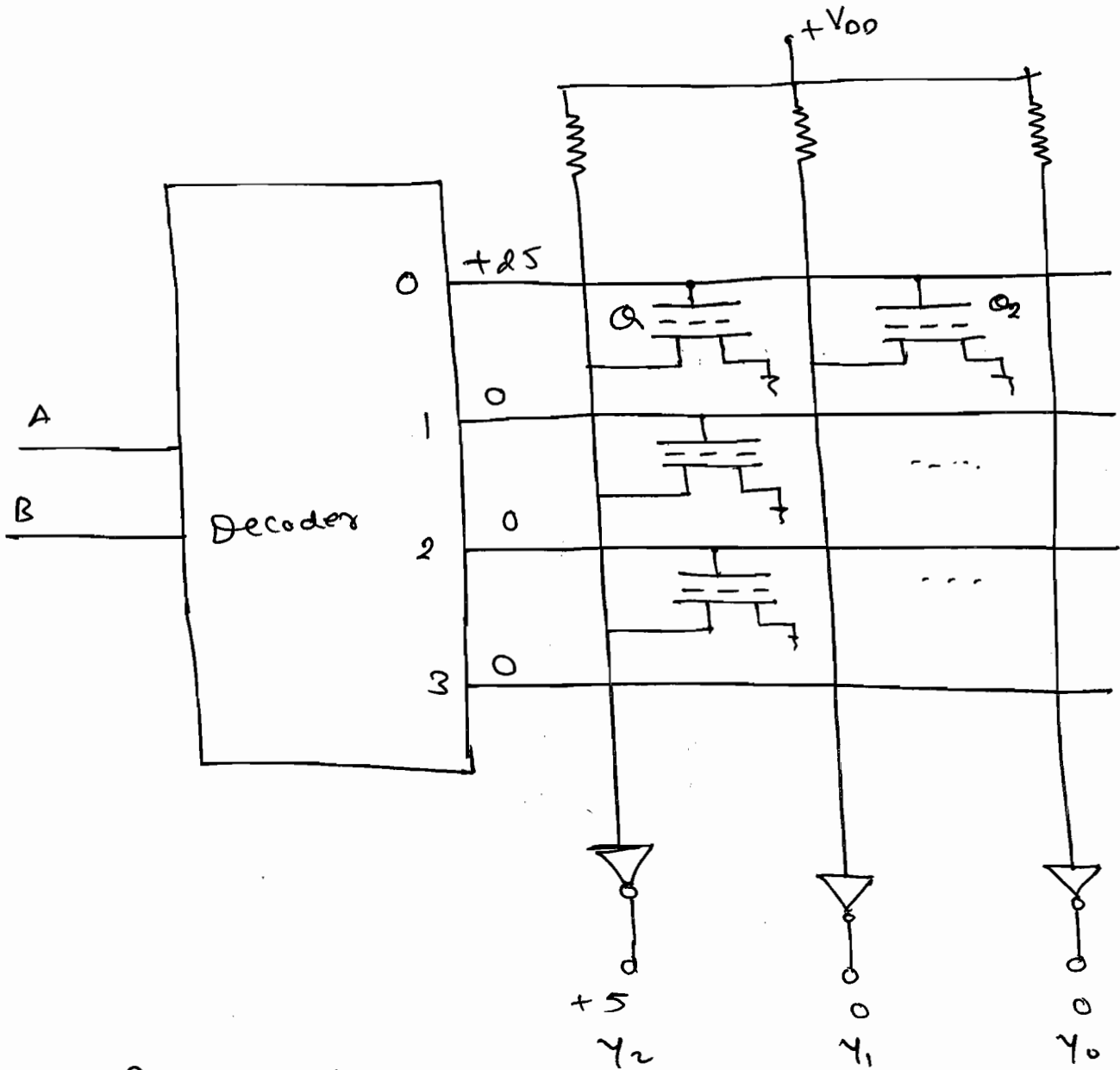

(1) Programming:

$\left\{ \begin{array}{l} Q_1 \rightarrow \text{has trapped electrons on floating gate} \\ Q_2 \rightarrow \text{has no trapped electrons on floating gate} \end{array} \right.$


(2) Reading:

→ In a floating gate MOSFET if the electrons are trapped on the floating gate it results in increasing in threshold voltage to 7V.
 → Hence, for 5V Q_1 is going to be off and Q_2 is on and corresponding outputs are

$V_2 = 0$ and $V_1 = 1$.

③ Erasing:

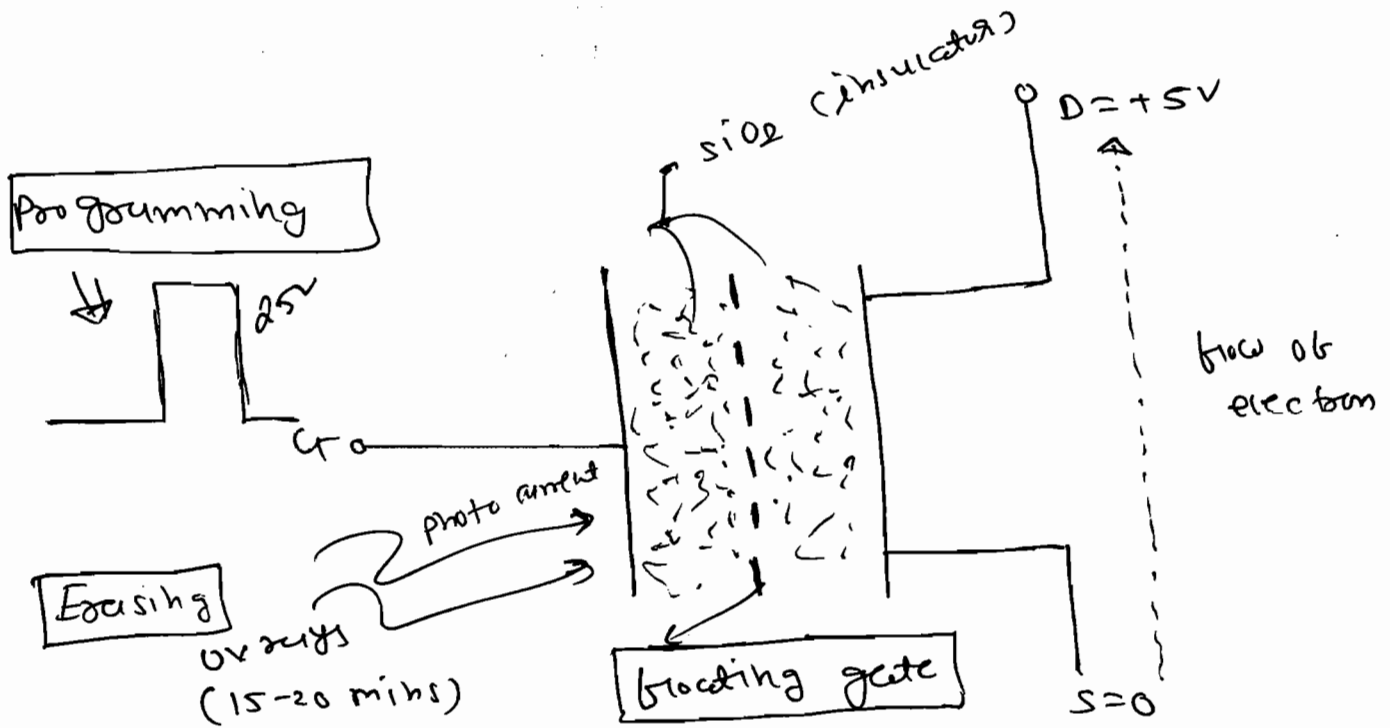→ To erase we have to use Ph UV rays bombarded into it so that the electrons goes into their normal condition.



* Disadvantages:

- (i) In system programming (ISP) not possible.
- (ii) Erasing takes more time.
- (iii) Partial erasing is not possible.

⇒ other name of it is

FAMOS
↓
Floating gate Avalanche injected MOSFET.

* E²PROM (Electrically Erasable PROM). 31

→ In E²PROM the thickness of silicon oxide layer in floating gate MOSFET is reduced because of this, 5 to 10V of programming pulse is sufficient to ~~erase~~ ^{trap} the electrons on the floating gate.



→ The MOSFET can be erased by reversing the polarity at the gate input.

FIOTAX

(a) Programming



(b) Erasing:

  

→ Floating gate tunneling oxide MOSFET.

flow of electrons

* Advantages:

- (1) Partial erasing is possible.
- (2) ISP (In system programming) is possible.
- (3) Erasing takes very less time.

* Disadvantages:

→ It has low package density because each bit

requires 2 MOSFETS one floating gate MOSFET and another one is ordinary MOSFET.

(2) High cost per bit.


* Flash Memory:

→ Advantages of Flash memory.

- ① High package density
- ② Partial Erasing
- ③ Isp is possible.
- ④ Low cost.
- ⑤ more no. of read/write cycles.

(c) SRAM (1 bit mem. cell) (Static RAM)

⇒ writing

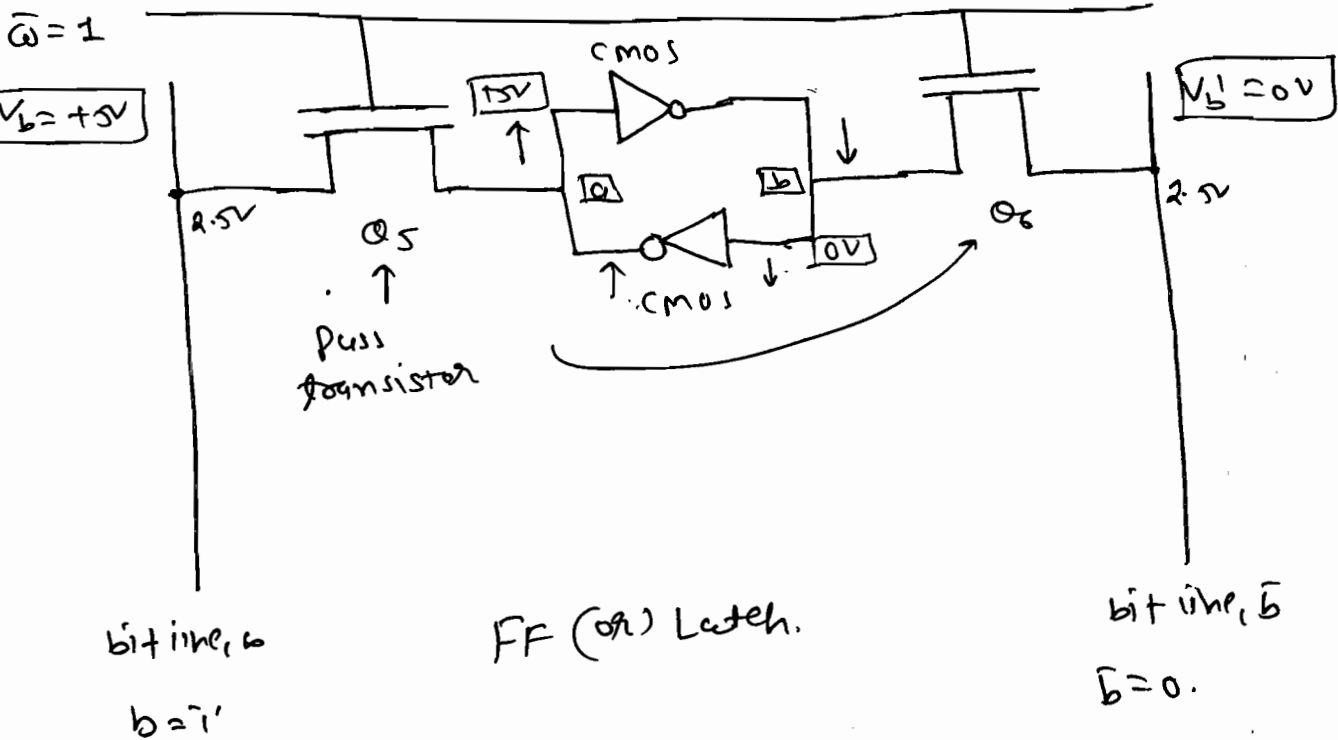

→ To store Logic '1' in SRAM cell.


- ① bit lines are precharged to $2.5V$
 - ② Choose $W=1$; $V_b = +5V$; $V_{b'} = 0V$.
 - ③ ' V_a ' rises to $+5V$; V_b drops to $0V$.
- Thus logic '1' is store in SRAM cell.

→ To Read SRAM Cell.

- ① Choose $W=1$.
- ② Q_5, Q_6 MOSFET are ON.
- ③ Hence, $b = '1'$, $\bar{b} = 0$.

(2) DRAM: (Dynamic RAM).

⇒

 

a) To write: Choose $W=1$; $V_b = +5V$ ⇒ Logic '1' is stored.

b) To Read: choose $W=1$
 ⇒ If bit line = $+5V$ ⇒ Logic '1'.
 ⇒ If bit line = $0V$ ⇒ Logic '0'.

SRAM

DRAM

Advantages:

- ① Speed is very high. (cache memory).
- ② Less hardware complexity.

- ① High package density.
- ② Low power consumption.
- ③ Less cost.

Disadvantages:


- ① Low package density
- ② High power consumption
- ③ High cost

- ① Speed is less. (primary memory)
- ② more hardware complexity.


because the voltage across capacitor has to be refreshed at regular interval of time 2-4ms by using Refreshing clock.

★ CAM:


(a)

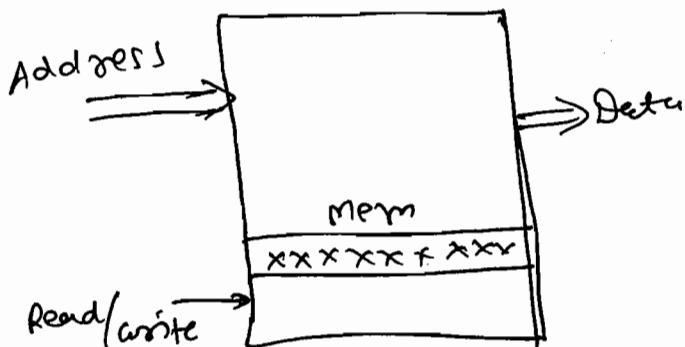

(b)

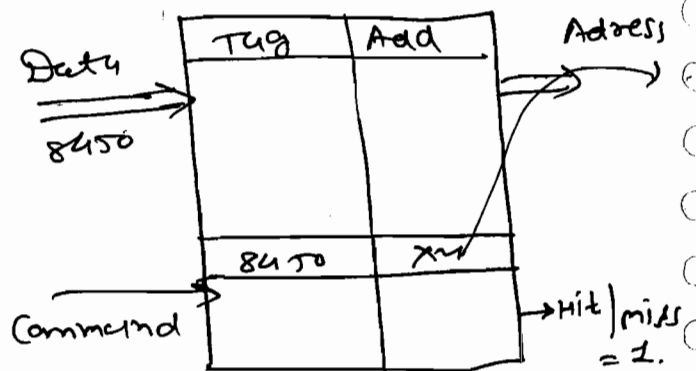

⇒ Cache memory:

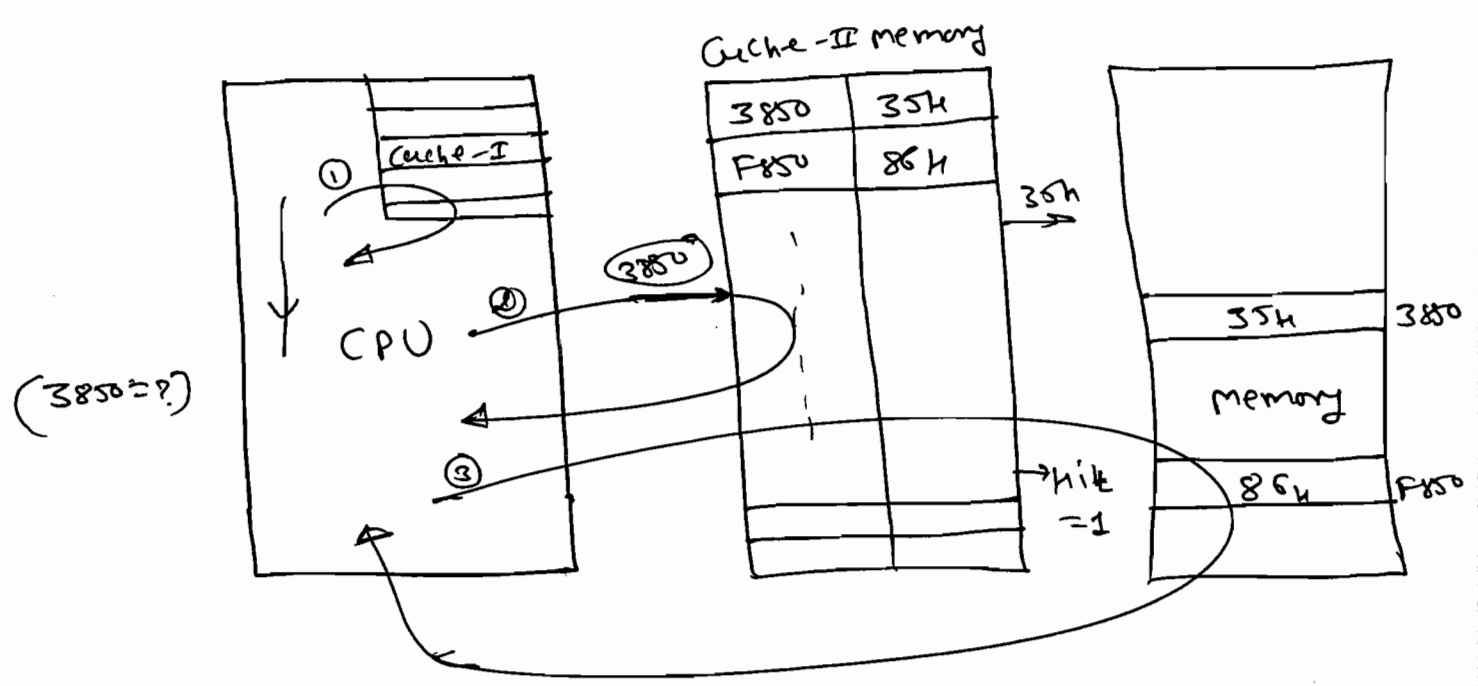


★ Digital to Analog Converter (DAC).


- (a) Binary weighted Resistor DAC.
- (b) R-2R Ladder DAC.

★ Analog to Digital Converter (ADC).

 - (a) Counter Type ADC
- (b) Successive Approx ADC.
- (c) Flash (or) Parallel ADC.
- (d) Dual slope (or) Integrating ADC.
- (e) signal - delta ADC ($\Sigma - \Delta$ ADC).



CLK	Counter	V_o
0	0000	0V
1	0001	(let) 1V
2	0010	2V
3		⋮
⋮		⋮
15	1111	15V
16	0000	0V

 

(1) F_{SO} (Full Scale O/P) = 15V

→ N-bit DAC = $(2^N - 1) \times \text{Stepsize}$.

(2) (a) Resolution:

→ It is the minimum change possible at the O/P of the DAC for any change in the digital input.

(a) Resolution = stepsize (volts).

(b) % Resolution = $\frac{\text{Stepsize}}{F_{SO}} \times 100$

= $\frac{\text{stepsize}}{(2^N - 1) \times \text{Stepsize}} \times 100$


= $\frac{100}{2^N - 1}$

∴ where N = size of DAC.

$\frac{DAC}{\checkmark 0.1V}$
 $0.5V$
 $1.0V$


$\frac{DAC}{8\text{-Bit}}$
 16-Bit
 $32\text{-Bit} \checkmark$

Ex 1

 


CLK | Counter | V_o


CLK	Counter	$V (V)$
0	0 0 0	0
1	1 0 0	4
2	1 1 0	6
3	1 1 1	7
4	0 1 1	3
5	0 0 1	1
6	0 0 0	0

 

1) Binary Weighted Resistor DAC:

 

 
① Let, $a_{N-1} = 1$; other Input bits = 0 $\Rightarrow V_0 = ?$



$$\therefore V_0 = (-V_R) \left(\frac{-R_F}{2R_F} \right)$$

$$\therefore \boxed{V_0 = \frac{+V_R}{2}}$$

 ② Let $a_n = 1$; other Input bits = 0 $\Rightarrow V_0 = ?$



$$V_0 = (-V_R) \left(-\frac{R_F}{2^{N-1}R} \right)$$

$$\therefore V_0 = \frac{V_R}{2^N} \text{ Volts.}$$

Resolution = Stepsize.


Disadvantages:

- ① It requires wide range of resistors.
- ② Using this DAC the stepsize may not be constant because it is difficult to maintain the ratio of two consecutive resistors equal to constant practically.



In general,

$$\therefore V_0 = V_R \left[\frac{a_0}{2^N} + \frac{a_1}{2^{N-1}} + \dots + \frac{a_{N-1}}{2} \right]$$

 ② 2-Bit R-2R Ladder DAC (Voltage Switched)



  
① Let $a_2 = 1 ; a_1 = a_0 = 0 \Rightarrow V_0 = ?$



$$\therefore V_0 = \left(-\frac{V_R}{2}\right) \left(-\frac{3R}{3R}\right)$$


$$\therefore V_0 = \frac{V_R}{2}$$

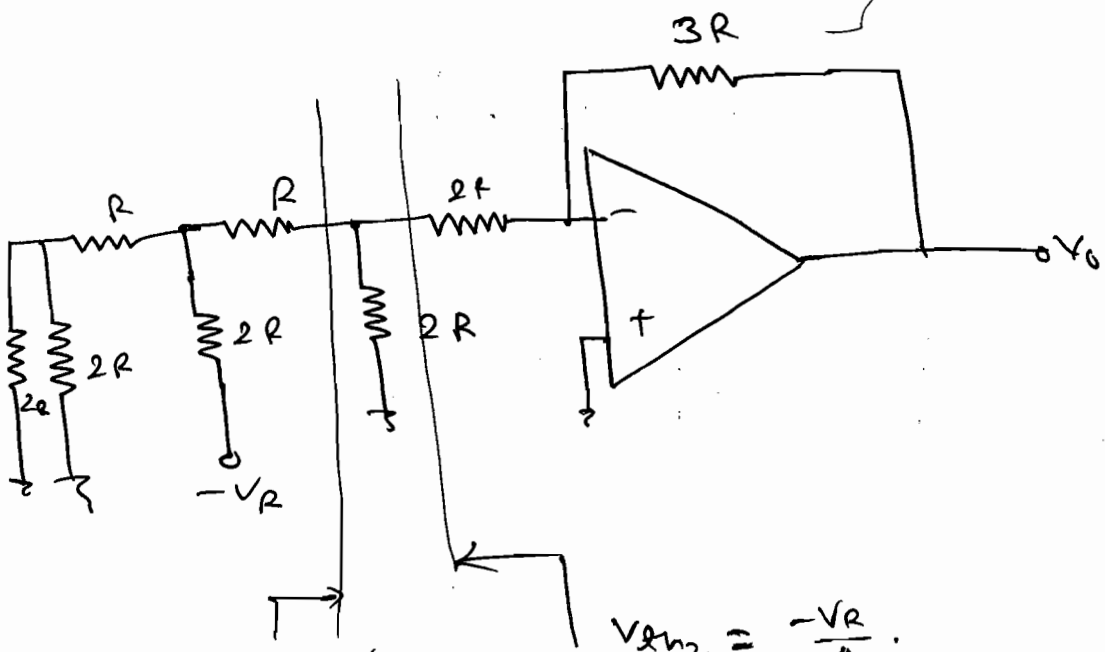② Let $a_1 = 1$, $a_2 = a_0 = 0 \rightarrow V_0 = 1$.



$V_{in1} = -\frac{V_R}{2}$
 $R_{in2} = 2R$

 $V_{in2} = -\frac{V_R}{4}$
 $R_{in2} = 2R$



$V_0 = \left(-\frac{V_R}{4}\right) \left(-\frac{3R}{3R}\right)$

$V_0 = \frac{V_R}{4}$

$V_0 = \left[\frac{C_{12} \xrightarrow{ASB}}{2} + \frac{C_1}{4} + \frac{C_0 \xrightarrow{ASB}}{8} \right] V_R$

① FSO

$V_o = FSO$ when $a_2 = a_1 = a_0 = 1$

i.e. $FSO = \left(\frac{V_R}{2} + \frac{V_R}{4} + \frac{V_R}{8} = \frac{7V_R}{8} \right)$

$= V_R - \frac{V_R}{8}$

⊗


$FSO = V_R - \text{weight of LSB.}$

∴ ② Step size = Resolution = $\frac{a_0}{8} V_R = \frac{V_R}{8}$

* Disadvantage of voltage switched Ladder DAC is: it produces unwanted spikes at the input while switching. To overcome this we use current switched DAC.

③ 3 Bit R-2R Ladder DAC (Current Switching)

⇒

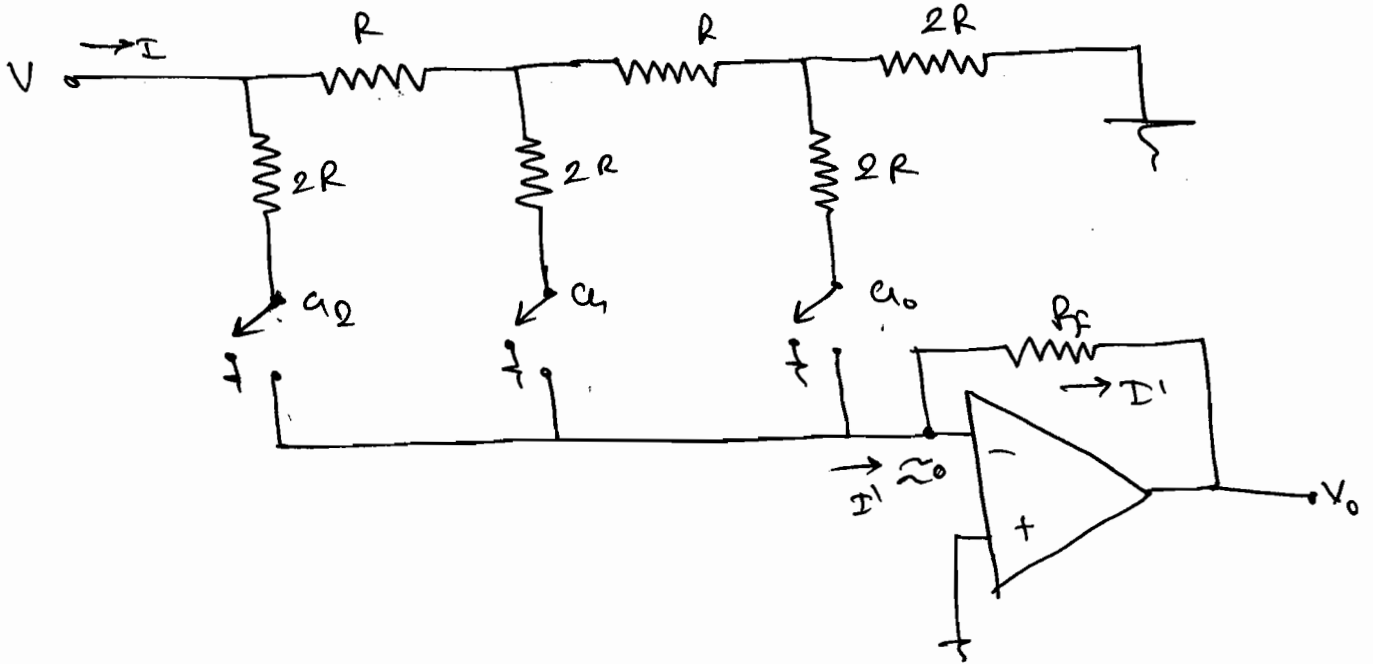

→ Duty of OP-Amp:

→ It is acting as Current to Voltage Amp.

$$\rightarrow I = \frac{V}{R_{eq}} = \frac{V}{R} \rightarrow \textcircled{1}$$

$$V_o = -I' R_f \rightarrow \textcircled{2}$$

P) Let $V = 10V$, $R = 1k\Omega$.

$2R = R_f$

Dig. 111 $a_2 a_1 a_0 = 101 \Rightarrow$ Analogue output.

$$\therefore I = \frac{V}{R} = 10mA$$


$$\therefore I' = \frac{I}{2} + \frac{I}{4} = 10 \left[\frac{1}{2} + \frac{1}{4} \right] = \frac{5 \times 10}{4} = \frac{25}{4}$$

$$\therefore V_o = -\frac{25}{4} \cdot (1)$$

$$V_o = -\frac{25}{4} V$$

$$V_o = -6.25V$$

 P=2) Determine the OP of the following Dk.45



$$A_F = \left(1 + \frac{7}{1}\right) = 8.$$

$$\therefore V_0 = A_F \left(\frac{1}{8} + \frac{1}{2}\right).$$

$$V_0 = 8 \times \frac{5}{8}$$

$$\therefore \boxed{V_0 = 5V}$$

$$\therefore \text{Contribution of } V_1 \text{ at Input} = \frac{V_R}{2} = \frac{1}{2}.$$

$$\therefore \text{Contribution of } V_2 \text{ at Input} = \frac{V_R}{8} = \frac{1}{8}.$$

$$\therefore \text{output} = \text{Input} \times \text{Gain}$$


$$= \left[\frac{1}{2} + \frac{1}{8}\right] \times 8.$$

$$= 8 \times \frac{5}{8} \times 8$$


$$\therefore \boxed{V_0 = 5V}$$

* Analog to Digital Converter:

(1) Counter Type ADC:

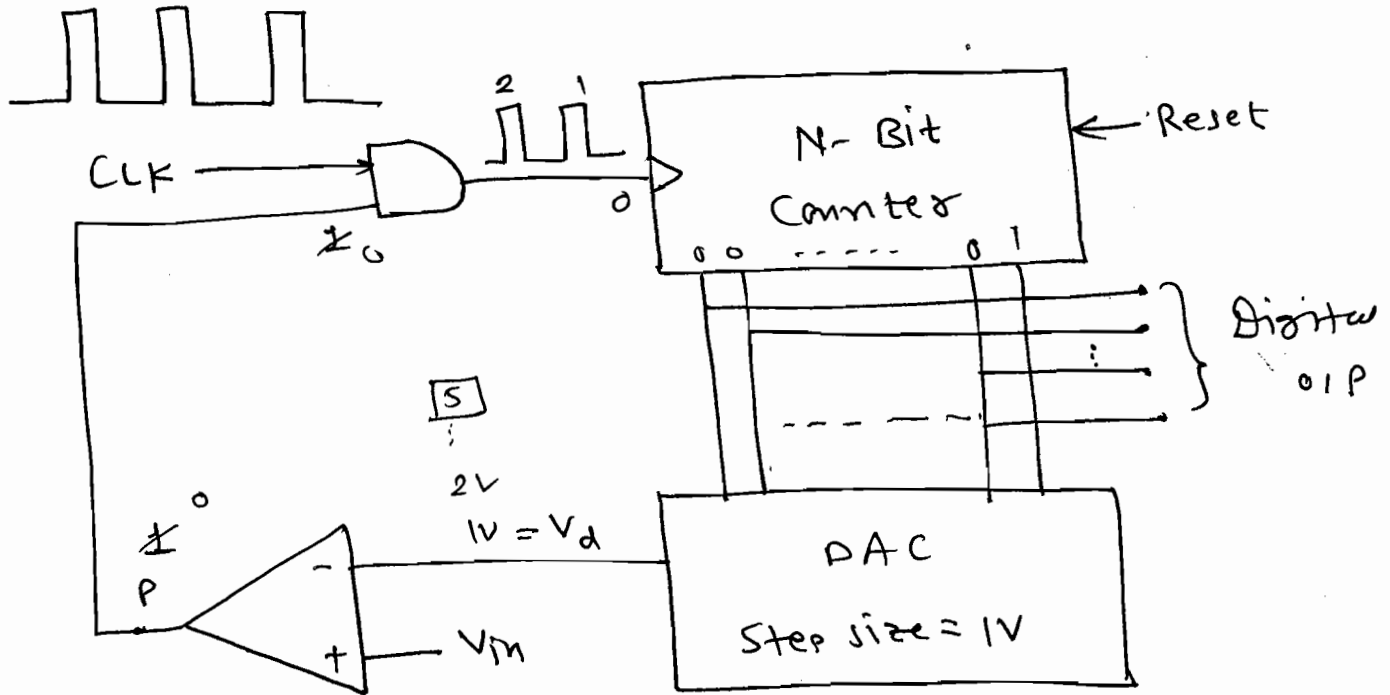

Analogue Input

 


→ Value of Counter = ceiling $\frac{\text{Input voltage}}{\text{step size}}$

* Two Features

① Conversion time depends on the input magnitude.

② Maximum Conversion time.

$$= \underline{\underline{2^N - 1}}$$

 

Sampling Period :

$$T_s \geq \text{max Conv. time.}$$


$$\text{i.e. } T_s \geq (2^N - 1) T$$

$$\text{Sampling rate } f_s = \frac{1}{T_s} = \frac{1}{(2^N - 1) T} \text{ Hz.}$$

NOTE:

→ In Counter type A/D converter the conversion time doubles for every 1 bit increase in size.

② Successive Approx ADC:

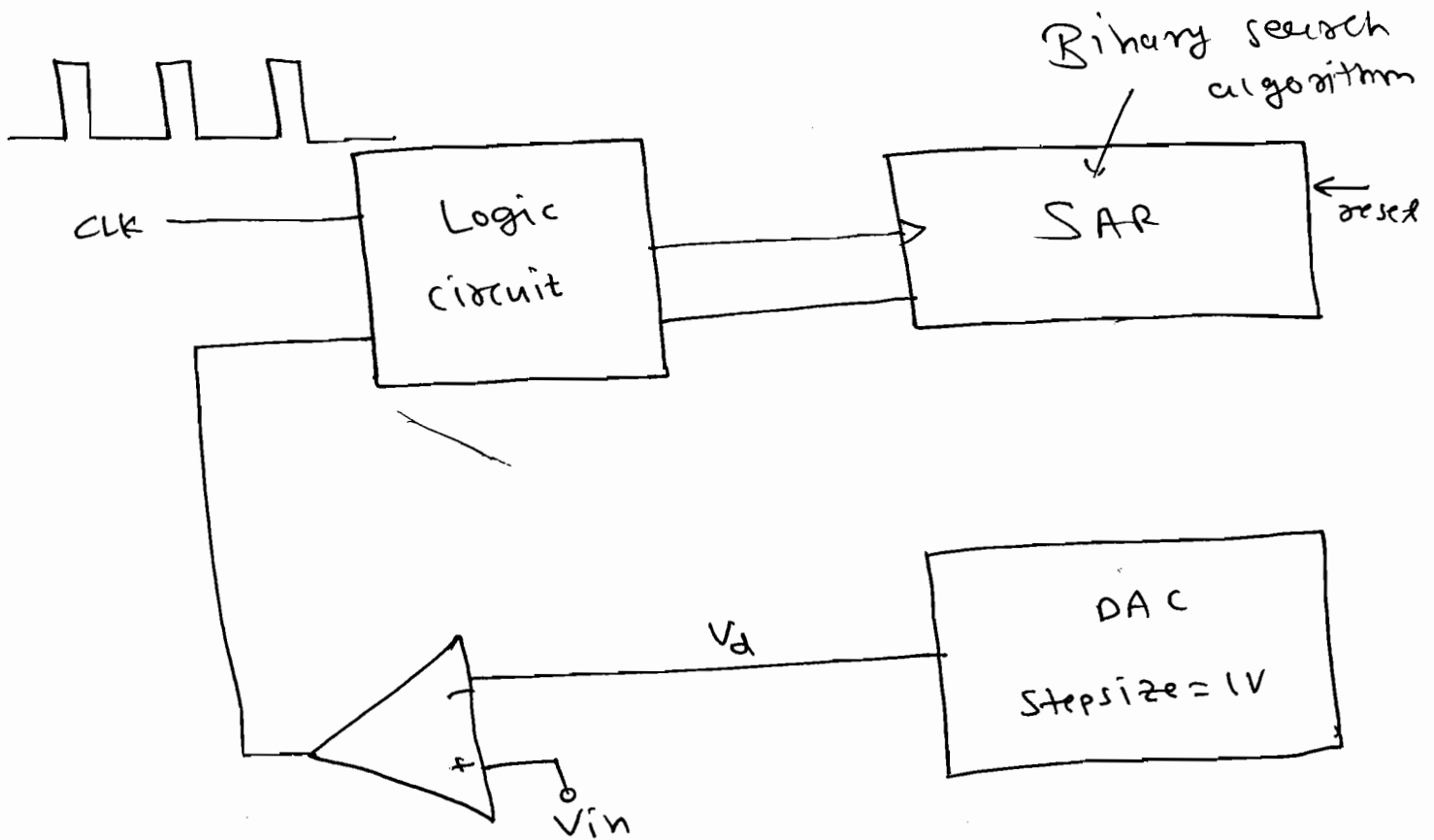

→ $V_d > V_{in} \Rightarrow V_d \downarrow \Rightarrow \text{SAR} \downarrow$.


→ $V_d < V_{in} \Rightarrow V_d \uparrow \Rightarrow \text{SAR} \uparrow$.

$V_d > V_{in} \Rightarrow p=0$.


$V_d = V_{in} \Rightarrow p=0$

$V_d < V_{in} \Rightarrow p=1$.

* 3 - BIT SAR

 

 $V_d = 4 \times 10 \times \text{Stepsize}$
 $= 4 \times 1$
 $= \boxed{4V}$



Time = 3T

→ In successive approximation A/D converter the digital output is always less than the analog input.

P) $V_{in} = 2V$ $V_d = 4V$

DAC stepsize = $1V$


Dig output = 001

→ In Successive approximation ADC,

① Conversion time doesn't depend on input magnitude.

② Maximum conversion time = NT .

③ 3-Bit Flash (parallel) ADC:

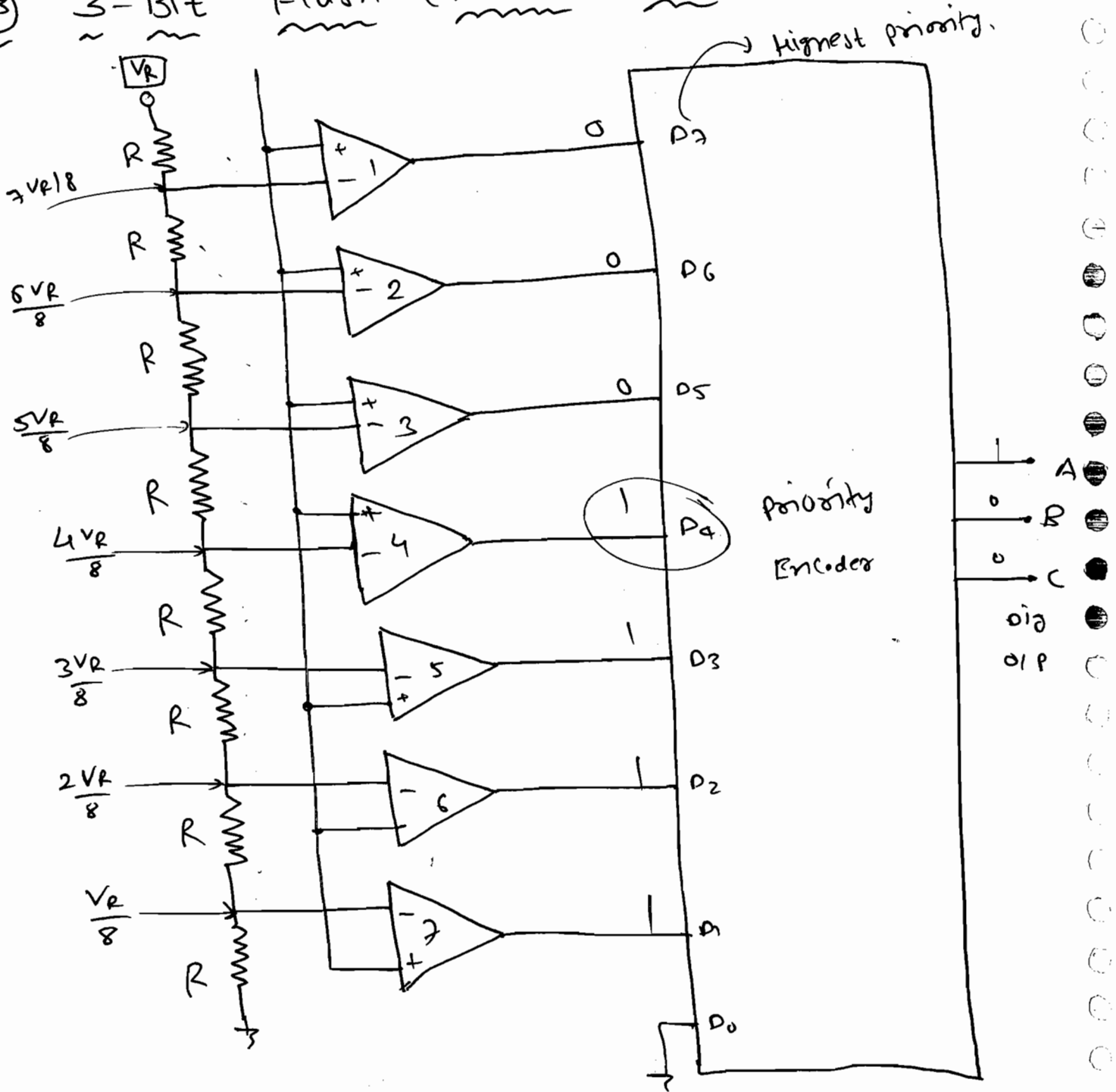

V_{in}	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	outputs		
									A	B	C
$\frac{4V_R}{8} \leq V_{in} \leq \frac{5V_R}{8}$	0	0	0	1	1	1	1	0	1	0	0
$\frac{3V_R}{8} \leq V_{in} \leq \frac{4V_R}{8}$	0	0	0	0	0	1	1	0	0	1	0

→ In flash time ADC


- ① Conversion time doesn't depend on input magnitude.
- ② Maximum conversion time is very less it decreases and hence it is the fastest ADC.

* Disadvantage

→ N-bit flash ADC requires $(2^N - 1)$ comparators.



(4) Dual Slope (or) Integrating ADC:

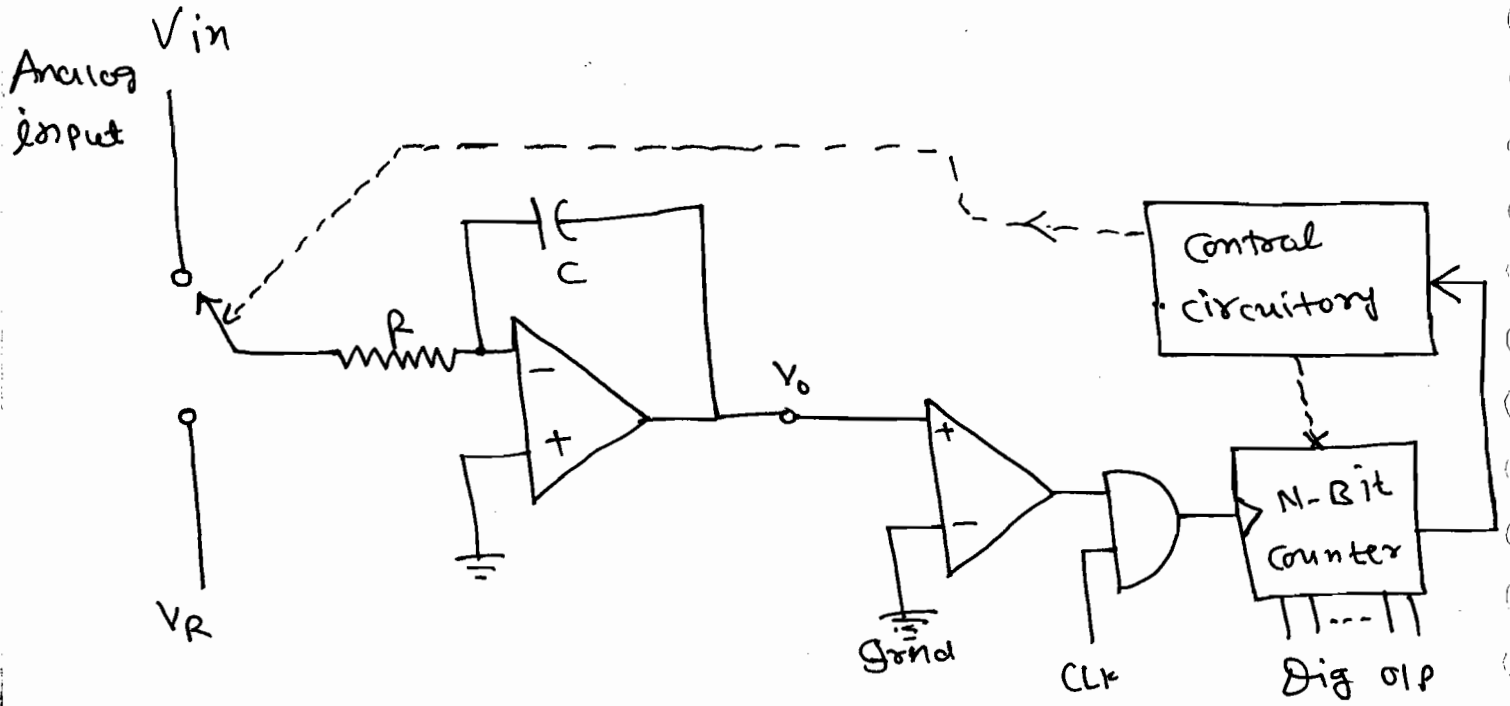

* V_{in}, V_R polarities must be opposite.

1) $V_o > 0 \Rightarrow$ CLK Pulses reach the Counter.

2) $V_o \leq 0 \Rightarrow$ Counter Stops.

2) $V_o = \frac{-1}{RC} \int v dt.$


If v is constant

$\therefore V_o = -\frac{V}{RC} \cdot t$

3) Control circuitry.

\rightarrow For fixed time " T_i " \Rightarrow $\left\{ \begin{array}{l} "S" \rightarrow V_{in} \text{ and} \\ \text{Counter is Reset} \end{array} \right.$

 (b) After " T_1 " \Rightarrow $\left\{ \begin{array}{l} "S \rightarrow V_R" \text{ cmd} \\ \text{Counter is started.} \end{array} \right.$ 53



CLOCK: $\Rightarrow T = 2 \mu s$.

$T_2(1)$: $100 \mu s$. \rightarrow Counter value: $\frac{100}{2} = 50$, 50 CP require

$T_2(2)$: $20 \mu s$. \rightarrow Counter value: $\frac{20}{2} = 10$, 20 CP require.

If clock period = $2 \mu s$.

Case-(i) Value of Counter = $\frac{100}{2} = 50 = (000 \dots 110010)_2$

Case-(ii) Value of Counter = $\frac{20}{2} = 10 = (000 \dots 1010)_2$

* Discharging time " T_2 ".

Voltage change during T_1 = Voltage change during " T_2 ".

ie. $\frac{V_{in}}{RC} \cdot T_1 = \frac{V_R}{RC} \cdot T_2$

$$* \therefore T_2 = \frac{|V_{in}| T_1}{|V_R|}$$

* Advantages:

- ① It is very accurate because the same capacitor is used for charging and discharging. So, that if any deviation exist the system will not be affected. Hence, it is used in all digital voltmeters.
- ② The integrator at the input eliminates the effect of power supply noise called as "50 Hz hum" (interference).

* Disadvantage:

→ Its speed of operation is very less.

⇒ ^{In.} Dual slope ADC,

(i) Conversion time depends on input magnitude.

(ii) Max. conversion time

$$T_{max} = T_1 + (2^N - 1) T$$

N = size of ADC
(no. of bits).

T = CP.

T_1 = fixed time.

But, $T_{1,max} = (2^N - 1) T.$


$\therefore T_{max} = (2^N - 1) T + (2^N - 1) T$

$\therefore T_{max} \approx 2^{N+1} \cdot T.$

→ In Dual Slope ADC the conversion time doubles for every 1 bit increase in size.

3) $\Sigma - \Delta$ ADC (Sigma-Delta ADC).
 ↳ 1 Bit DPCM.

Concept:

 



In $\Sigma - \Delta$ ADC

signal → LPF $\left(\frac{1}{stl} \right).$

Noise → HPF $\left(\frac{s}{stl} \right).$

* Resolution of A/D:

  → It is the minimum change required at the input to obtain 1-bit change at the output.






$$\text{Resolution} = \frac{\text{Input Voltage Range}}{(2^n - 1)}$$

* For proper ADC operation.

⇒ Ripple voltage at input < Resolution of ADC.

* Continuous signals can't be applied to the ADC. ADC can not convert continuous analog signal into digital signal directly. We require some circuitry for that. i.e. Sample and Hold CKT.

*
→

   

→ Acquisition time:

→ It is the time taken for the switch to close and capacitor charge to the input voltage.

→ Aperture time:

→ It is the time taken by the capacitor to disconnect from ip after the switch is open.

Ex-9 Page 29 CR

$$\rightarrow T_1 = 300 \text{ ms} \quad V_R = 100 \text{ mV}$$

$$T_2 = 370.2 \text{ ms}$$

$$\therefore |V_{in}| T_1 = |V_R| T_2$$

$$\therefore V_{in} = \frac{370.2}{300} \times 100 \text{ mV}$$

$$V_{in} = 123.4 \text{ mV}$$

Q-10

Hint:

In ADC,

$$\text{Quantization error} = \pm \frac{\text{Stepsize}}{2}$$

$$\text{Stepsize} = \frac{1.275}{2^{8-1}} = 5 \text{ mV.}$$

$$\therefore \text{Quantization error} = \pm \frac{5}{2} \\ = \pm 2.5 \text{ mV.}$$

Q-11

Maximum Conversion Time

$$T_{\text{max}} = 2^{N+1} \cdot T$$

$$= 2^{11} \cdot 1 \mu\text{s}$$

$$T_{\text{max}} = 2048 \mu\text{s.}$$

$$\therefore T_s \geq T_{\text{max.}}$$

$$\therefore T_s = 2048 \mu\text{s.}$$

$$\therefore f_s \leq \frac{1}{2048 \mu\text{s}}$$

$\therefore f_s \leq 500 \text{ Hz.}$

Let, $f_s = 500 \text{ Hz.}$

$\therefore \text{Input BW} = \frac{f_s}{2}$
 $= \frac{500}{2}$

$\therefore \text{BW} = 250 \text{ Hz.}$

Q-5

$F_{SO} = (2^N - 1) \times \text{Stepsize.}$

$\therefore 20 = (2^8 - 1) \times \text{Stepsize.}$

$\therefore \text{Stepsize} = \frac{20}{255} \text{ Volts.}$

$\therefore V_{in} \approx (219)_{10} \times \frac{20}{255}$

$\therefore V_{in} = 17. \text{ V}$

Q-3

8-bit ADC \rightarrow 0-5V.

0V \rightarrow 0000 0000 = 00h.
⋮

2.5V \rightarrow 1000 0000 = 80h


⋮
5V \rightarrow 1111 1111 = FFh.

R) 8-bit ADC \rightarrow -5 to +5

-5 \rightarrow 0000 0000 = 00h.

⋮
0 \rightarrow 1000 0000 = 80h

⋮
5 \rightarrow 1111 1111 = FFh.

 



MICROPROCESSORS

- 80% Instruction Set
- 10% Mem, I/O Interfacing
- 10% Miscellaneous.


→ TOPICS:

- ① Block diag. & pin diag of 8085 UP.
- ② Mem Interfacing.
- ③ I/O Interfacing.
- ④ Instruction, Machine cycles.
- ⑤ Timing Diagram.
- ⑥ Instruction set.
- ⑦ Addressing modes.

∴ 8085 μ P

① ~~16 Address~~ * Features:

① 16 Address Lines

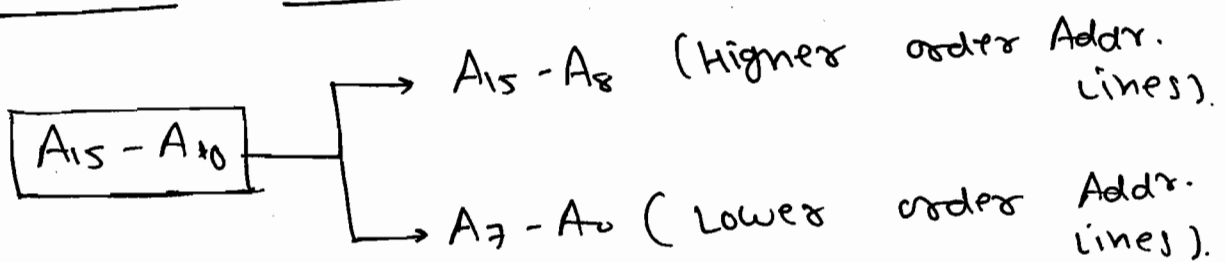

$$\text{Mem. Capacity} = 2^{16} = 2^6 \cdot 2^{10} = 2^6 \cdot 1 \text{KB}$$

$$= \boxed{64 \text{KB}}$$

② 8 Data lines:

$$= \boxed{D_7 - D_0}$$

③ Frequency of μ P.

$$f = 3.072 \text{ MHz}$$

$$\boxed{f = 3.072 \text{ MHz}} ; \text{ Clock period } T = \frac{1}{f}$$

$$\boxed{T = \frac{1}{f} = 320 \text{ ns}}$$



④ Von Neumann Architecture.

↓

X [Harvard Architecture]

→ In Von Neumann architecture Program⁶³ and data are store into the same memory.

→ In Harvard Architecture Program and data are stored in separate memories with separate Buses.

Eg: ARM microcontroller.
= Dsp processors.

⑤ CISC Processor.

CISC = Complex instruction set Computer.

↓
RISC = Reduced instruction set Computer.

e.g. (i) ARM Controller.
= (ii) Dsp processor.

⑥ NMOS Tech.

⑦ only +5V supply is used.


⑧ TTL Compatible.

⑨ 8085 μ P is a 8-bit μ P because its ALU Capacity is 8-bits.

NOTE:


4004, 8008
used +5, -5, +12
supply.

* Block Diagram of 8085 μ P.

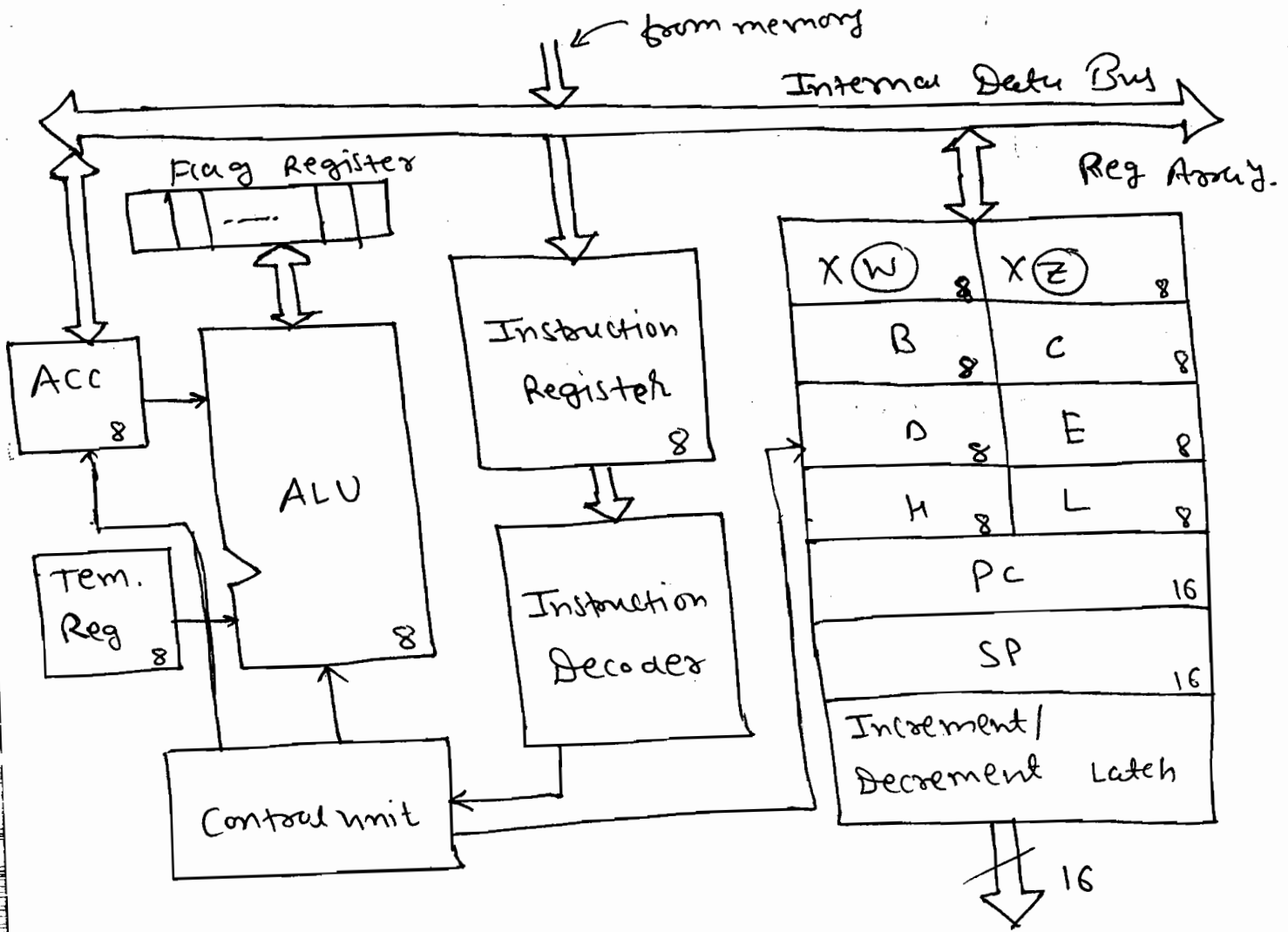


W, Z = Temp. Reg.

→ 8-bit Register (R) ⇒ (7), Reg. pairs | 16 bit Reg.
 (RP) ⇒ (3)

 

A = Acc


→ PSW₁₆ = Program Status Word₁₆

 

→ PC: Program Counter.


⇒ Program Counter contains the address of the next instruction.

 → It is called IP (Instruction pointer) in 8086 μP .



⇒ SP₁₆ = Stack Pointer₁₆

* Flag Register:

 

S: Sign flag.

Z: zero flag.

P: Parity flag.

CY: Carry flag.

① Sign flag:

→ $S=1$ if MSB of ALU Result = 1
⇒ $S=1$ if ALU Result is '-ve'.

② zero flag:

→ $Z=1$ if ALU operation Results = $00H$.

③ Parity flag:

→ $P=1$ if ALU Results has "even parity".

④ CY: Carry Flag:

→ $CY=1$ if Carry occurs during Addition (OR)
borrow occurs during Subtraction.

⑤ AC: Aux Carry:

→ $AC=1$ if Carry occurs from Lower to Upper Nibble (or)
if borrow occurs from Upper to Lower Nibble.

NOTE:

→ The programmer can not excess the Ac flag, μP uses internally for BCD addition.

E.g.

$$\begin{array}{r}
 \text{EDH} = 1110 \quad 1101_2 \\
 + \text{CBH} = \begin{array}{r} 1100 \quad 1011_2 \\ \hline 1011 \quad 1000 \end{array} \\
 \hline
 \text{S} = 1
 \end{array}$$

(Note: In the original image, there are handwritten annotations: 'y=1' and 'x=1' with arrows pointing to the 1s in the 4th bit of the first number, and 'AC=1' with an arrow pointing to the carry-out of the 4th bit.)


$AC = 1.$
 $Z = 0.$
 $P = 1$ (even Parity).
 $CY = 1.$

* As $x=1, y=1.$
 \Rightarrow No overflow

(cont)

* Two -ve nos are added.
 Result is -ve
 \Rightarrow No overflow.


* Pin Diagram of 8085 MP.

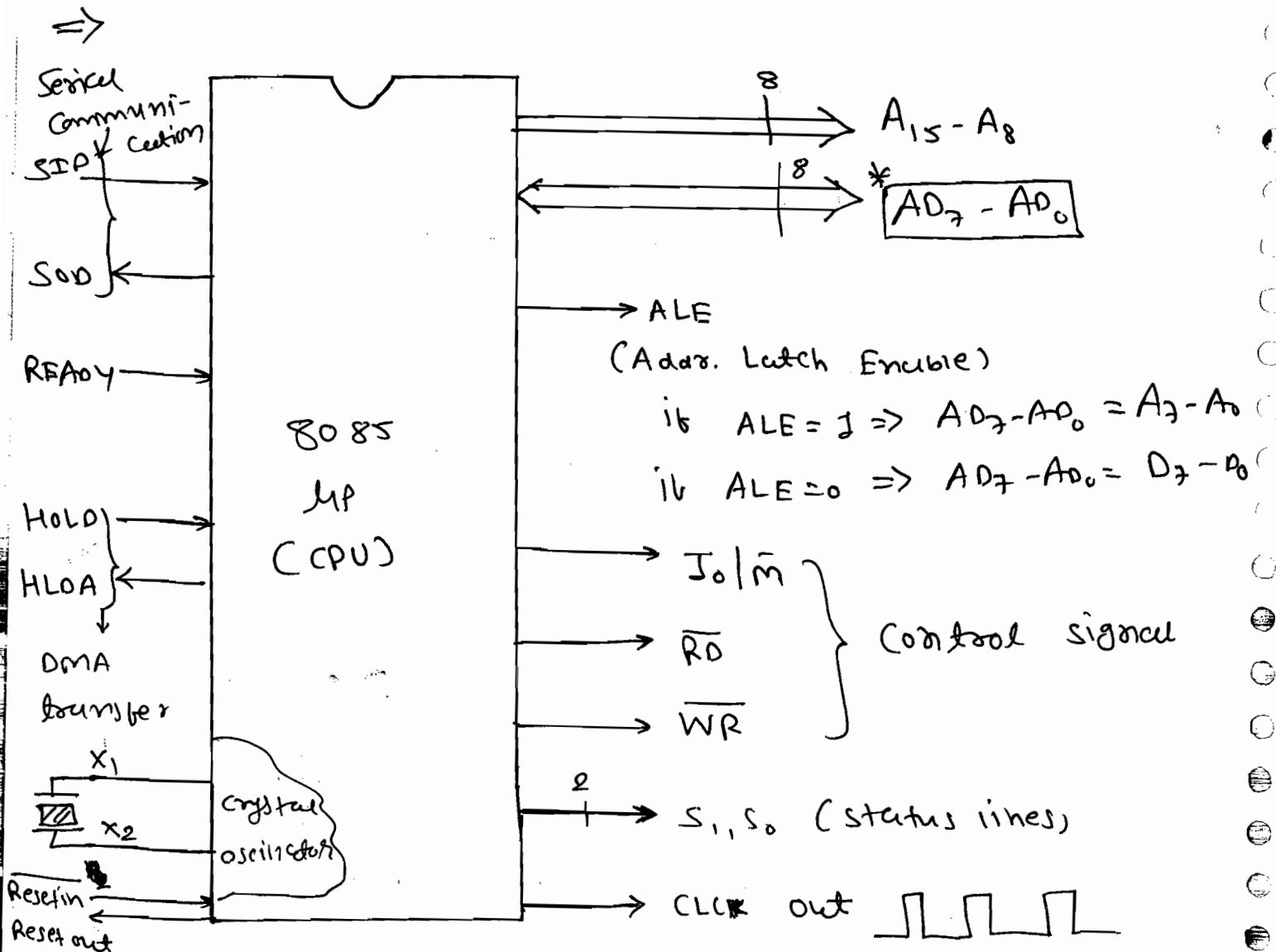

⇒

I ₀ /m	S ₁	S ₀	operation
0	1	1	opcode Fetch M/C
0	1	0	mem Read M/C
0	0	1	mem write M/C
1	1	0	PAIO Read M/C
1	0	1	IO write M/C
↑	1	1	Interrupt ACK M/C

⇒ Multiplexing:

 


* READY

- 1 Normal
- 0 WAIT State

→ Ready pin is used to synchronised the MP with slow speed peripherals and memories.


Eg.

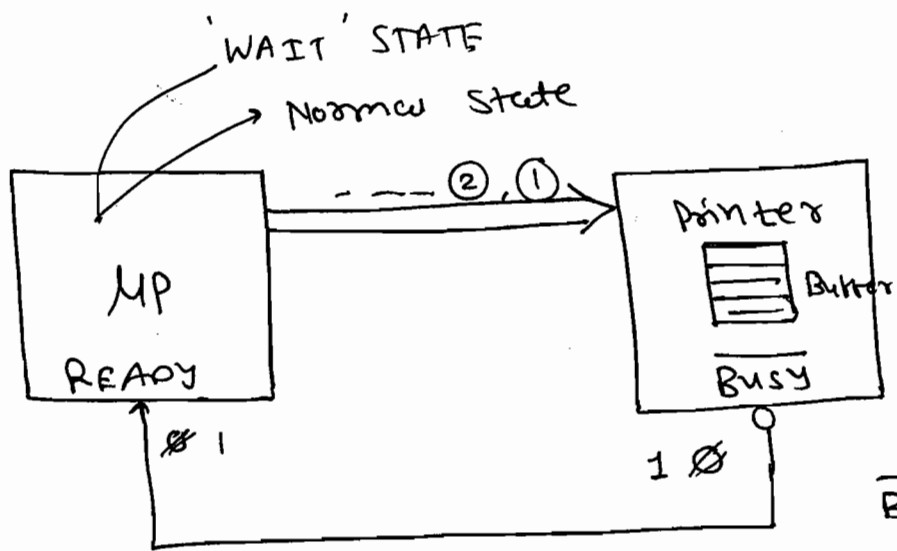

$\overline{BUSY} = 0$ printing over.
 $= 1$ over.

* HOLD and HLOA:

e.g.

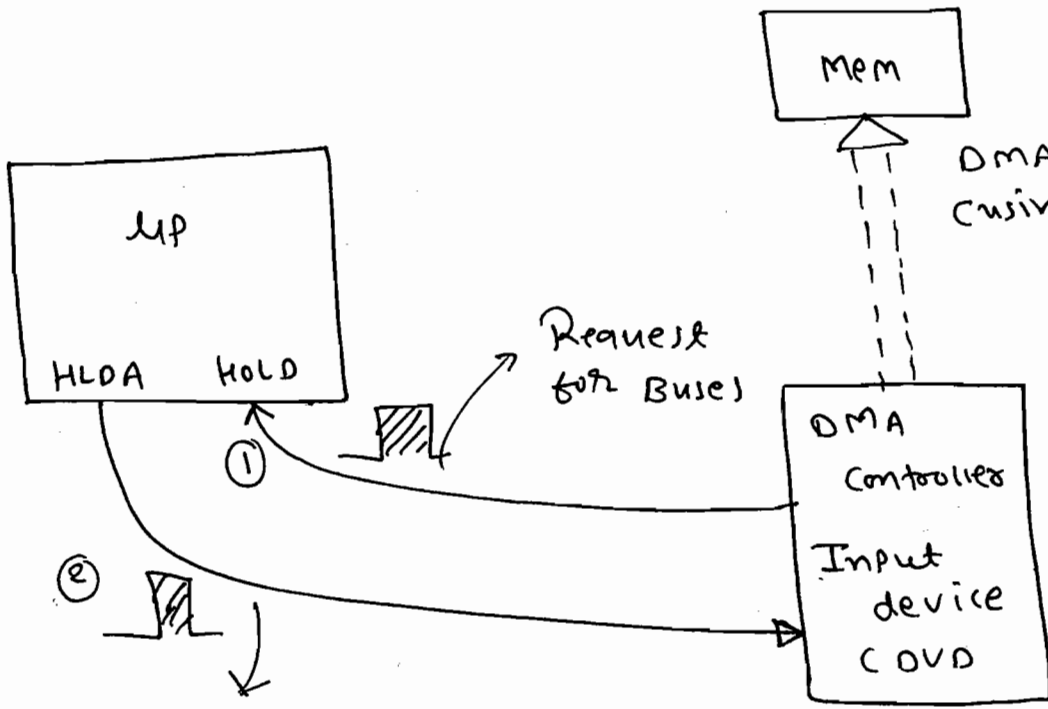

Buses are given to DMA Controller.

DMA = Direct Memory access.

→ In DMA transfer up acquires the Buses from DMA Controller when the HOLD pin becomes Low

→ Two Modes of operation:

① Burst mode:

→ In this mode the Buses are handed over to the microprocessor only after the entire data transferred to memory.

② Cycle Stealing:

→ In this mode the Control of the Buses switches back and forth betⁿ MP and DMA Controller.

* X_1 & X_2 :



$$f = 3.072 \text{ MHz.}$$

$$f_{\text{crystal}} = 2 \times f_{\text{MP}} \\ = 2 \times 3.072 \text{ MHz}$$


$$f_{\text{crystal}} = 6.144 \text{ MHz}$$

→ The crystal freq. is divided by two to convert single phase clock into a two phase clock because 2 phase MOSFET Shift Registers are faster than single phase

MOSFET Shift Register.


* Reset in & Reset out.

⇒ Power on Reset

 


→ When MP is reset

 
- (i) All the Registers are clear including PC.
- (ii) All the Buses enter into high impedance state.
- (iii) MP Processor fetches its next instruction from memory location 0000H.



* CLK out:

 

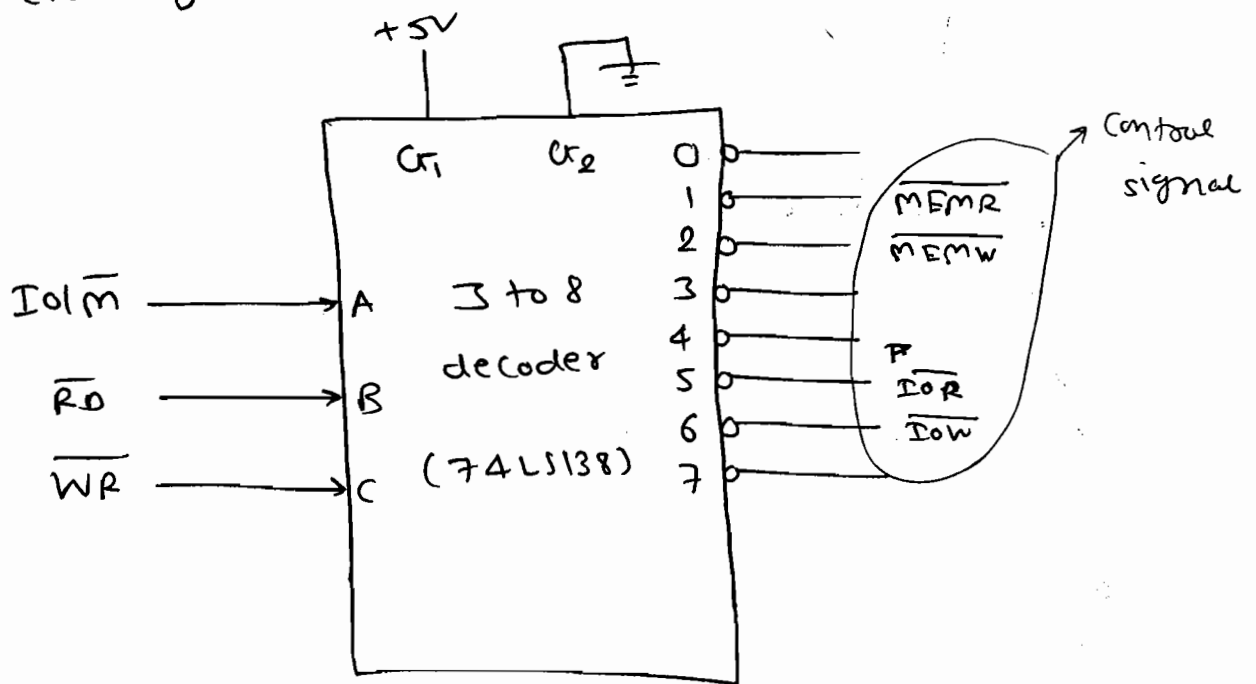
Ex: In the following decoder, determine the number of valid outputs and their functions



Ans:

I_o/\bar{m}	\bar{R}_D	\bar{W}_R	Outputs
0	0	0	0 → Invalid
0	0	1	1 → \overline{MEMR}
0	1	0	2 → \overline{MEMW}
0	1	1	3 → Invalid
1	0	0	4 → Invalid
1	0	1	5 → \overline{IOR}
1	1	0	6 → \overline{IOW}
1	1	1	7 → Invalid.

* Demultiplexing of $AD_7 - AD_0$.

 

MP

① Address = $4250h$.



② Data = $F7h$.

* Latch is enable, when Address is sent on $AD_7 - AD_0$

* Latch is disable, when data is sent on $AD_7 - AD_0$


→ The disadvantages of multiplexing is it reduces the MP speed of operation because of the time taken in demultiplexing.

* Hardware Interrupts.

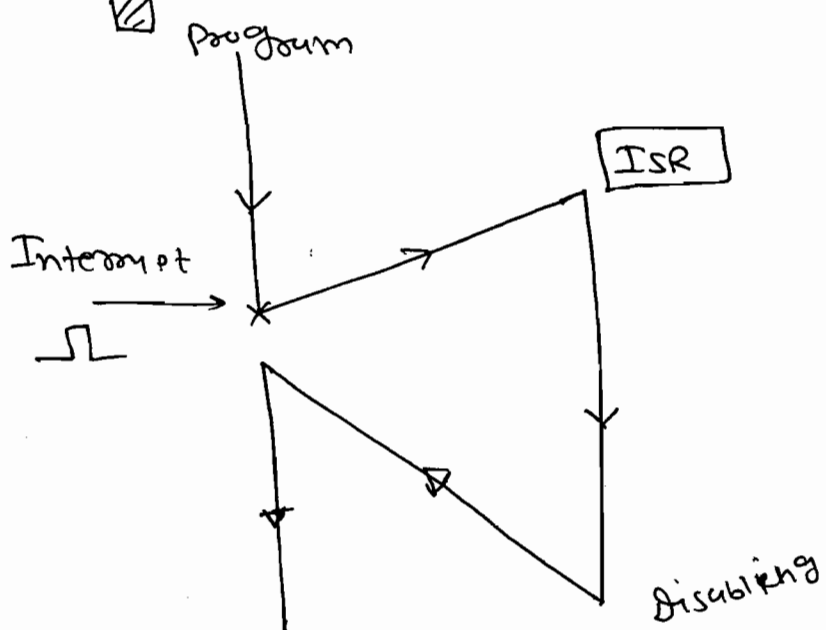 

	Priority	Vector Address	Masking	Types of triggering
TRAP (RST 4.5)	Highest	0024H	(NMI)	Positive edge + level
RST 7.5	003CH	} Maskable	Positive edge
RST 6.5		0034H		Level
RST 5.5		002CH		
INTR	Least	(NVI)		

* Memory IC's:

 

1 KB memory = 1024 x 8
 = $2^{10} \times 2^3$
IP O/P

→ if S.A = 3800 then E.A. = $\begin{matrix} 3800 \\ + 03FF \\ \hline 3BFF_H \end{matrix}$

→ if E.A. = FFFF then S.A. = $\begin{matrix} FFFF_H \\ - 03FF_H \\ \hline FC00_H \end{matrix}$

Ex-1 Determine the starting address of 2764 memory IC if its ending address is AA5FH.

Ans:

NOTE:

	MEM IC	RAM
←	$2^7 \frac{16}{8} = 2KB$	← $6 \frac{16}{8}$
	$2^7 \frac{32}{8} = 4KB$	← $6 \frac{32}{8}$
	$2^7 \frac{64}{8} = 8KB$	← $6 \frac{64}{8}$
	$2^7 \frac{128}{8} = 16KB$	← $6 \frac{128}{8}$

→ Memory size 8KB

$$= 2^3 \times 2^{10} \times 8$$

$$= 2^{13} \times 8.$$

13 → Address lines.


∴ AA5FH.

E.A. = 0001 1111 1111 1111
1FFF

$$\begin{array}{r} \therefore \text{S.A.} = \text{AA5FH} \\ - \text{1FFFH} \\ \hline \text{8A60H} \end{array}$$

Ex 2 Determine the size of the memory whose starting and ending address are 3A00H & 79FFH respectively.

Ans:

 


Hence, Memory size
 $= 2^{14} \times 8 = 2^4 \times 2^{10} \times 8 = 16 \times 1KB = 16KB.$

* Memory Expansion:

* Construct a 4KB memory by using 1KB Memory ICs


~~1KB~~ ~~1KB~~ ~~1KB~~

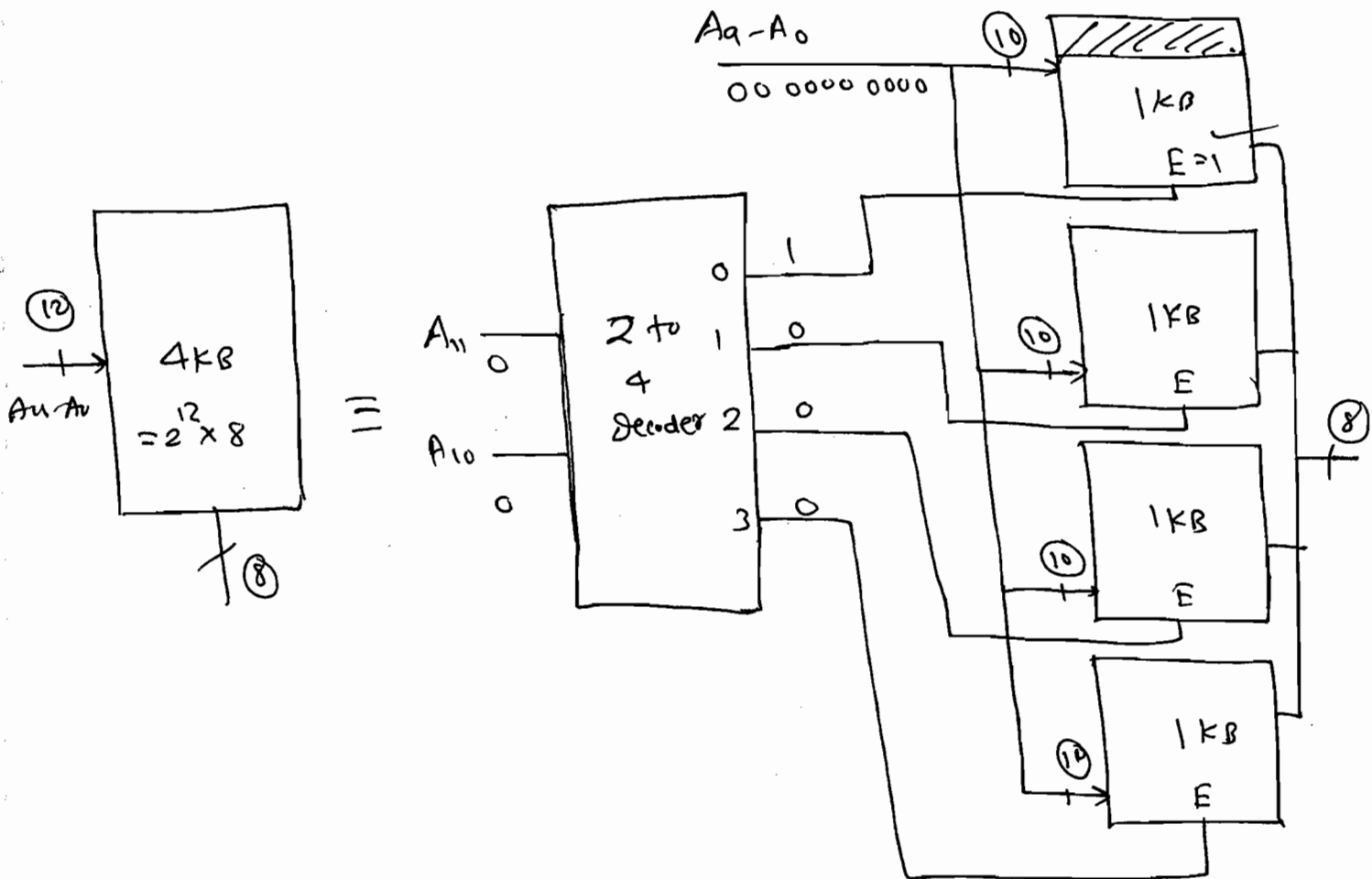

* Construct a 1KB memory using 1024×8 Mem IC's \rightarrow 1KB Mem. = 1024×8 .

P) Construct a 1KB memory using 1024×4 IC's.


→ 1KB mem = 1024×8 .

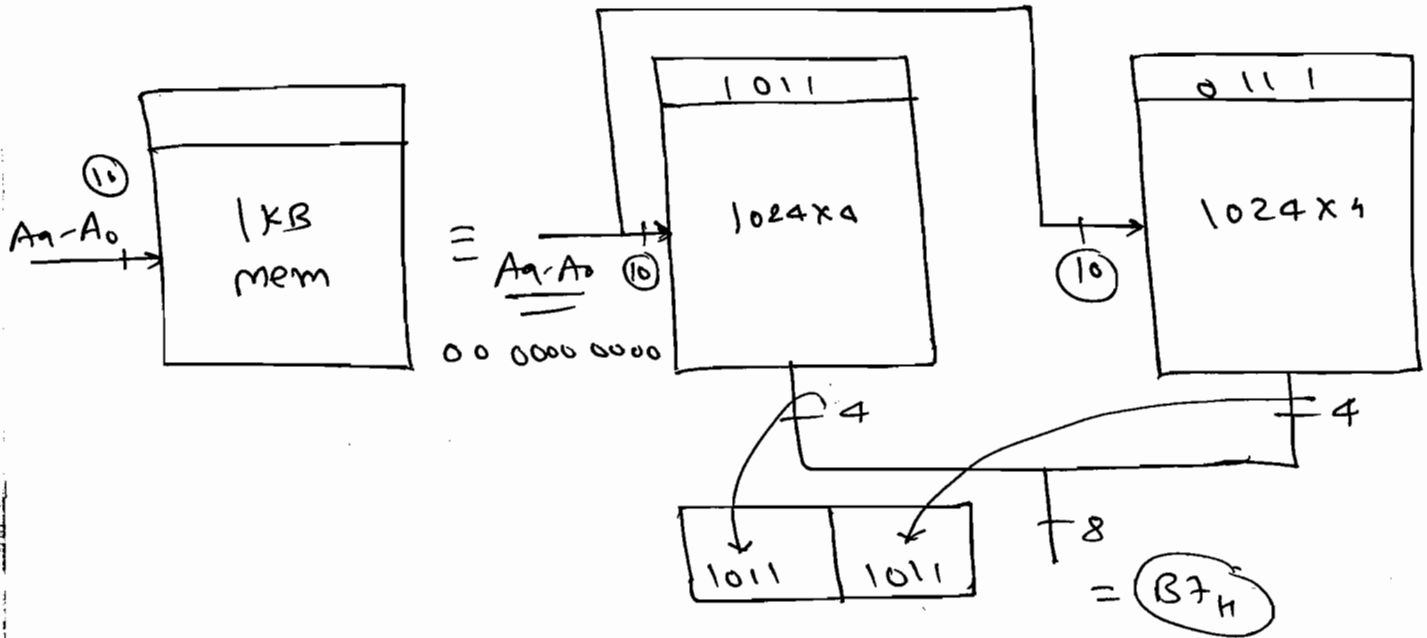

P) How many 256×4 memory IC's are require to construct a 32KB memory.

Ans: No. of mem ICs = $\frac{\text{Required size of mem}}{\text{Given size of mem.}}$
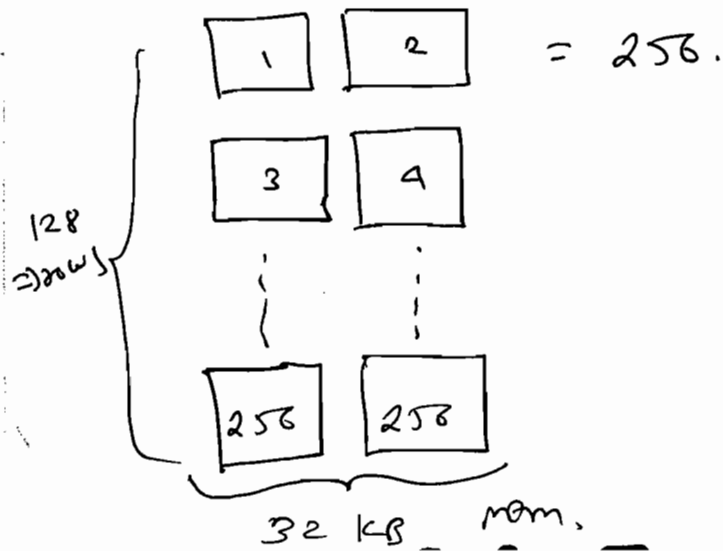
$$= \frac{32 \times 1024 \times 8}{256 \times 4}$$



Ex-2 A digital computer has 20 address lines and 24 data lines. How many memory ICs having 16 address lines and 8 data lines are required to feed the memory of the computer?

Ans:


$$\text{No. of mem ICs} = \frac{\text{Required size of mem}}{\text{Given size of mem.}}$$

$$= \frac{2^{20} \times 24}{2^{16} \times 8}$$

$$= 16 \times 3$$

$$= 48.$$



→ 16 rows, 3 columns.

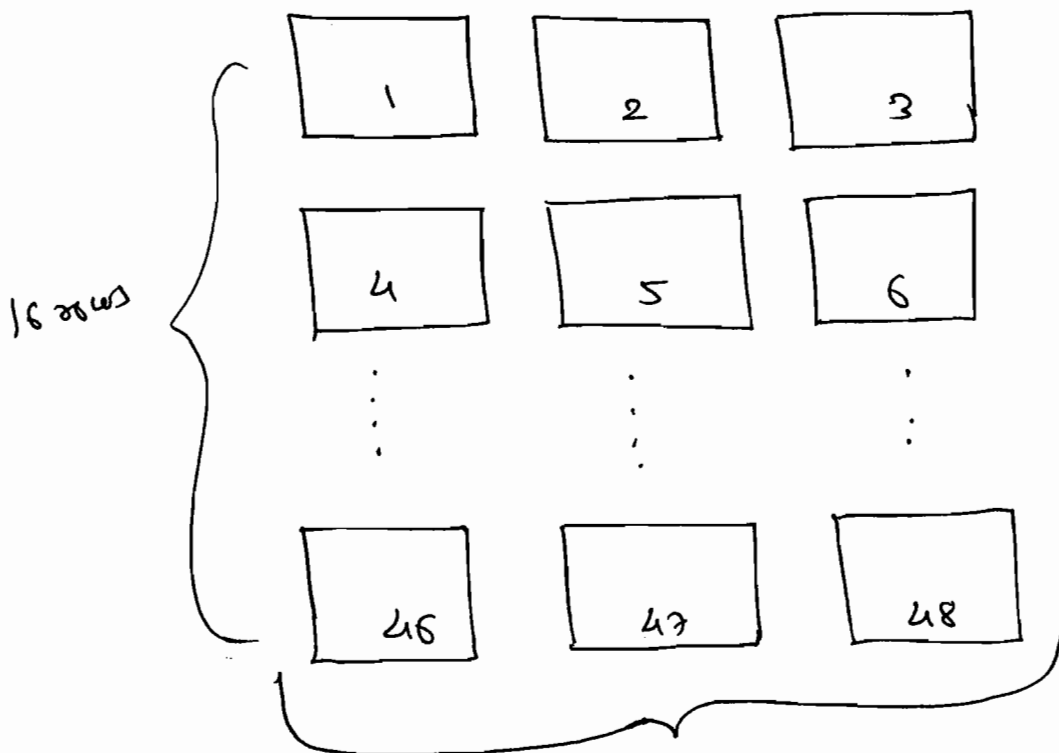


$$2^{20} \times 24 = \text{memory.}$$


* Memory Mapping:

 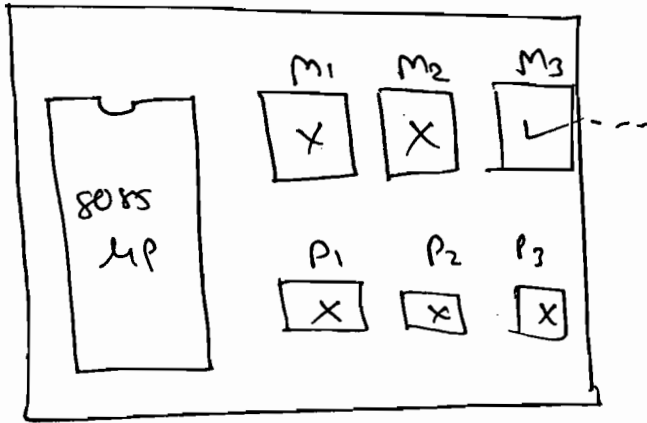→ It is the process of assigning address range to all the memory ICs in a microcomputer.



 Ex 1 In a micro computer a 1KB memory IC is interface with the MP as shown in the following figure: Determine the address range of the memory IC



 


Addr. Range: $D400_H - D7FF_H$.


→ In the above interfacing as all 16 addr. lines are utilized it is called absolute decoding which results in one to one mapping.

Ex-2 A 8kB memory IC is interface to the microprocessor as shown in the figure. Determine the address range of the memory IC.

Ans:

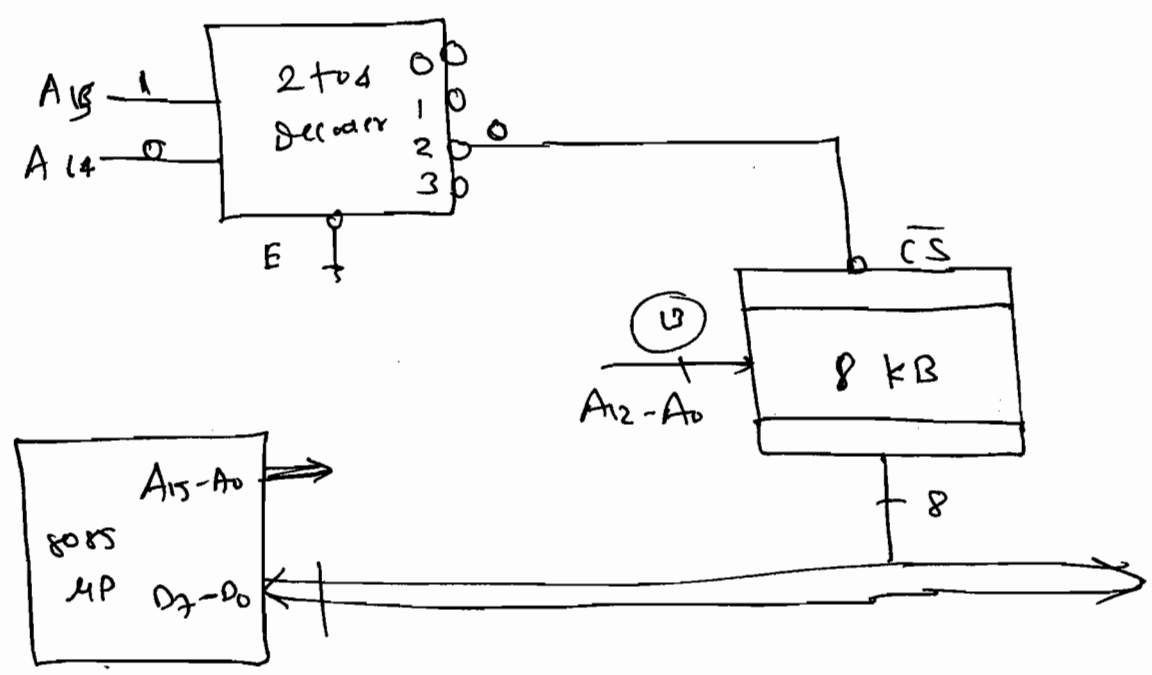

 
* A_{13} address line is unused.
 ~~A_{15}~~



* "A₁₃" addr line is unused
 => Partial Decoding => many to one mapping.

NOTE: In partial decoding if n address line are unused into results $\frac{n}{2}$ foldback memories.

 Ex 1: Which of the following indicate the address of the memory IC shown below:




→ mem is selected only when

$$A_{15}A_{14}A_{13}A_{12} = 1101 = D_{16}H.$$

 - (a) B200H - B3FFH
- (b) F800H - FAFFH
- ✓ (c) DA00H - DBFFH
- (d) 8900H - 8AFFH

Ex 2. Which of the following doesn't indicate the address of the memory IC shown below: 512 Byte mem.




S.A. = $A_{15} - A_{10}$ A_9 A_8 $A_7 \dots A_0$
 0 1 0 000 0000.
 E.A. = 1 0 0000 0000

→ Starting Add. must have $A_9=0, A_8=1$.
 → Ending Add. must have $A_9=1, A_8=0$.

- | | | A_{15} | A_{14} | A_{13} | A_{12} | A_{11} | A_{10} | |
|-----|--------------------------------|-------------|----------|----------|----------|----------|----------|---------|
| (a) | $3100_H - 32FF_H \Rightarrow$ | $3100_H =$ | 0 | 0 | 1 | 0 | 0000 | Valid |
| | | $32FF_H =$ | 0 | 0 | 1 | 0 | 0000 | |
| (b) | $8D00_H - 8E FF_H \Rightarrow$ | $8D00_H =$ | 1 | 1 | 0 | 1 | | valid |
| | | $8E FF_H =$ | 1 | 1 | 1 | 0 | | |
| (c) | $F400_H - F5 FF_H \Rightarrow$ | $F400_H =$ | 0 | 1 | 0 | 0 | | Invalid |
| | | $F5 FF_H =$ | 0 | 1 | 0 | 1 | | |
| (d) | $C900_H - CA FF_H \Rightarrow$ | $C900_H =$ | 1 | 0 | 0 | 1 | | valid. |
| | | $CA FF_H =$ | 1 | 0 | 1 | 0 | | |

★ I/O Interfacing:

① Memory mapped I/O \Rightarrow I/O devices are treated as Memory.

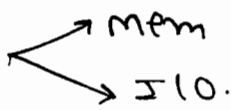② I/O mapped I/O \Rightarrow 


	mem mapped I/O		I/O mapped I/O	
	mem	I/O	mem	I/O
① No. of Addr lines	16	16	16	8 (A ₇ -A ₀)
② Control signals	\overline{MEMR} , \overline{MEMW}	\overline{MEMR} , \overline{MEMW}	\overline{MEMR} , \overline{MEMW}	\overline{IOR} , \overline{IOW}
③ No. of peripherals	* (i) — (ii) 60 KB	64 KB 4 KB	64 KB +	$2^8 = 256$ I/O devices

*

	mem mapped I/O	I/O mapped I/O.
<u>Advantages</u>	1) I/O \overline{M} pin is not required. 2) No separate inst ⁿ for I/O devices. 3) Arithmetic and Logic operations are directly performed on I/O device data.	1) Max capacity of μP is utilized. 2) Less hardware complexity for I/O interfacing.
<u>Disadvantages:</u>	1) more hardware complexity for I/O device interfacing 2) Effective memory space is reduced.	(1) Separate inst ⁿ for I/O device are required. (2) Can't perform Arith, Logical operations directly on I/O data.

Ex-1 A Peripheral is interfaced to the 8085 MP as shown in the following figure.

 Determine (i) The mode of interfacing
 (ii) No. of internal Registers in the peripheral and their addresses.



Ans: 1) I/O mapped I/O Mode
 (∵ only 8 addr lines used and control signal is \overline{IOW}).

(2) A₅, A₂, A₁, A₀ are connected directly to the peripheral, no. of internal Registers

$= 2^3 = \boxed{8}$


~~A₇ A₆ A₅ A₄ A₃ A₂ A₁ A₀~~

	A								X=0	X=1
	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀		
R ₀	0	0	1	1	X	0	0	0	B0h	B8h
R ₁	1	0	1	1	X	0	0	1	B1h	B9h
⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮
R ₇	1	0	1	1	X	1	1	1	B7h	Bfh

→ Address range: B0h - Bfh.

⇒ In IO mapped IO mode the value on higher order address mode A₁₅-A₈ is same as the value on lower order add. Bus. (A₇-A₀).

 Ex ⇒ Determine the max. addr. of Register B in the following peripheral:




Given ⇒

A ₁	A ₀	Register
0	0	A
0	1	B
1	0	C
1	1	D

Ans: memory mapped IO.

→ For Register B.

 

→ Max Add. for Reg. 'B' is when all x's = 1.

1111 1111 1111 1101.
 = (FFFF) H.


(1) Instruction cycle:

→ It is the time required to execute an instruction

→ Range: 1 nsec to 5 nsec.

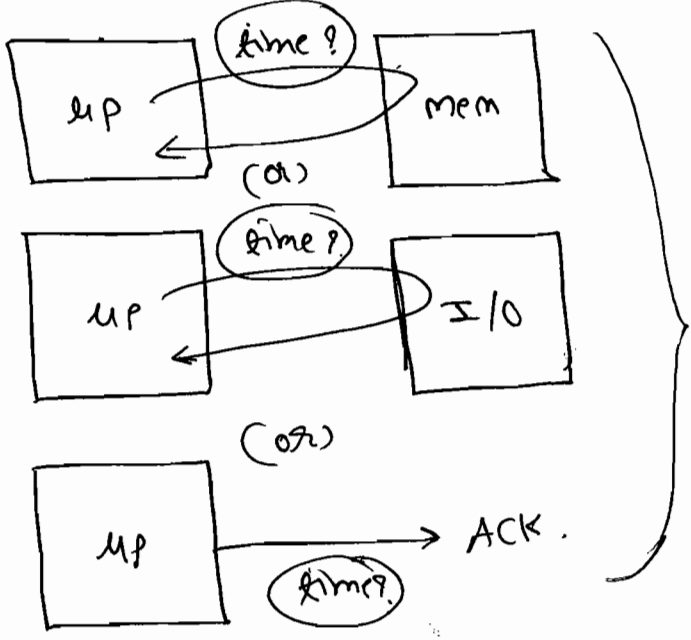(2) Machine cycle:


→ It is the time required to complete one operation of accessing memory, accessing I/O device or sending an acknowledgment.



3T to 6T state.


③ T state:

 → It is the task performed in one clock period.



* Types of Machine cycle:

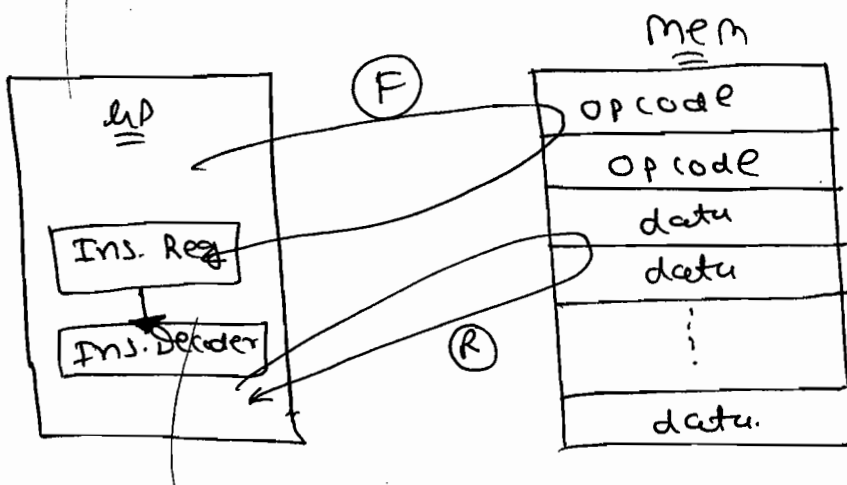
- 1) opcode fetch MIC (F) ⇒ $4T = 3T + 1T$
 - 2) mem. Read MIC (R)
 - 3) mem. Write MIC (W)
 - 4) I/O Read MIC (I)
 - 5) I/O Write MIC (O)
 - 6) Int. ACK MIC
 - 7) Hold ACK MIC
- Time to decode the opcode.



⇒ Special MIC:


- ① S = opcode Fetch MIC (6T)
- ② B = Bus Idle MIC (3T)

*

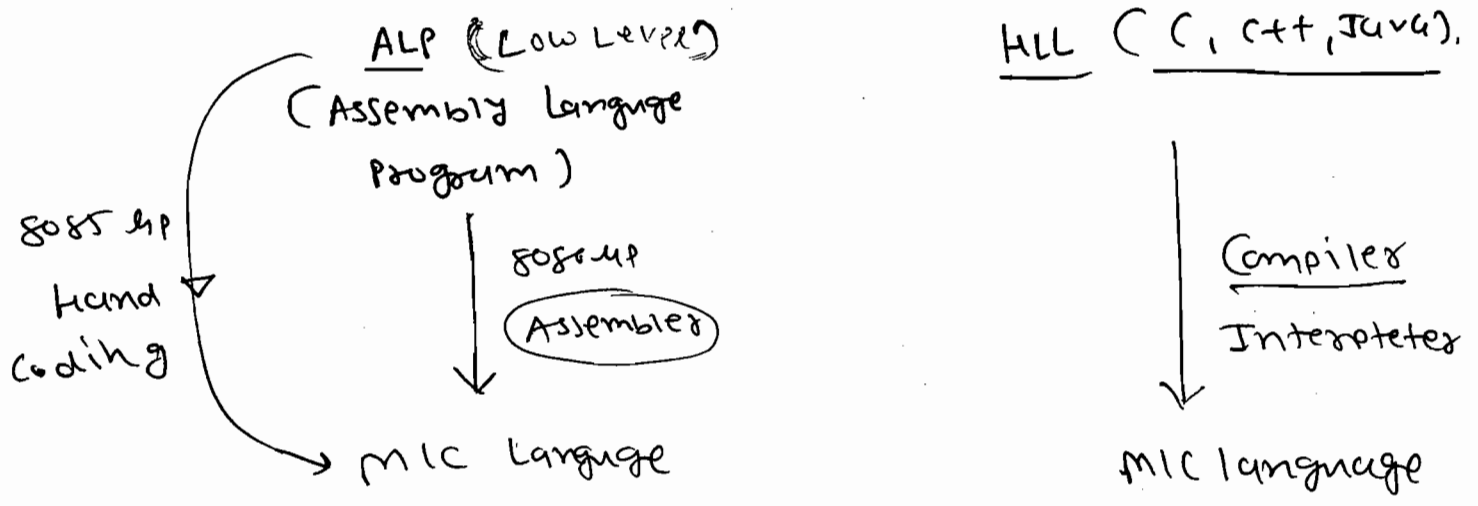


Eg:

 (1) MOV C, A ⇒ Ass. lang instruction.
(mnemonic).




(2) Opcode = 0100 1111₂
= 4Fh.

(3) MEM

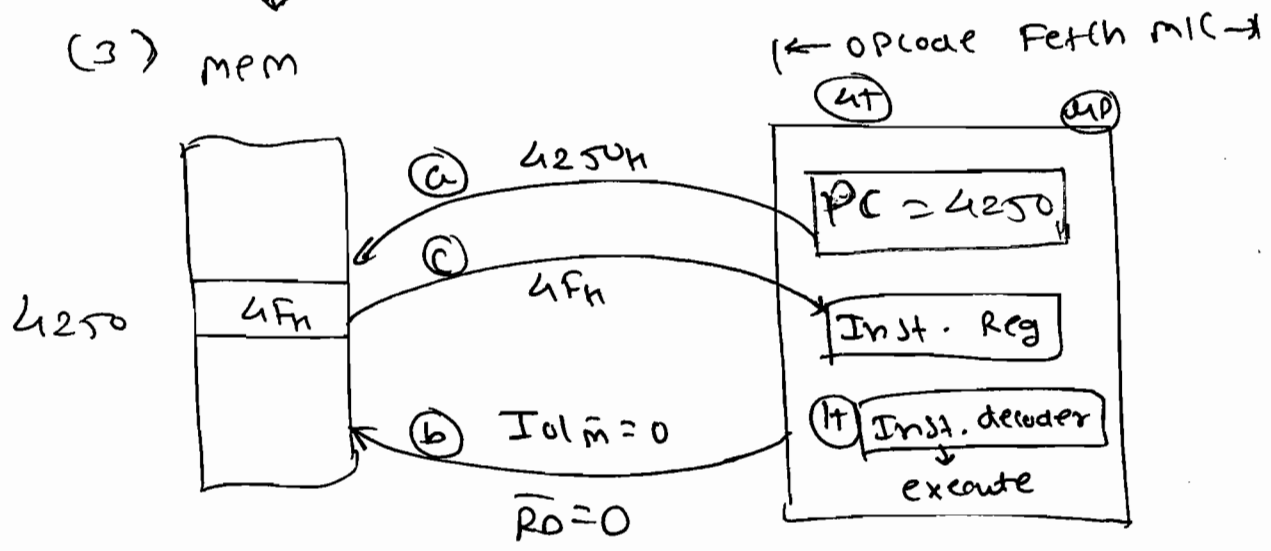

* Timing Diagram of Opcode / Fetch mic:

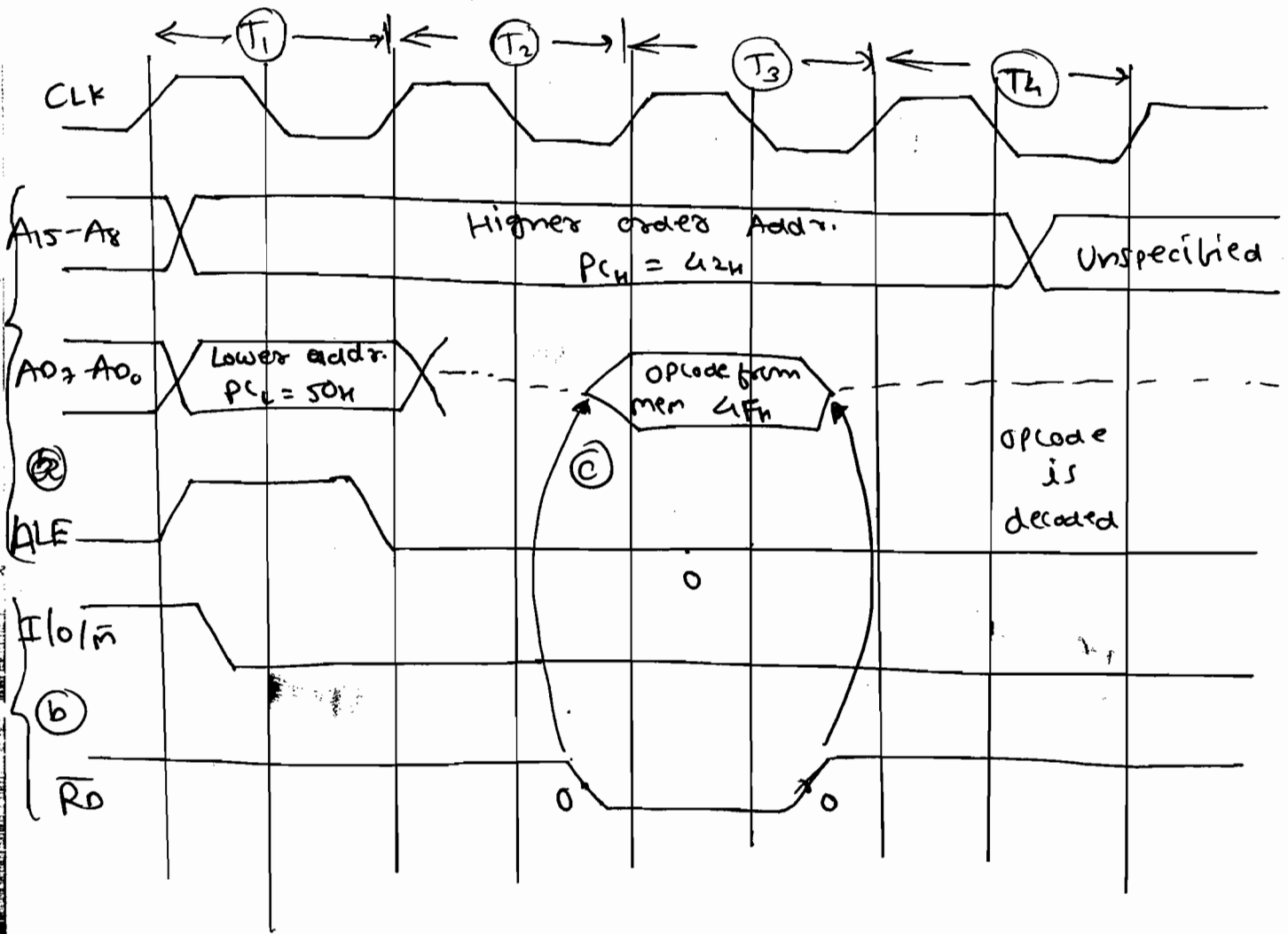

→ $PC_{16} = PC_H + PC_L = 4250h$

→ In T₂ state of any machine cycle the PC is incremented


NOTE: In the opcode fetch machine cycle it (T₄) state is removed then it converts into the timing diagram of memory read MIC cycle.

* Types of Instructions (Based on size):

- ① 1-Byte Instructions.
- ② 2-Byte Instructions.
- ③ 3-Byte Instructions.


⇒ ① 1-Byte Instruction:

e.g. MOV C, A

 


⇒ ② 2-Byte Instruction:

⇒ MVI C, 32 ⇒
 Opcode = XX

 

③ 3-Byte Instruction:


e.g. LDA 9250
 Opcode: XY

 

→ In Any instruction cycle the first machine cycle is opcode fetch machine cycle.

- Ex.
- ① XRI 46H \Rightarrow 2B
 - ② Push PSW \Rightarrow 1B.
 - ③ LOAX B \Rightarrow 1B.
 - ④ LHLD 8000H \Rightarrow 3B.
 - ⑤ DAD SP \Rightarrow 1B.

* Stack:

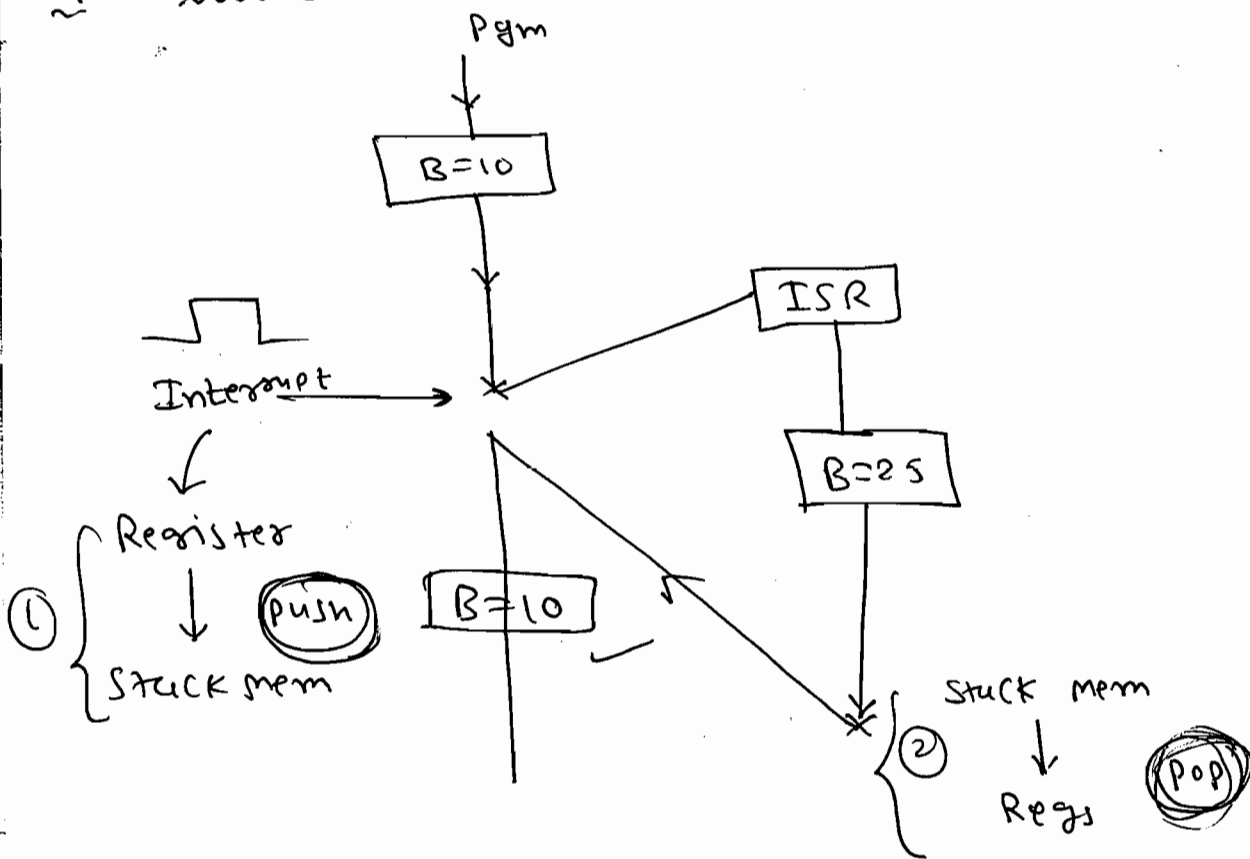

⇒ SP₁₆ = Stack Pointer₁₆;

∴ LIFO = Last in First out.

① Push RP

- Push B
- Push D
- Push H
- Push PSW

Predecrement


⇒ decrement SP + push \mathcal{R}_H
 ⇒ decrement SP + push \mathcal{R}_L

$$\mathcal{R}_{PI6} = \mathcal{R}_H + \mathcal{R}_L$$

Eg. Given SP = FFFF_H; BC = 1040_H; HL = A2C4_H.

- ① push B ② push H.

- Ans: ① push B.
 ② push H

 



P1) SP = 0000H.

- ① push B.

BC, regs → mem location = ?

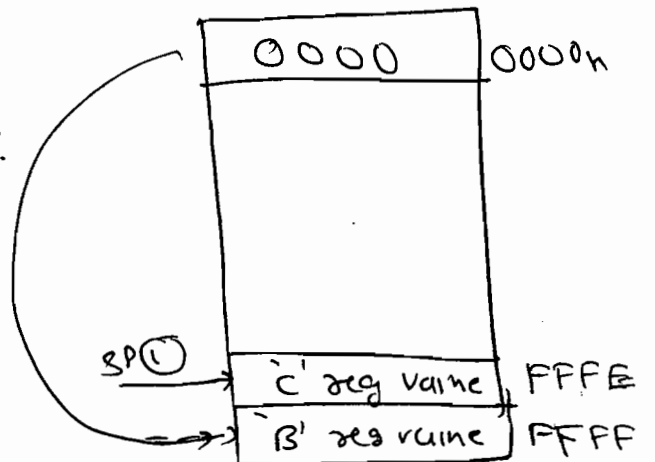
$$\begin{array}{r} 0000 \\ - \quad 1 \\ \hline FFFF \\ - \quad 1 \\ \hline FFFE \end{array}$$



 

POP B \Rightarrow get 1 Byte from stack into R_L
 POP D \Rightarrow get 1 Byte from stack into R_L
 POP H \Rightarrow get 1 Byte from stack into R_L
 POP PSW \Rightarrow get 1 Byte from stack into R_{PH}
 + Increment SP.

Ex. Given

 

- ① POP D
- ② POP PSW


DE = ?

PSW = ?

DE = 2211_H

PSW = 4433_H

 P2) Let SP = FFFF ; BC = 5065_H ; HL = A1F4_H




HL \rightarrow DE \Rightarrow DE = A1F4_H

BC \rightarrow PSW \Rightarrow PSW = 5065_H

* Types of Instructions:

- 1) Arithmetic
- 2) Logical
- 3) Data Transfer
- 4) Branching
- 5) Machine related, I/O.
- 6) Additional.

* Reference:

 

$$(4250) = 11H.$$

$$(4253) = 44H$$

$$(BC)$$

↓


$$(4250) = 11H.$$

$$M = ((HL)) = 33H.$$

① Arithmetic Instruction:


Sr. NO.	Instruction	operation	B m T	Flags affected
1)	ADD R	$A+R \rightarrow A$	1 1 4 (F)	All

 E.g. 1) ADD B \Rightarrow (2) opcode = XY




2)	ADD M	$A+M \rightarrow A$	2 R 7 (F,R)	All
----	--------------	---------------------	-------------	-----

 E.g. 1) ADD M \Rightarrow (2) opcode = XY.



3) ADI 8 bit data $A + 8\text{bit data} \rightarrow A$ 2|2|7(F,R) All 97

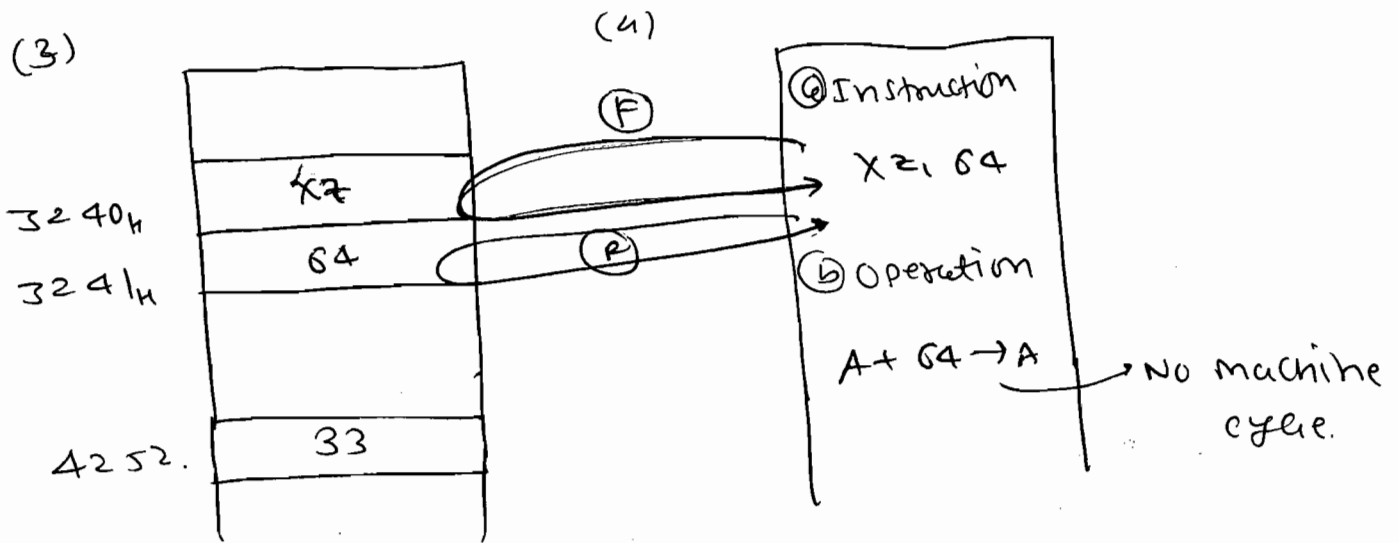Eg. (1) ADI 64H \Rightarrow (2) Opcode = XZ, 64H.



2) (1) SUB R $A - R \rightarrow A$ 1|2|7(F,R) All.
 (2) SUB M $A - M \rightarrow A$
 (3) SUBI 8 bit data $A - 8\text{bit data} \rightarrow A$

3) (1) ADC R $A + R + CY \rightarrow A$ 1|1|4(CF) All.
 ADC M $A + M + CY \rightarrow A$ 1|2|7(F,R).
 ACI 8 bit data $A + 8\text{bit data} + CY \rightarrow A$ 2|2|7(F,R).

4) SBB R $A - R - CY \rightarrow A$ 1|2|7(F,R) All.
 SBB M $A - M - CY \rightarrow A$
 SBI 8 bit data $A - 8\text{bit data} - CY \rightarrow A$


5) INR R $R + 1 \rightarrow R$ 1|2|4(CF)
 INR M $M + 1 \rightarrow M$ 1|3|10T (CF, RW).
 DCR R $R - 1 \rightarrow R$ 1|1|4.
 DCR M $M - 1 \rightarrow M$ 1|3|10.

S, Z, P, AC affected. but CY not affected.

1) INR M 2) opcode = 72.

3) Memory.

4)

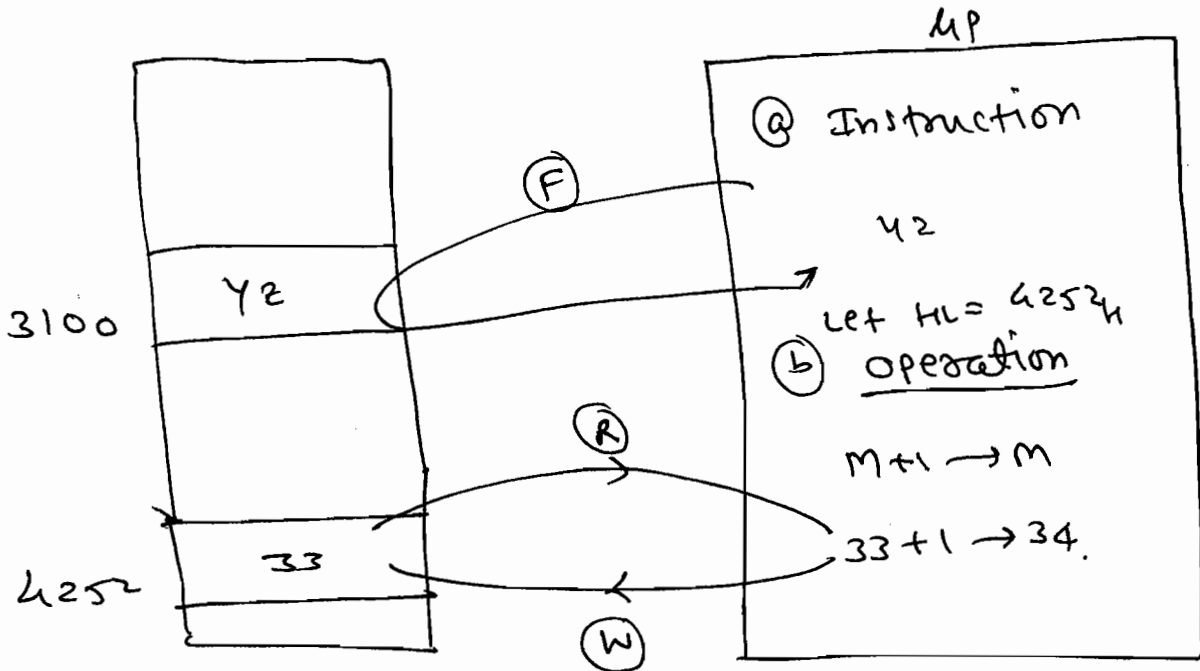

5) INX R_p

$R_p + 1 \rightarrow R_p$

DCX R_p

$R_p - 1 \rightarrow R_p$

1/1/0 (S) ✓
 2/2/0 (S) ✓

No flags are affected


[∵ operation doesn't take place in ALU].

- INX B
- INX D
- INX H
- INX SP

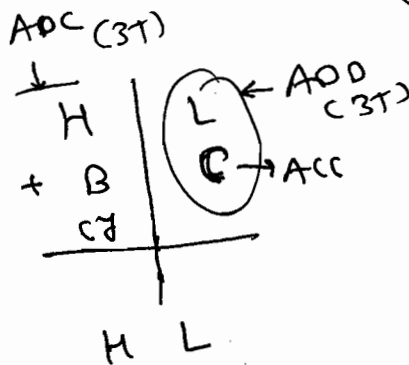7) DAD R_p

$HL + R_p \rightarrow HL$ 1/3/10 (FBB) ✓

* only carry flag if carry occurs out of 16 bits.



- DAD B
- DAD D
- DAD H
- DAD SP

Q Logical operations:

→ Sr. No.	Instruction	operation	B M T	Flags affected.
1)	a) ORA R	$A \vee R \rightarrow A$	2 1 4	* $CY=0$ S, Z, P are affected.
	ORA M	$A \vee M \rightarrow A$	1 2 7 (FR)	
	ORI 8 bit data	$A \vee 8\text{bit data} \rightarrow A$	2 2 7 (FR)	
b)	XRA R	$A \oplus R \rightarrow A$	2 1 4	
	XRA M	$A \oplus M \rightarrow A$	1 2 7 (FR)	
	XRI 8 bit data	$A \oplus 8\text{bit data} \rightarrow A$	2 2 7 (FR)	
c)	ANA R	$A \wedge R \rightarrow A$	2 1 4	
	ANA M	$A \wedge M \rightarrow A$	1 2 7 (FR)	
	ANI 8 bit data	$A \wedge 8\text{bit data} \rightarrow A$	2 2 7 (FR)	

2) ~~CMP R~~

CMP R

$A - R$ 2|1|4

$A < R \Rightarrow CY=1, Z=0$
 $A = R \Rightarrow CY=0, Z=1$
 $A > R \Rightarrow CY=0, Z=0$

* Register values are unchanged.
only flags are affected.

S, P, AC are affected.

CMP M	A-M	2 2 7	$A < M \Rightarrow CY=1, Z=0$ $A = M \Rightarrow CY=0, Z=1$ $A > M \Rightarrow CY=0, Z=0$
-------	-----	-------	---

CPI 8 bit data

A - 8 bit data


1 | 2 | 3

$A < 8\text{-bit} \Rightarrow CY=1, Z=0$
data -

$A = 8\text{-bit} \Rightarrow CY=0, Z=1$
data



$A > 8\text{-bit} \Rightarrow CY=0, Z=0$
data

3) RAL
(with CY)

 


only carry flag is affected.

RLC
(without carry)

  

1 | 2 | 4 ✓


4) RAR
with carry

 

only

'CY' flag is affected.

RRC
without carry.

 

2 | 3 | 4

4) CMA $\bar{A} \rightarrow A$ 1|1|4 No flags are affected (∵ operation is within Acc.).
 ✓ CMC $\overline{CY} \rightarrow CY$ 1|1|4 } only 'cy' flag.
 ✓ STC $CY = 1$

Ex-1
 Let, $A = F2H$.
 $CY = 1$.


XRA A $\Rightarrow A \oplus A \rightarrow A$.
 $F2H \oplus F2 \rightarrow 00H$.

Ans $A = 00H$
 $CY = 0$.

Ex-2 Let $A = 08H$

1) RLC

3) RLC

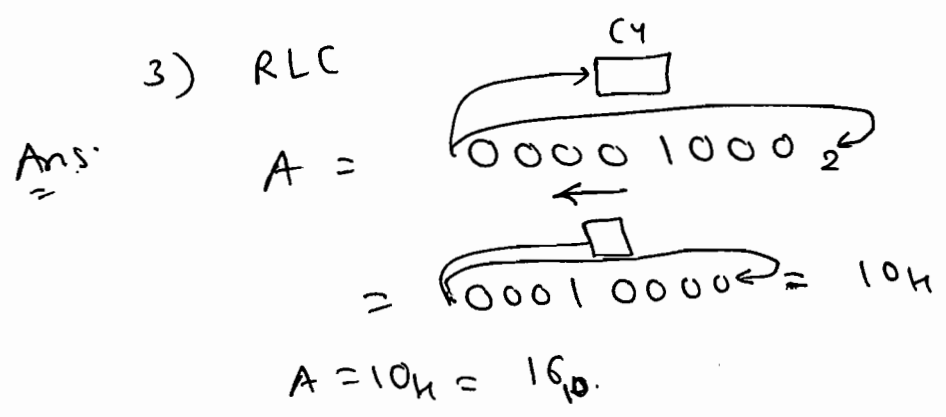

$A = 00100000 = 20H$.

Ex-3 Let, $A = 3CH$. ; All flags are cleared.
 CPI 7F. $S = ?$ $CY = ?$
 $A = ?$ $Z = ?$ $AC = ?$
 $P = ?$

Ans:

CPI 7FH.

$$\begin{aligned} \therefore & \rightarrow A - 7F. \\ & = 3C_H - 7F_H. \\ & = +bd_H. \end{aligned}$$

$$\begin{array}{r} 12 \\ 21C \\ 3C \\ - 7F \\ \hline B0H \\ = 10111101 \end{array}$$

$\therefore A = 3C_H.$

$$\begin{aligned} S &= 1 \\ Z &= 0 \\ P &= 1 \\ CY &= 1 \\ AC &= 1 \end{aligned}$$

Ex-4

→ In a MP XOR (P, Q) is defined as $P \oplus Q \Rightarrow P$

What is the fn of the following program.

XOR (r2, r1) → $r_2 = r_2 \oplus r_1$

XOR (r1, r2) → $r_1 = r_1 \oplus r_2 \Rightarrow r_1 = r_1 \oplus r_2 \oplus r_1 = 0 \oplus r_2 = r_2$

XOR (r2, r1) → $r_2 = r_2 \oplus r_1$

$r_2 = r_2 \oplus r_1 \oplus r_1$

$r_2 = 0 \oplus r_1$



$r_2 = r_1$

Ans:

Swap.
 $r_2 \leftrightarrow r_1$


3 Data transfer Instruction:

Sr. No.	Instruction	Operation	B/M/T.
1	Mov R _d , R _s	R _s ^{copy} → R _d	1 1 4.
	MOV R, M	M → R	1 2 7 (FR)
	MOV M, R	R → M	1 2 7 (FR).
	MVI R, 8 bit data	8 bit data → R	2 2 7 (FR)
	MVI M, 8 bit data	8 bit data → M	2 3 10 (FRW).
	LXI R _p , 16 bit data	16 bit data → R _p	3 3 10 (FRW).

 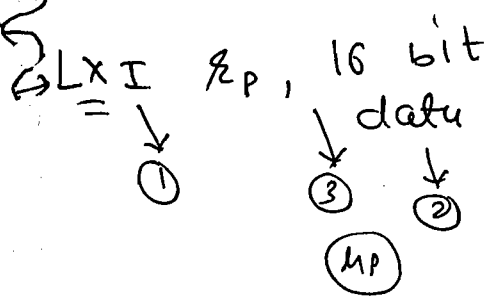

3 | 4 | 13.
(F.R.R.R.)

 - 1) LOA 4020
- 2) Opcode = X4, 20, 40.
- 3) Memory
- 4)



	Address
M1	PC = 3100h
M2	PC = 3101h
M3	PC = 3102h
M4	PC = 4020h

2) STA 16 bit address

A → (16 bit address)
→ ④ write

3 | 4 | 13.
(F.R.R.W)

3) LDAX Rp ((Rp)) → A.

1 | 2 | 7T
(F.R.)

e.g. LOAX B

((BC)) → A.

(4250) → A.


11 → A

1) LOAX B

2) opcode = Pz.

3) Memory

4) Rp

 

→ LDAX B.

~~LOAX D.~~

~~LOAX H~~


⇒ ((HL)) → A.

⇒ i.e. M → A = MOV A, M.

⇒ STAX Rp



A → ((Rp))

1 | 2 | 7T (FW)

 


E.g.
LHLD 4251

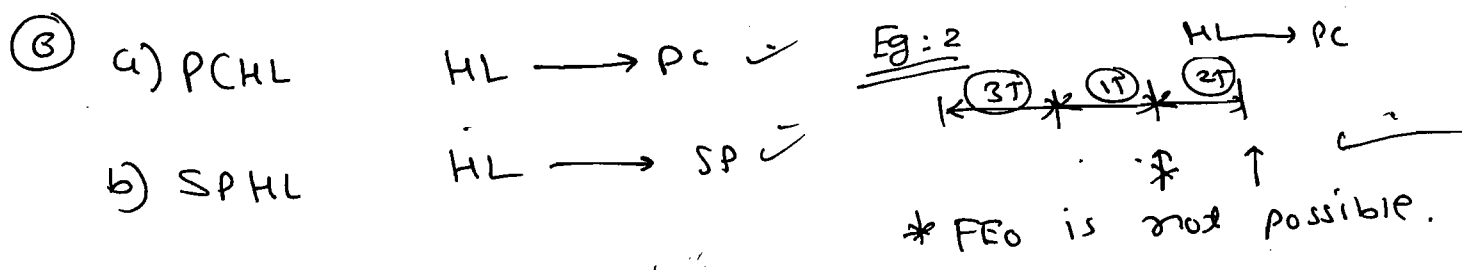 (4251) → L i.e. L=27.
 (4251+1 = 4252) → H i.e. H=33.




 NOTE → In 8085 μP opcode fetch machine cycle is extended by two T-states if the PC (or) SP value is changing. This results in the following example.



* INX \mathcal{R}_p ✓

INX SP ✓

 


7) XTHL
 (F) → (1)

Top of the Stack ↔ HL


1 | 5 | 16 ✓

E.g. ⇒

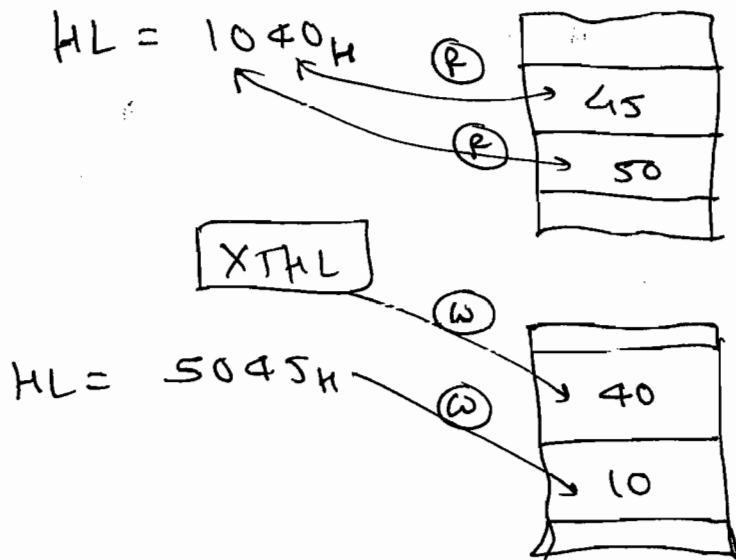

a) Push \mathcal{R}_p .

Pre-decrement

 


1 | 3 | 12

(SWW
6 3 3)

b) Pop \mathcal{R}_p

Post-increment

 

1 | 3 | 10

(FRR
4 3 3)

Eg: Let, $(F250)_H = 4B_H$
 $(F251)_H = 50_H$
 $(F252)_H = F2_H$
 $(FF53)_H = 04_H$

① LXI, H, F250. \rightarrow HL = F250 i.e. M = 4BH.
 INX H. \rightarrow HL = F251 i.e. M = 50H.
 DCR M \rightarrow M = 4FH.
 MOV C, M. \rightarrow C \rightarrow 4FH. \Rightarrow M $\xrightarrow{\text{Copied}}$ C

C = ?

\therefore $C = 4FH$

$(F251) \rightarrow L$ i.e. $L = 50$ $H = F2_H$
 $(F252) \rightarrow H$ i.e. $H = F2_H$ $\& H = F250_H$
 i.e. M = 4BH.

② LHLD F251. \rightarrow L = 50H, H = F2H.
 INX H \rightarrow H = F2H, L = 51H. $\xrightarrow{F2}$ i.e. M = 50H.
 INR M \rightarrow M+1 = 51H.
 MOV C, M. \rightarrow C = 51H.

C = ?

$C = 51H$

③ LXI D, F252. \rightarrow DE = F252H
 LXI H, F253. \rightarrow $HL = F253H$ \Rightarrow M = 04H.

LOAX D. ((DE)) \rightarrow A i.e. (F252) \rightarrow A. A \rightarrow F2.

ADD M A+M = F2 + 04H = A.

A = ? A = 06H with CY=1.

Ex-4 Find the Value of Accumulator after executing the following program.

(4)	(3) Address	(1) Mnemonics	(2) Opcode
execute	3000, 01	MVI A, 36	3E, 36 \Rightarrow A = 36
	3002, 03	ADI 40h	82, 40. \Rightarrow A + 40 \Rightarrow A = 76
	3004, 05106	STA 3007	32, 07, 30.
	3007	XRA A HLT	AF 76
	3008	HLT	76.

* 'XRA A' instⁿ is not executed because its opcode 'AF' is replace by '76' which is opcode of HLT Instruction.

(4) Branching Instructions:


* Unconditional Jump.

Sr. No.	Instruction	Operation	B M T	Addr.
D	(a) JMP 16 bit address	16 bit addr → PC	3 3 10	(RRR).

e.g. PC ⇒ 3800

3806, 07, 08
PC ⇒ ~~3807~~


PC = 8250
8251

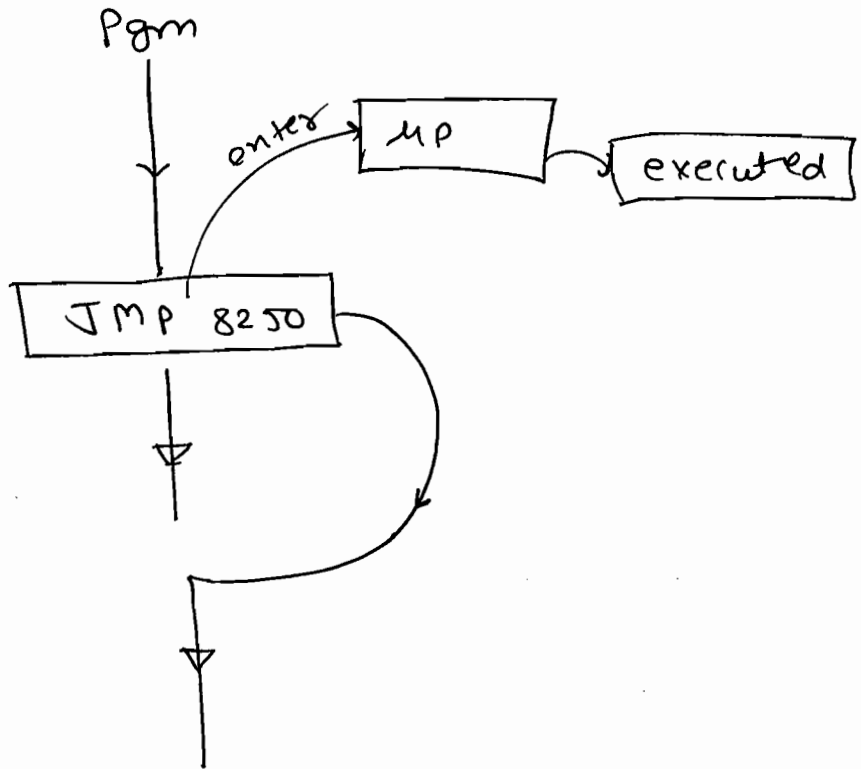

* Conditional Jump:

(b) Jc 16 bit address ⇒ If CY = 1 ← True
16 bit addr → PC

① and ② and CY = ?

 

Instruction	Address	Operation	True
→ JNC	16 bit address	⇒ If	CY = 0
- JZ	16 bit add.	⇒ If	Z = 0
→ JNZ	16 bit add.	⇒ If	Z = 1

→ JM 16 bit address ⇒ $\frac{\text{True}}{If \boxed{S=1}}$
 Jump on minus

→ JP 16 bit address ⇒ If $\boxed{S=0}$
 Jump on plus


→ JPE 16 bit address ⇒ If $\boxed{P=1}$
 Jump on parity even

JPO 16 bit address ⇒ If $\boxed{P=0}$
 Jump on parity odd

* Unconditional Call:

- 2) (a) CALL 16 bit address.
 (1) (2) (3) (4)
 (a) $PC_H \rightarrow (SP-1)$
 $PC_L \rightarrow (SP-2)$ cmd $SP = SP - 2$.
 (b) 16 bit addr $\rightarrow PC$.

(Eg.) 3/5/18
(S.R.R.W.)

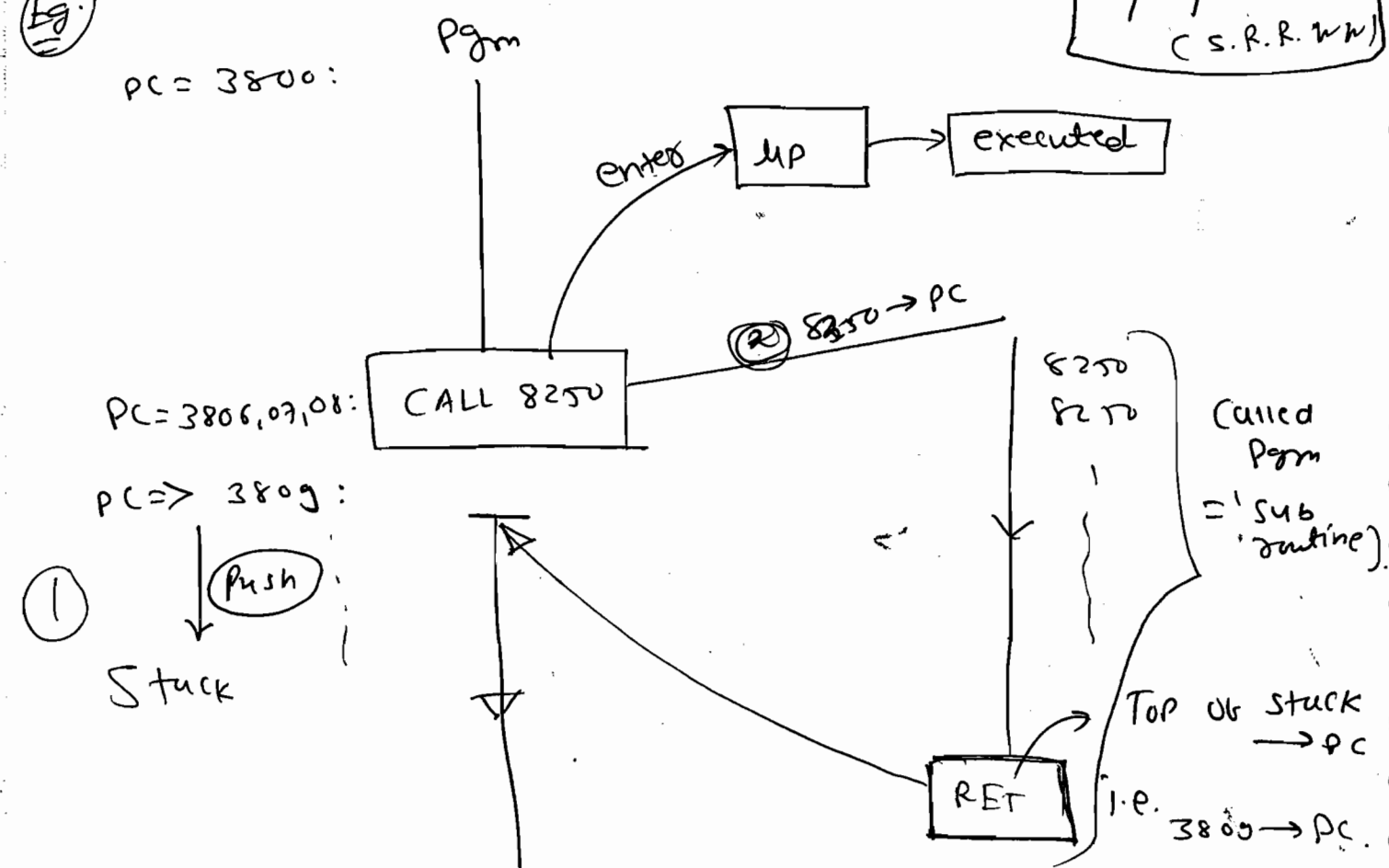

* Conditional CALL:

(b) CC 16 bit add.
 ↓ ↓ ↓
 5 ① ② ③

If CY=1
 (a) $PC_H \xrightarrow{⑥} ((SP-1))$
~~(b)~~ $\rightarrow PC_L \xrightarrow{⑤} ((SP-2))$
 (b) 16 bit add. $\rightarrow PC$.

(3 | 5 | 18)
 S.P.R.WW
 SP = SP - 2.
 ✓

\rightarrow CNC 16 bit add.

True
 (a) if CY=0

3 | 2 | 9 ← False

 3 | 5 | 18 ← True
 ✓

\rightarrow CZ 16 bit add.

if Z=1
~~Z=0~~

\rightarrow CNZ 16 bit add.

if Z=0

\Rightarrow CM 16 bit add.

\Rightarrow If S=1

CP 16 bit add.

\Rightarrow If S=0

CPE 16 bit add.

\Rightarrow If P=1

CPO 16 bit add.

\Rightarrow If P=0


(3) a) RET \Rightarrow Top of stack $\rightarrow PC$
 i.e. $((SP)) \xrightarrow{⑥} PC_L$
 $((SP+1)) \xrightarrow{⑤} PC_H$
 similar to POP Instⁿ.

(2 | 3 | 10)
 (C.F.R.R.)
 ✓
 and SP = SP + 2.

- b) Conditions
- RC ✓
 - RNC ✓
 - RE ✓
 - RNZ ✓
 - RM ✓
 - RP ✓
 - RPE ✓
 - RPO ✓


2 | $\frac{1}{3}$ | $\frac{4+2}{10} = 6T$ ← False
 10 ← True

Ex-1

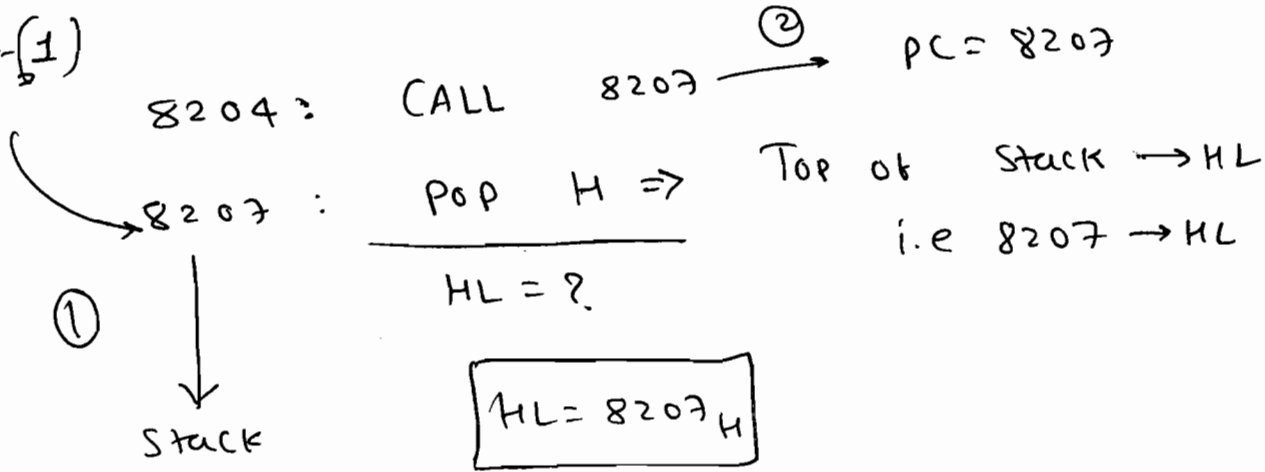


Ex-2 In the following program determine the return address of the Subroutine

LXI D, 705F \Rightarrow DE = 705F

 

 
Ex-3 Determine the acc. value after executing the following program



⑤ Machine related, I/O Instruction: III

- 1) a) NOP No operation 1 | 1 | 4. (a) Delay
 (b) To avoid Addr. Relocation.
 b) HLT μ is halted 1 (2 (or) more) | 5 (or) more.

E.g. NOP


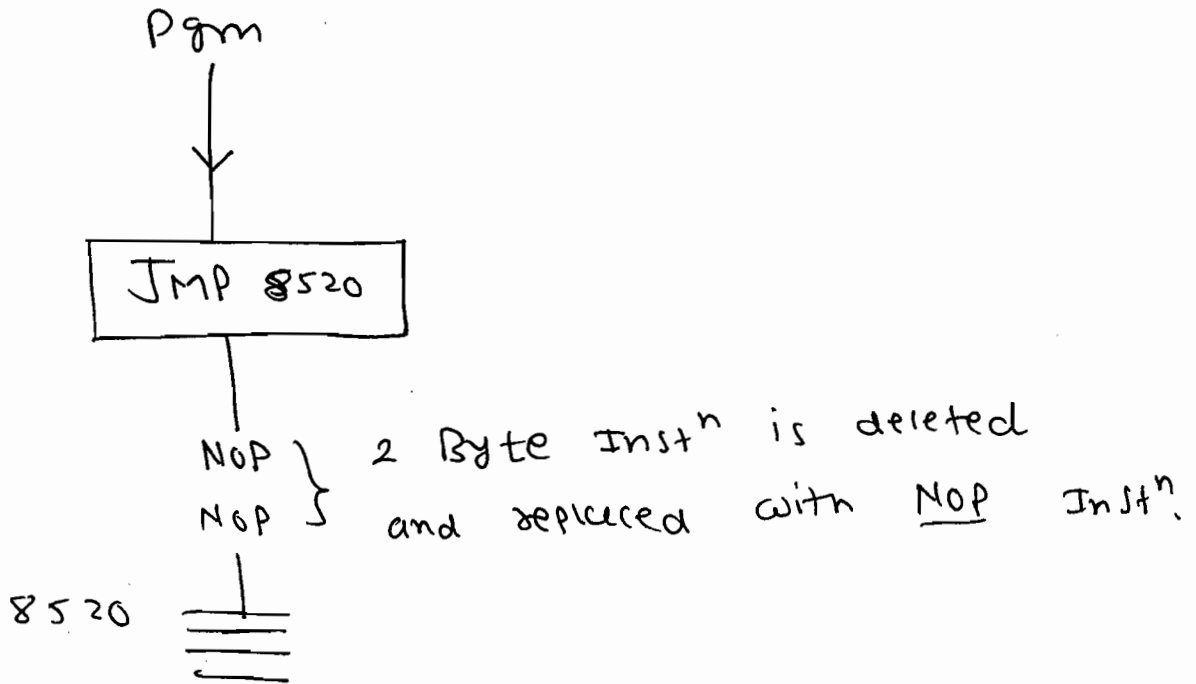


* HLT:


- After executing the halt instruction:
- (i) it enters into halt acknowledgement machine cycle.
 - (ii) the Buses are tristated.
 - (iii) Registers values are uncorrected.
 - (iv) Either reset (or) interrupt is required to bring the μ out of the halt state.

⇒ As a Good program we have to use BPI (Break point ~~point~~ ^{interrupt}) instead of HLT *
 as it takes less time^s than of HLT for executing.

2)
Used in
"I/O mapped
I/O mode".

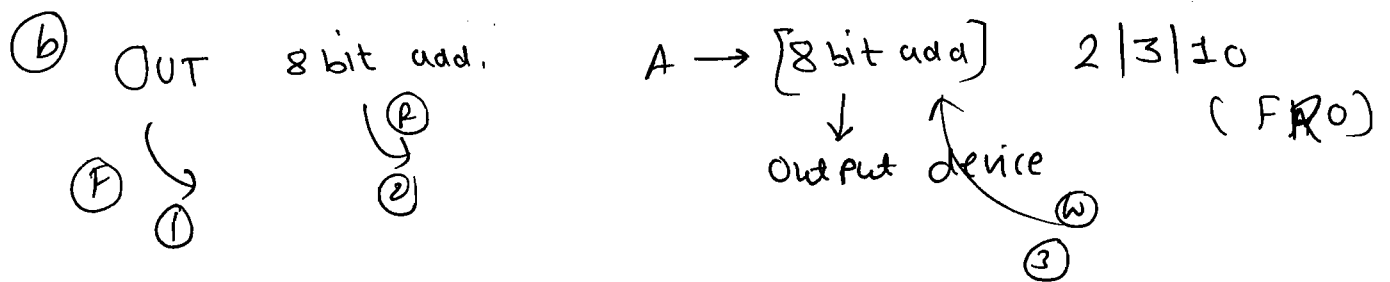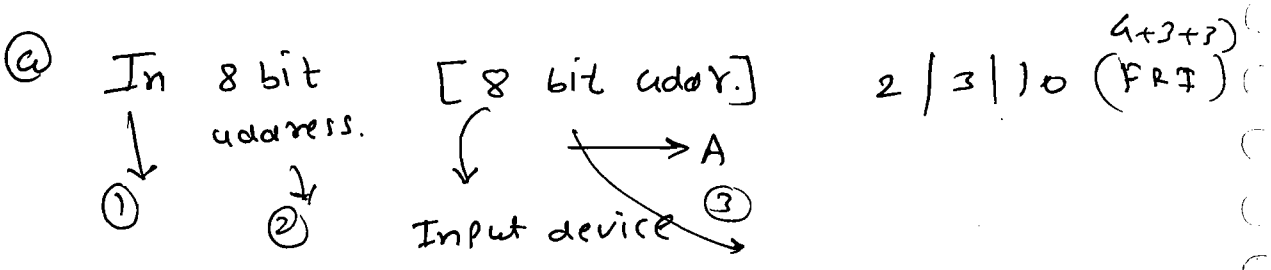

* IN 84_H
OUT FA_H.

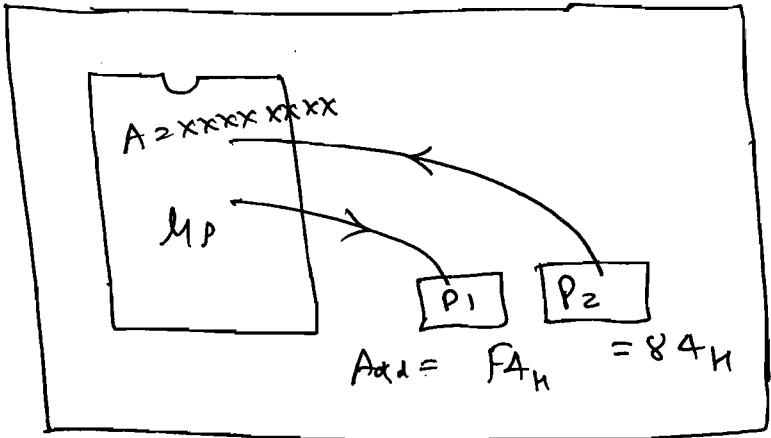

Ex-1 After executing the following program determine which port receives the data

```
MVI A, 87H. => A = 87H
```

```
MOV B, A. => B = 87H
```

Ans: PORT 2.

```
Again: JMP Next
XRA B
OUT PORT 1
HLT
```

```
Next: XRA B 87H A ⊕ B => A = 00H.
```

0000 0000
+ 1000 0111


1000 0111
=> 87H.
1000 0111
=> True False

```
JP Again
OUT PORT 2 ← Acc = 87H
HLT
```

$\Rightarrow 87_H$ is sent to PORT2.

Ex-2 The following Program sends signed no. in 2's Comp. form from port-1 when the execution of the program stops?

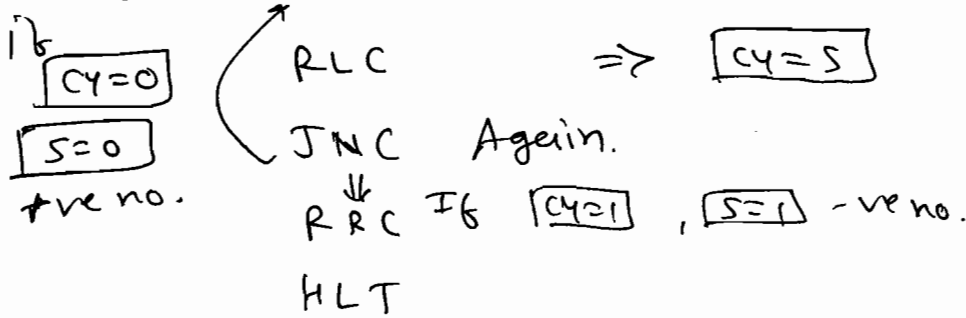Again: In port 1 ~~Port 1~~ \Rightarrow PORT 1 $\rightarrow A = Sxxx xxxx_2$



\Rightarrow the above program stops the execution when it reads a -ve no. from port-1.


6 Additional Instruction:

① @ DI Disable Interrupts 1114

\Rightarrow $\begin{cases} RST 7, 5, 6, 5, 5, \\ INTR \text{ are disabled.} \end{cases}$

② EI Enable Interrupts 1124

\Rightarrow All ints are Enabled.

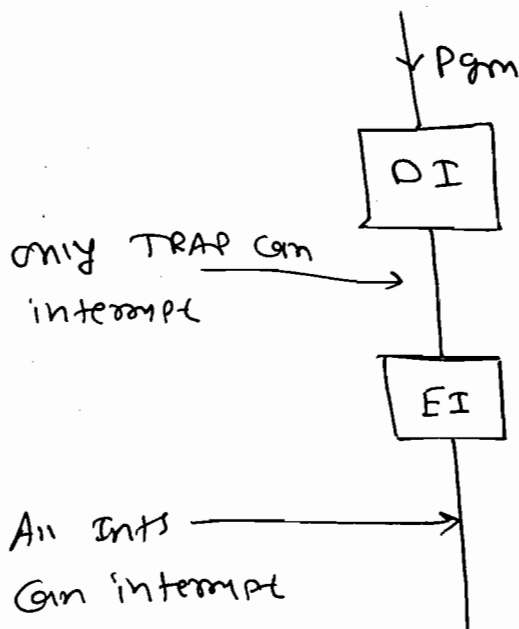

2) DAA Decimal adjust
 Acc $1114 \Rightarrow$ All flags
 are affected.
 (BCD addition).

$$\begin{array}{r} 27_{10} \\ + 36_{10} \\ \hline 63_{10} \end{array}$$

MVI A, 27.

MVI B, 36

ADD B $\Rightarrow A+B \rightarrow A=50H$

DAA $\Rightarrow A=63$

HLT

$$\begin{array}{r} 27 = 0010 \ 0111 \\ + 36 = + 0011 \ 0110 \\ \hline 0101 \ 1007 \ x \\ + 0000 \ 0110 \\ \hline 0110 \ 0011 \\ \hline 6 \quad 3 \\ = 63 \end{array}$$

Ex-1 Determine the PC value after executing
 the following program.

LXI H, 8A79 $\Rightarrow HL=8A79$.

MOV A, H $\Rightarrow A \rightarrow 8A$

ADD L $\rightarrow A+L \rightarrow A \rightarrow 8A+79$.

DAA $A \rightarrow 69$.

MOV H, A $H \rightarrow 69$.

PCHL $PC \rightarrow \underline{6979}$.

PC = ?

$$\begin{array}{r} 1000 \ 1000 \\ + 0111 \ 1001 \\ \hline 10000 \ 0011 \\ 0110 \ 0110 \\ \hline 0110 \ 1001 \\ 69 \end{array}$$

NOTE: \rightarrow DAA instruction is effective only after
 add instⁿ it doesn't work for BCD subtraction.

Ex-2 Determine the fⁿ of the following program in B & C Register contain BCD numbers

```



MVI A, 99. => A = 99.
SUB C -> A -> 9910 - C = 9's comp. (C)
INR A -> A + 1 -> A -> 10's comp. (C).
ADD B -> B + 10's C -> A.
DAA -> A -> B - C.
      A -> B - C.
HLT ->
  
```


Let, B = 64 ;
 C = 42 ;

99 - C = 99 - 42 = 57 -> A
 10's of A = A = 58H.


3) a) SIM (set Interrupt mask) :

 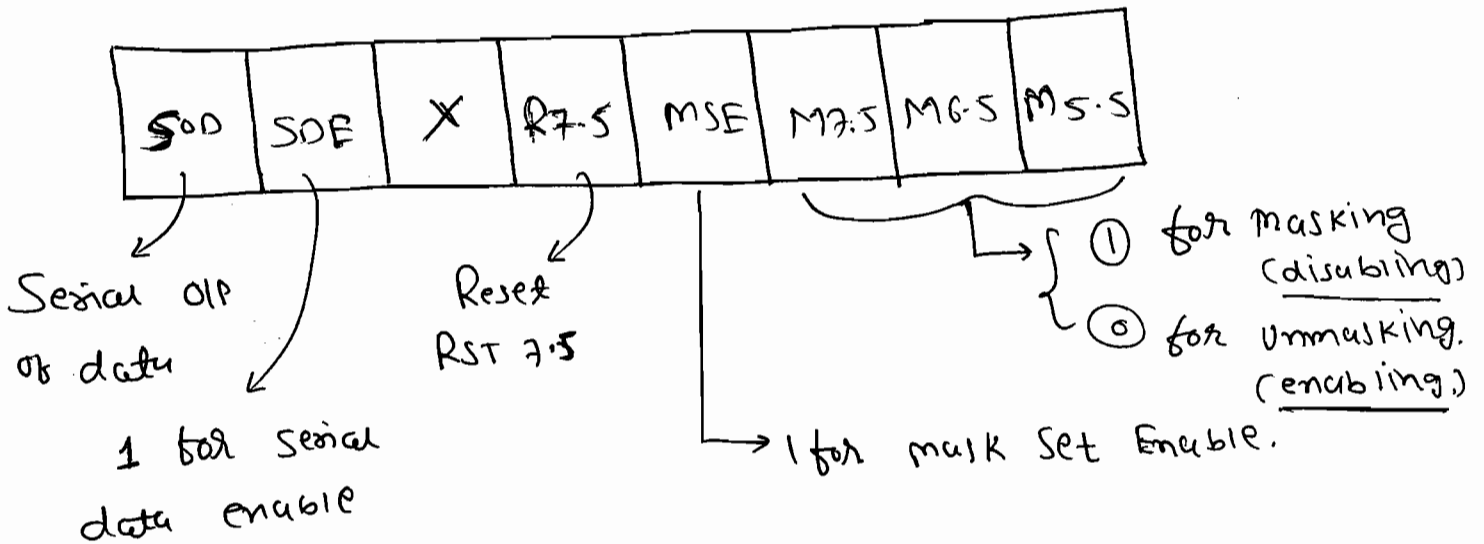- i) selective disabling Interrupts.
- ii) serial output of data.



TRAP 

0024H

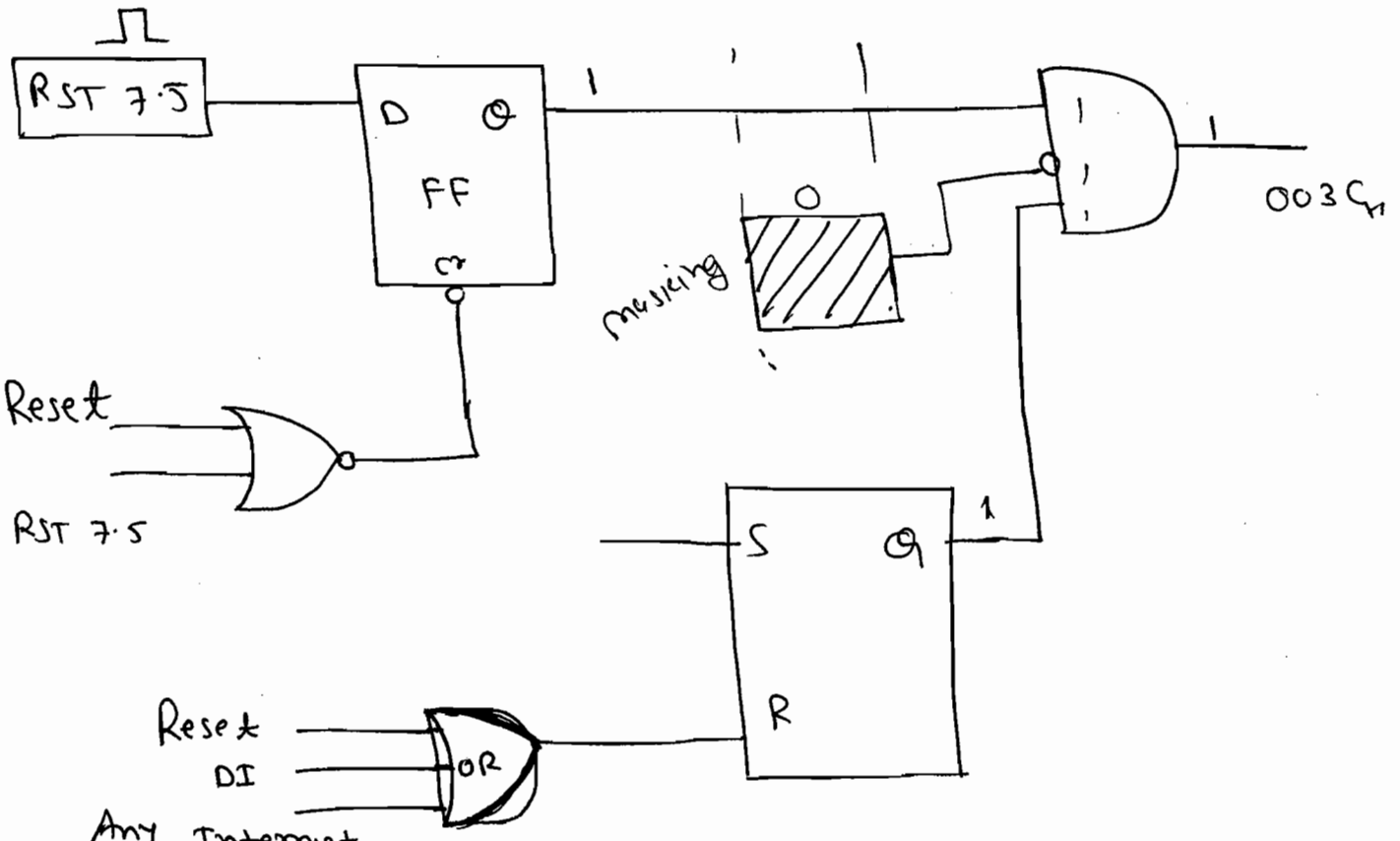

Any Interrupt is recognized.

* For setting RST 7.5 the required values are $\alpha=1$, masking = 0, $\alpha=1$.

Ex-1 Write instructions to mask RST 6.5 and

RST 5.5.


⇒

```
MVI A, 0BH.
SIM
```

⇒ RST 6.5, 5.5 are masked (disabled).

TRAP, RST 7.5
INTR can interrupt

 
Ex-2 Determine the O/P of the following program. 117




b) RIM (Read Interrupt Mask)

- (a) To know status of Interrupts.
 (b) To read serial input [on SIO pin of μP].

1/1/4

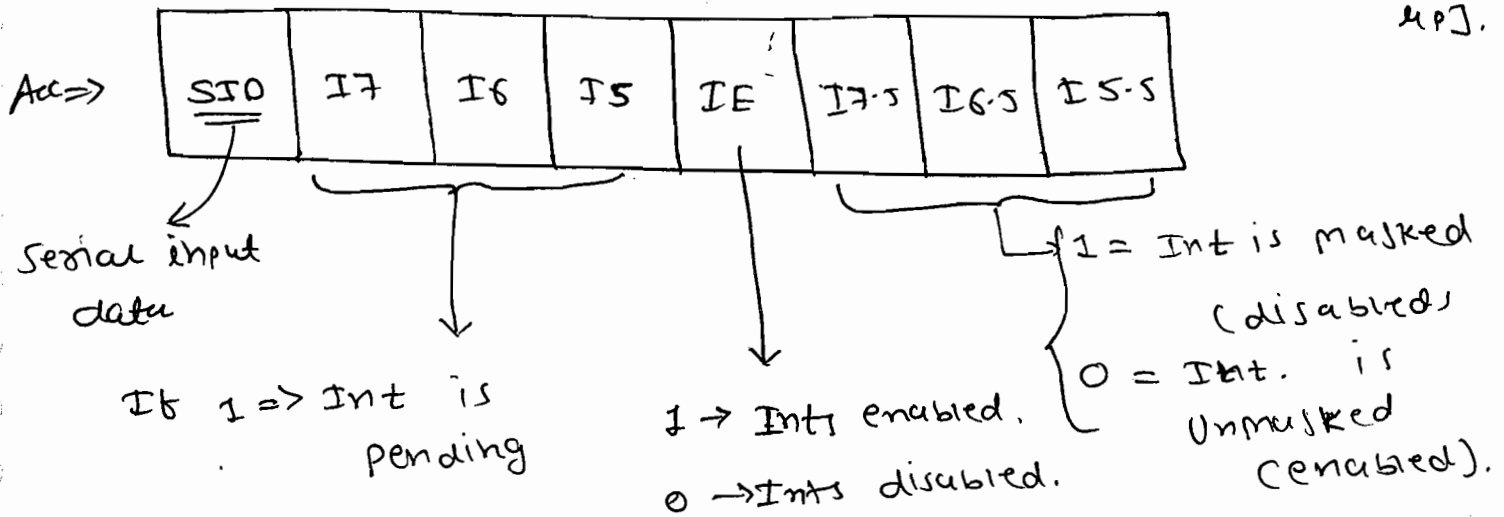


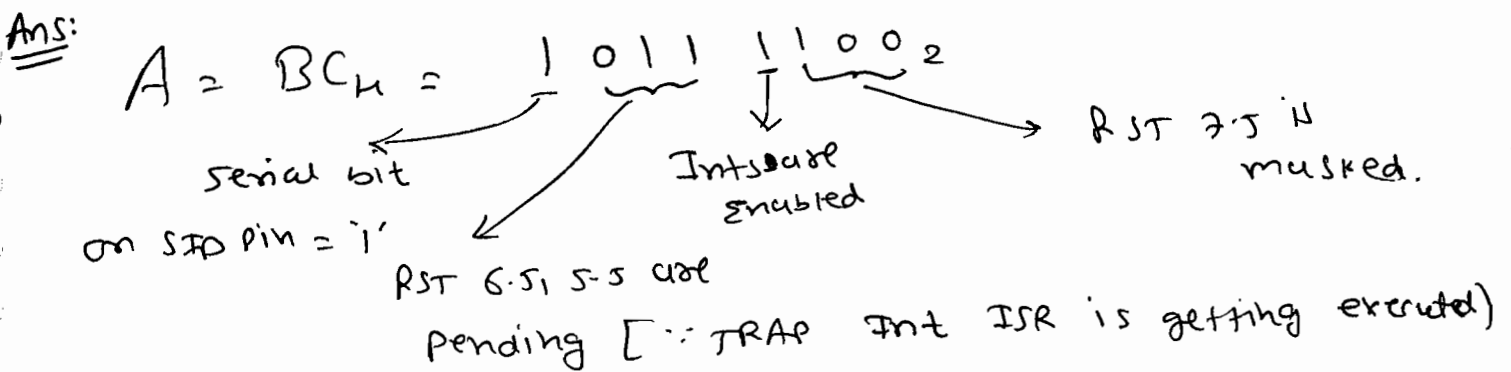Ex-1 After executing RIM instruction the accumulator value is BC_H . Determine the status of the interrupt and the serial input.



⇒ In 8085 μP the interrupts are disabled in the following cases:

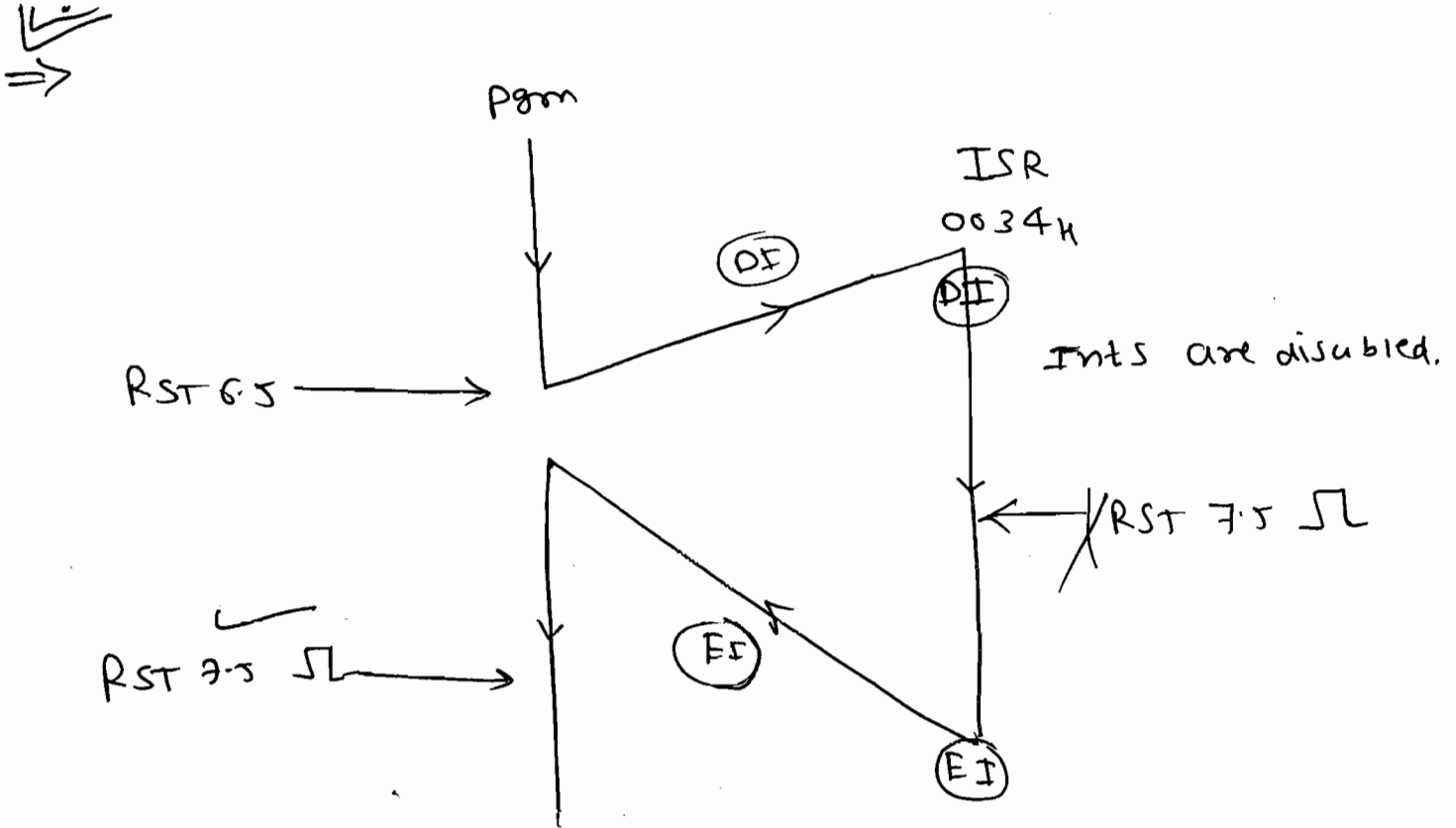- (i) when 'DI' instⁿ is executed.
- (ii) when μP is Reset.
- (iii) when μP Recognizes any one interrupt




* Restart Interrupts (Software Interrupts)!!


⇒ RST n ; n = 0, 1, ..., 6, 7.

Instruction	Opcode	Address
RST 0	C7H	0000H
RST 1	CFH	0008H
RST 2	D7H	0010H
RST 3	OFH	0018H
RST 4	E7H	0020H
RST 5	EFH	0028H
RST 6	F7H	0030H
RST 7	FFH	0038H

Stack.
⊛

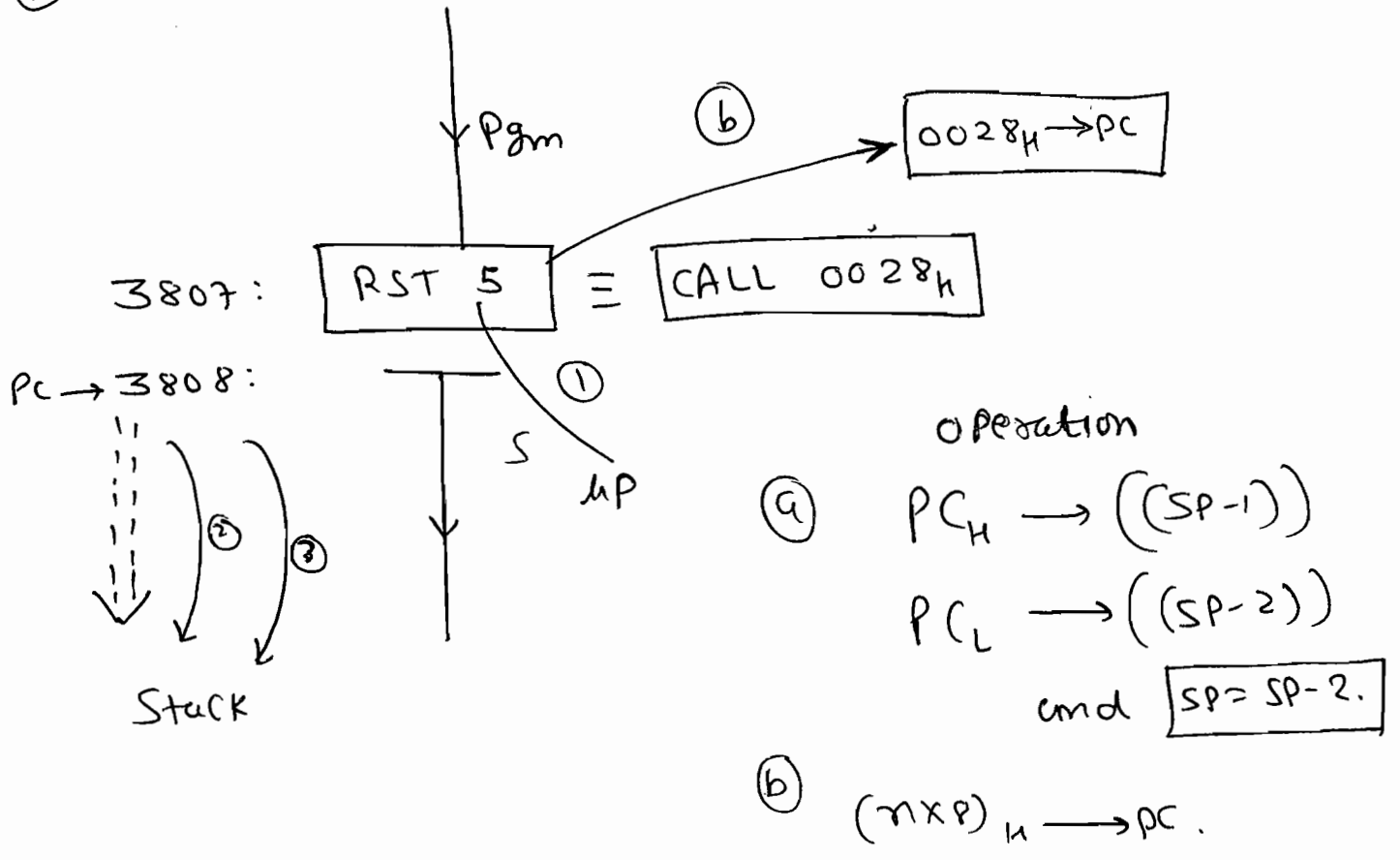


⇒ Providing Addr. Location to NVI INTR:

 

Ex-1 = How many times the following loops will be executed?

Assume initially All the flags are cleared.

(a) LXI B, 0002H Given Z=0.

 

* Infinite loop [∵ only Arith Instrn "DCX B" doesn't affect any flags].

* **Exceptions:**

① $\left. \begin{matrix} \text{ANA} \\ \text{ORA} \\ \text{XRA} \end{matrix} \right\} \Rightarrow \boxed{\text{CY} = 0}$

② $\left. \begin{matrix} \text{INX } R_p \\ \text{DCX } R_p \end{matrix} \right\} \Rightarrow \text{No flags are affected.}$

③ $\left. \begin{matrix} \text{INR } R/M \\ \text{DCR } R/M \end{matrix} \right\} \Rightarrow \text{'CY' flag is not affected.}$

b) $\text{XRA } A \quad \text{given } z=0 \Rightarrow A = 00H \Rightarrow \boxed{Z=1}$
 * $\text{Imp} \text{ * } \text{LXI } B, 0002 \Rightarrow B = 0002H$
 LOOP: $\text{DCX } B \Rightarrow B = 0001H$
 ① $z=0 \rightarrow \text{JNZ LOOP} \rightarrow \boxed{Z=1}$
 ↓ ② $z=1$
 ↓ ③

* only once it is executed.


[∵ $\text{XRA } A$ will set the zero flag.]

Ex-2 In the following program How many times the decrement c instn is executed.

a) $\text{MVI } C, 00H \Rightarrow C = 00H$
 LOOP: $\boxed{\text{DCR } C}$
 ↓ ① $z=0 \rightarrow \text{JNZ LOOP}$
 ↓ ② $z=1$ ③
 C = $FFH = 255_{10}$
 C = $FEH = 254_{10}$
 :
 C = $00H = 0_{10} \quad \boxed{z=1} \Rightarrow$

* DCR C is executed 256 times.

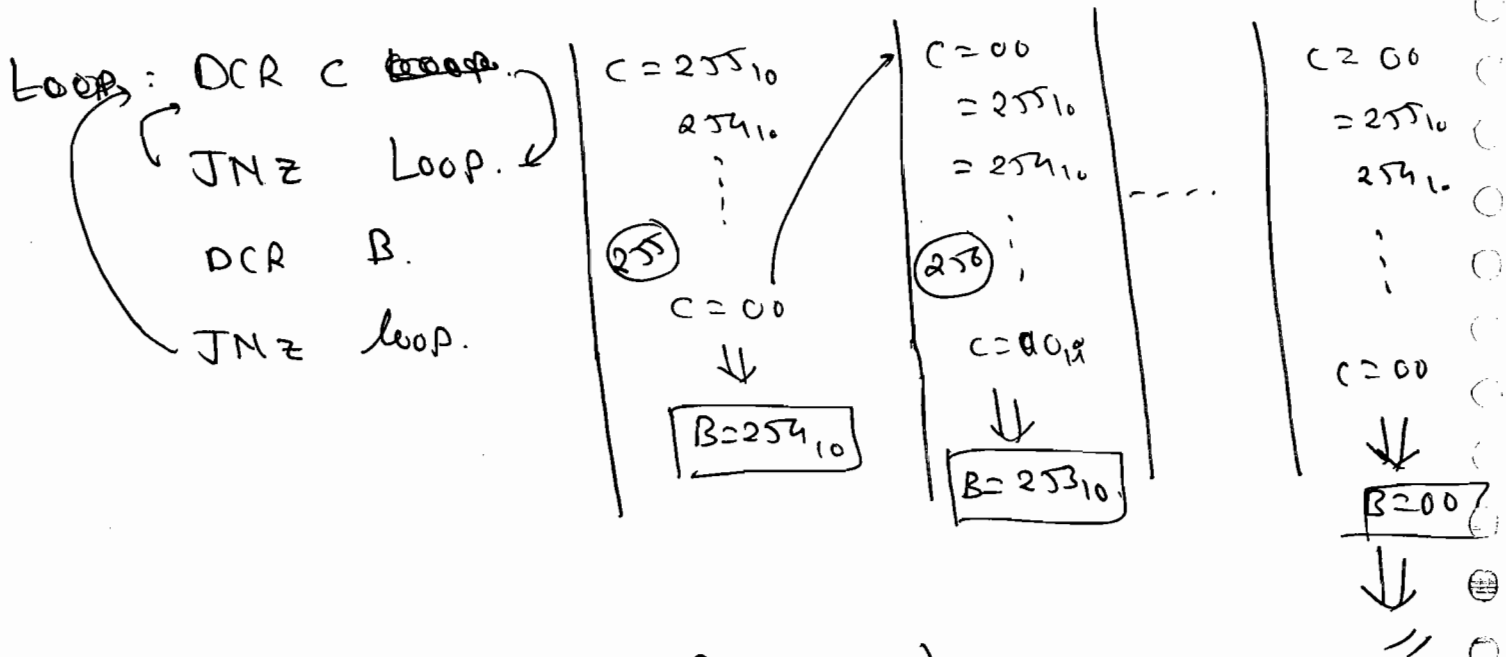b) $\left. \begin{array}{l} \text{MVI B, 255D.} \\ \text{MVI C, 255D.} \end{array} \right\} B = C = 255D$




Ans: $(1 \times 255) + (254 \times 256)$ times.

* 1st time \Rightarrow 255 times.

* Remaining 254 times \Rightarrow 256 times

Hence, $(1 \times 255) + (254 \times 256)$

 c) $\left. \begin{array}{l} \text{MVI B, 255D.} \\ \text{MVI C, 255D.} \end{array} \right\} B = C = 255D$



① Register Addressing Mode:

⇒ Regs | R_n

Eg. (i) MOV C, A

→ A → C

(ii) ADD R


→ A + R → R

(iii) DAD R_p

→ HL + R_p → HL.

② Direct Addressing Mode:


→ It involves memory access.

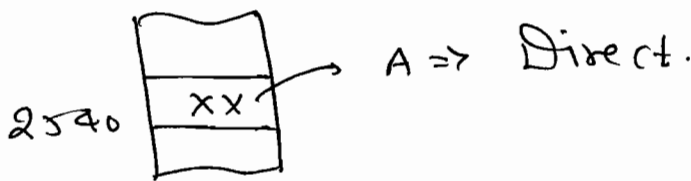e.g.: (i) LDA 2540 ⇒ 

memory
→ ↓ Address is given directly.


③ Register Indirect Addressing Mode:

→ memory Address is specified by R_p & R.

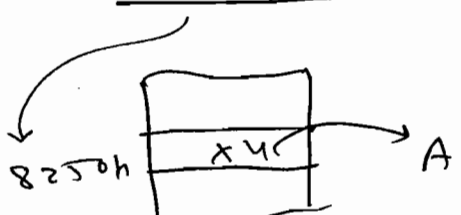e.g.: (i) LDAX B ⇒ BC = 8250H


So, Reg indirect.

 (ii) Push H \Rightarrow SP = A000H. \Rightarrow Reg. Indirect



④ Immediate Addressing Mode:

\Rightarrow Source operand is always 8 bit / 16 bit value.

E.g. : (i) MVI C, 32 \Rightarrow $\boxed{32 \rightarrow C}$

(ii) ADI 45 \Rightarrow $\boxed{A + 45 \rightarrow A}$

(iii) LXI B, 1020h \Rightarrow $\boxed{1020h \rightarrow BC}$

(iv) XRI 30h \Rightarrow $A \oplus 30 \rightarrow A$

⑤ Implicit / Implied Addressing Mode:

\Rightarrow Source and destination are predefined.

E.g. RAL, RAR, CMA, CMC, STC, PCHL, XCHG, PCHL, XTHL.

Ex-1 Determine the addressing modes of the following instructions:

1) LHLD 9A00. \rightarrow Direct


2) MOV C, M \rightarrow Reg. Indirect

3) NOP/HLT \rightarrow ~~Implicit~~ & ~~Implied~~ NO Addr. mode.

4) JMP 8250 \rightarrow $\boxed{8250 \rightarrow PC}$ \rightarrow Immediate

5) MVI M, 32. \Rightarrow Reg. Indirect and also Immediate.

6) RET. \Rightarrow Reg. Indirect.

 

7) CALL 3800 \Rightarrow Reg. Indirect / Immediate.

8) DAA \Rightarrow Implied.

P) Which of the following Instⁿ is getting executed given the following:

Address : 4040h

Data : 44h

$\overline{IO}/\overline{M}apped \overline{IO} \leftarrow \overline{IO} / \overline{M} : 1$

$\overline{X} \overline{RD} : 1$

$\overline{WR} : 0$
Writing \leftarrow

(a) IN 40h

(b) IN 44h.

(c) OUT 40h

(d) OUT 44h

P) Which of the following will store the value of accumulator into a output device, whose address is $F250h \rightarrow$ mem. mapped IO

(i) LXI H, F250
MOV A, M

(iii) LXI H, F250
OUT F250

(ii) LXI H, F250
OUT M

(iv) LXI H, F250
MOV M, A.

$\rightarrow A \rightarrow M$

$A \rightarrow$ i.e. output device.

* Delay Program:

T-States

1) MVI B, FF

7T

Loop: DCR B

4T

JNZ LOOP.

7T / 10T

False

True

≈ 10T

⇒ $T_D = T_0 + T_L;$

T_0 = Delay outside Loop.

$T_0 = 7T = (7 \times 320ns)$

T_L = Delay within the loop.

$= (\text{Count}_{10} \times \text{NO. of T-states in loop} \times T)$

$T_L = (255_{10} \times 14 \times 320ns)$

∴ $T_D = (7 \times 320ns) + (255 \times 14 \times 320ns) - (3 \times 320ns)$
↑
correction.

2) LXI B, FFFF_h

10T

Loop: DCX B

6T

MOV A, C

4T

ORA B

4T

JNZ LOOP

10T / 9T

↓ 2=1

True

False

$$\Rightarrow T_0 = 10T = [10 \times 320ns]$$


$$T_L = [Count_{10} \times 24T]$$

$$= [65,535 \times 24 \times 320ns]$$

$$\therefore T_D = T_0 + T_L$$

$$T_D = [10 \times 320ns] + [65,535 \times 24 \times 320ns]$$

* Nested loop: (Loop within loop).

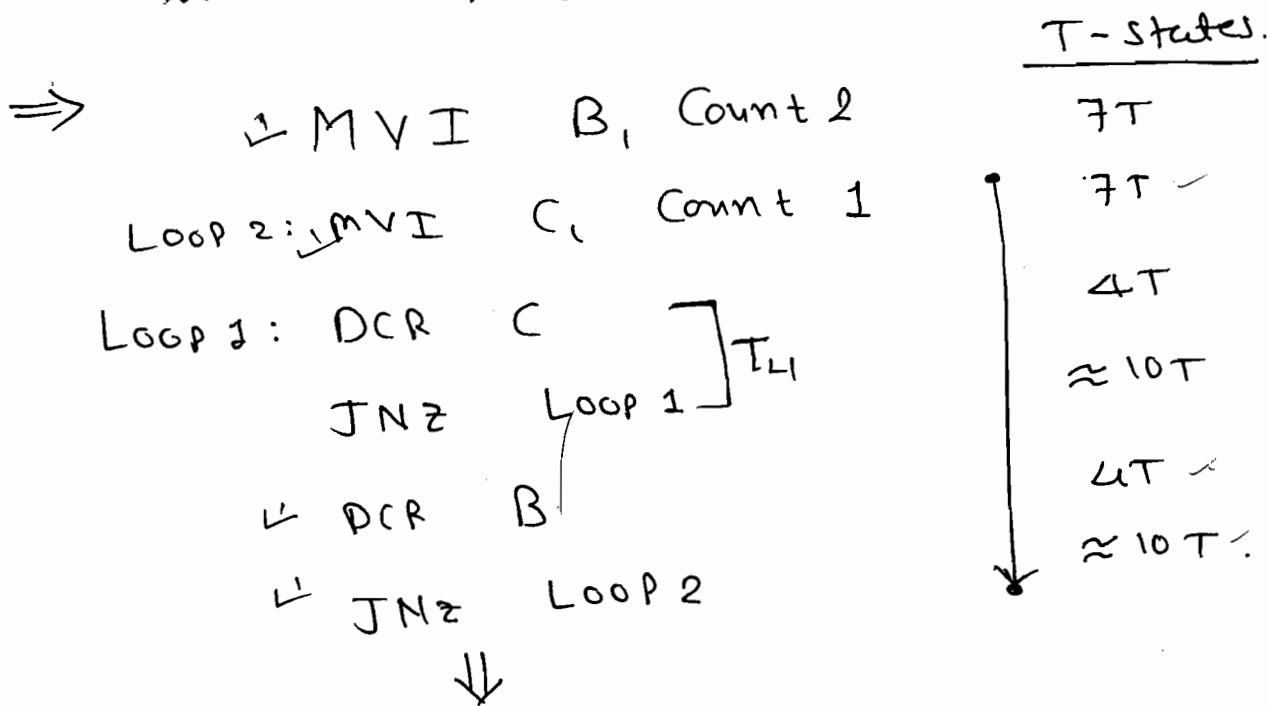

$$T_D = [21T + T_{L1}] \text{Count}_{2,10} + [7 \times 320ns] - [Count_2 \times 3T] - [3T]$$

Where $T_{L1} = [Count_{1,10} \times 14 \times 320ns]$

$$* T_D = (21T + T_{L1}) \text{Count}_{2,10} + (7 \times 320ns) - [Count_2 + 1] 3T$$

→ JNZ Loop 1 is false Count 2 times. 129

⇒ Subtract [Count 2 × 3T].

JNZ loop 2 is false only one time.

⇒ Subtract 3T.

* General Points:

- ① (a) 1-Byte unconditional CALL Instruction = RSTn
(b) 1-Byte unconditional JMP Instruction = PCHL

② The PMA input HOLD is having the preference over non-maskable interrupt TRAP.

③ \checkmark μp checks the ready pin in 'T₂' state of each machine cycle. If it finds it as 'zero' it inserts wait T-states both T₂ & T₃ until the ready becomes one.

④ How to shift 16 bit data towards left by 1 bit?



⇒ i) Store 16 bit no. into HL pair.

ii) Use DAD H instruction.

$$\begin{array}{r} \text{HL} = 0000 \quad 0000 \quad 0000 \quad 0100_2 = 4_{10} \\ + \text{HL} = 0000 \quad 0000 \quad 0000 \quad 1000_2 = 8_{10} \\ \hline \underline{\text{HL}} \end{array}$$

⑤ In I/O mapped I/O Mode can we give the same address to a input device and output device?

  ⇒ Yes, because they can be recognized based on their control signals. Hence, in this mode we can connect 256 input devices and 256 output devices in total 512.



Addr = F4H

Addr = F4H

8085
MP

- ① Address ⇒ $A_{15} - A_0 = F4H$ | $A_{15} - A_8 = F4H$
- ② Control signal ⇒ $\begin{cases} I/O\bar{M} = 1 \\ \overline{WR} = 0 \end{cases}$ → output device.
- ③ Data